



Microcoded Instruction Set Processor

LABORATORY 2

CS2022 COMPUTER ARCHITECTURE

ALEXANDRU SULEA
D STREAM
#12315152
8 APRIL 2016

Contents

List of Tables	2
1 CODE	1
1.1 Microcoded Instruction Set Processor	1
1.2 Memory M	5
1.3 Micro-Programmed Control	16
1.3.1 CAR	20
1.3.2 MUX8 TO 1BIT	21
1.3.3 MUX2 TO 8BIT	22
1.3.4 extend	23
1.3.5 IR	24
1.3.6 PC	25
1.3.7 Control Memory	26
1.3.8 zero fill	32
1.4 bit	33
1.5 DATA PATH	34
1.6 REGISTER FILE	37
1.6.1 REG8	41
1.6.2 DECODER	42
1.6.3 MUX3 TO 16BIT	44
1.6.4 MUX8 TO 16BIT	45
1.7 FUNCTION UNIT	47
1.8 SHIFTER	49
1.8.1 MUX3 TO 1BIT	52
1.9 ALU	53
1.9.1 B LOGIC	56
1.9.2 MUX2 TO 1BIT	59
1.9.3 RIPPLE	60
1.9.4 FULL ADDER	63
2 TESTBENCHES	64
2.1 Microcoded Instruction Set Processor	64
2.2 Memory M	66
2.3 Micro Programmed Control	68
2.3.1 CAR	69
2.3.2 MUX8 TO 1BIT	71
2.3.3 MUX2 TO 8BIT	73
2.3.4 extend	75
2.3.5 IR	76
2.3.6 PC	78
2.3.7 Control Memory	80
2.3.8 zero fill	82
2.4 DATA PATH	84
2.5 REGISTER FILE	86
2.5.1 REG8	89
2.5.2 DECODER	91
2.5.3 MUX3 TO 16BIT	94
2.5.4 MUX8 TO 16BIT	96
2.6 FUNCTION UNIT	99
2.7 SHIFTER	103

2.7.1	MUX3 TO 1BIT	105
2.8	ALU	107
2.8.1	LOGIC	110
2.8.2	B LOGIC	112
2.8.3	MUX2 TO 1BIT	114
2.8.4	RIPPLE	116
2.8.5	FULL ADDER	118

List of Tables

1 CODE

1.1 Microcoded Instruction Set Processor

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity microprogrammed_control is
    Port ( IR_mpc : in STD_LOGIC_VECTOR(15 downto 0);
          status_mpc : in STD_LOGIC_VECTOR(3 downto 0);
          reset_mpc : in STD_LOGIC;
          control_mpc : out STD_LOGIC_VECTOR(17 downto 0);
          PC_mpc : out STD_LOGIC_VECTOR(15 downto 0);
          MC_in_mpc : out STD_LOGIC;
          MC_TD_mpc : out STD_LOGIC;
          MC_TA_mpc : out STD_LOGIC;
          MC_TB_mpc : out STD_LOGIC);
end microprogrammed_control;
architecture Behavioral of microprogrammed_control is

    component mux8_1bit Port (
        in_00 : in STD_LOGIC;
        in_11 : in STD_LOGIC;
        in_C2 : in STD_LOGIC;
        in_V3 : in STD_LOGIC;
        in_Z4 : in STD_LOGIC;
        in_N5 : in STD_LOGIC;
        in_C6 : in STD_LOGIC;
        in_Z7 : in STD_LOGIC;
        in_MS : in STD_LOGIC_VECTOR(2 downto 0);
        MUXS_out : out STD_LOGIC);
    end component;

    component mux2_8bit Port (
        in_0 : in STD_LOGIC_VECTOR(7 downto 0);
        in_1 : in STD_LOGIC_VECTOR(7 downto 0);
        in_MC : in STD_LOGIC;
        MUXC_out : out STD_LOGIC_VECTOR(7 downto 0));
    end component;

    component CAR Port (
        car_in : in STD_LOGIC_VECTOR(7 downto 0);
        muxs_in : in STD_LOGIC;
        res : in STD_LOGIC;
        car_out : out STD_LOGIC_VECTOR(7 downto 0));
    end component;

    component extend Port (
        E_in : in STD_LOGIC_VECTOR(5 downto 0);
        E_out : out STD_LOGIC_VECTOR(15 downto 0));
    end component;
```

```

component IR Port (
    IR_in : in STD_LOGIC_VECTOR(15 downto 0);
    IL : in STD_LOGIC;
    opcode : out STD_LOGIC_VECTOR(6 downto 0);
    DR : out STD_LOGIC_VECTOR(2 downto 0);
    SA : out STD_LOGIC_VECTOR(2 downto 0);
    SB : out STD_LOGIC_VECTOR(2 downto 0));
end component;

component PC Port (
    PC_in : in STD_LOGIC_VECTOR(15 downto 0);
    PL : in STD_LOGIC;
    PI : in STD_LOGIC;
    reset : in STD_LOGIC;
    PC_out : out STD_LOGIC_VECTOR(15 downto 0));
end component;

component control_memory Port (
    car_in : in STD_LOGIC_VECTOR(7 downto 0);
    NA : out STD_LOGIC_VECTOR(7 downto 0);
    MSout : out STD_LOGIC_VECTOR(2 downto 0);
    MC : out STD_LOGIC;
    IL : out STD_LOGIC;
    PI : out STD_LOGIC;
    PL : out STD_LOGIC;
    TD : out STD_LOGIC;
    TA : out STD_LOGIC;
    TB : out STD_LOGIC;
    MB : out STD_LOGIC;
    FSout : out STD_LOGIC_VECTOR(4 downto 0);
    MD : out STD_LOGIC;
    RW : out STD_LOGIC;
    MM : out STD_LOGIC;
    MW : out STD_LOGIC);
end component;

signal src_mpc_in : STD_LOGIC_VECTOR(5 downto 0);
signal src_mpc_out : STD_LOGIC_VECTOR(15 downto 0);
signal src_control : STD_LOGIC_VECTOR(17 downto 0);
signal src_opcode, src_car_in, src_car_out, src_na : STD_LOGIC_VECTOR(7 downto 0);
signal src_ms, src_sa, src_sb, src_dr : STD_LOGIC_VECTOR(2 downto 0);
signal src_mc, src_il, src_car_sig, src_pl, src_pi : STD_LOGIC;

begin
    reg_mux8_1bit: mux8_1bit PORT MAP (
        in_00 => '0',
        in_11 => '1',
        in_C2 => status_mpc(2),
        in_V3 => status_mpc(3),
        in_Z4 => status_mpc(0),
        in_N5 => status_mpc(1),
        in_C6 => not status_mpc(2),
        in_Z7 => not status_mpc(0),
        in_MS => src_ms,
        MUXS_out => src_car_sig);

```

```

reg_mux2_8bit :mux2_8bit PORT MAP (
    in_0 => src_na,
    in_1 => src_opcode,
    in_MC => src_mc,
    MUXC_out => src_car_out);

reg_CAR: CAR PORT MAP (
    car_in => src_car_out,
    muxs_in => src_car_sig,
    res => reset_mpc,
    car_out => src_car_in);

reg_extend : extend PORT MAP (
    E_in => src_mpc_in,
    E_out => src_mpc_out);

reg_IR : IR PORT MAP (
    IR_in => IR_mpc,
    IL => src_il,
    opcode => src_opcode(6 downto 0),
    DR => src_dr,
    SA => src_sa,
    SB => src_sb);

reg_PC : PC PORT MAP (
    PC_in => src_mpc_out,
    PL => src_pl,
    PI => src_pi,
    reset => reset_mpc,
    PC_out => PC_mpc);

reg_control_memory : control_memory PORT MAP (
    car_in => src_car_in,
    NA => src_na,
    MSout => src_ms,
    MC => src_mc,
    IL => src_il,
    PI => src_pi,
    PL => src_pl,
    TD => MC_TD_mpc,
    TA => MC_TA_mpc,
    TB => MC_TB_mpc,
    MB => src_control(8),
    FSout => src_control(7 downto 3),
    MD => src_control(2),
    RW => src_control(1),
    MM => src_control(0),
    MW => MC_in_mpc);

src_mpc_in(5 downto 3) <= src_dr;
src_mpc_in(2 downto 0) <= src_sb;

src_opcode(7) <= '0';
src_control(17 downto 15) <= src_dr;
src_control(14 downto 12) <= src_sa;
src_control(11 downto 9) <= src_sb;

```

```
    control_mpc <= src_control;  
end Behavioral;
```

1.2 Memory M

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity memory_m is
Port ( data_in : in STD_LOGIC_VECTOR(15 downto 0);
      mw : in STD_LOGIC;
      address_in : in STD_LOGIC_VECTOR(15 downto 0);
      data_out : out STD_LOGIC_VECTOR(15 downto 0));
end memory_m;

architecture Behavioral of memory_m is
    type mem_array is array(0 to 511) of STD_LOGIC_VECTOR(15 downto 0);

begin
    mem_process : process(data_in, address_in, mw)
        variable data_mem : mem_array := (

--0
            x"0000", --0
            x"0000", --1
            x"0241", --2
            x"0482", --3
            x"0964", --4
            x"0165", --5
            x"0982", --6
            x"A528", --7
            x"0000", --8
            x"0000", --9
            x"1AAA", --A
            x"11B7", --B
            x"1E54", --C
            x"1D85", --D
            x"1547", --E
            x"1528", --F
--1
            x"4568", --0
            x"5622", --1
            x"EE52", --2
            x"ED56", --3
            x"AB85", --4
            x"0000", --5
            x"0000", --6
            x"0000", --7
            x"0000", --8
            x"0000", --9
            x"0000", --A
            x"0000", --B
            x"0000", --C
            x"0000", --D
            x"0000", --E
            x"0000", --F
```



```

--2
x"0000", --0
x"0000", --1
x"0000", --2
x"0000", --3
x"0000", --4
x"0000", --5
x"0000", --6
x"0000", --7
x"0000", --8
x"0000", --9
x"0000", --A
x"0000", --B
x"0000", --C
x"0000", --D
x"0000", --E
x"0000", --F
--3
x"0000", --0
x"0000", --1
x"0000", --2
x"0000", --3
x"0000", --4
x"0000", --5
x"0000", --6
x"0000", --7
x"0000", --8
x"0000", --9
x"0000", --A
x"0000", --B
x"0000", --C
x"0000", --D
x"0000", --E
x"0000", --F
--4
x"0000", --0
x"0000", --1
x"0000", --2
x"0000", --3
x"0000", --4
x"0000", --5
x"0000", --6
x"0000", --7
x"0000", --8
x"0000", --9
x"0000", --A
x"0000", --B
x"0000", --C
x"0000", --D
x"0000", --E
x"0000", --F
--5
    x"0000", --0
x"0000", --1
x"0000", --2
x"0000", --3

```

```

x"0000", --4
x"0000", --5
x"0000", --6
x"0000", --7
x"0000", --8
x"0000", --9
x"0000", --A
x"0000", --B
x"0000", --C
x"0000", --D
x"0000", --E
x"0000", --F
--6
x"0000", --0
x"0000", --1
x"0000", --2
x"0000", --3
x"0000", --4
x"0000", --5
x"0000", --6
x"0000", --7
x"0000", --8
x"0000", --9
x"0000", --A
x"0000", --B
x"0000", --C
x"0000", --D
x"0000", --E
x"0000", --F

--7
    x"0000", --0
x"0000", --1
x"0000", --2
x"0000", --3
x"0000", --4
x"0000", --5
x"0000", --6
x"0000", --7
x"0000", --8
x"0000", --9
x"0000", --A
x"0000", --B
x"0000", --C
x"0000", --D
x"0000", --E
x"0000", --F
--8
x"0000", --0
x"0000", --1
x"0000", --2
x"0000", --3
x"0000", --4
x"0000", --5
x"0000", --6
x"0000", --7

```

```
x"0000", --8
x"0000", --9
x"0000", --A
x"0000", --B
x"0000", --C
x"0000", --D
x"0000", --E
x"0000", --F
```

```
--9
x"0000", --0
x"0000", --1
x"0000", --2
x"0000", --3
x"0000", --4
x"0000", --5
x"0000", --6
x"0000", --7
x"0000", --8
x"0000", --9
x"0000", --A
x"0000", --B
x"0000", --C
x"0000", --D
x"0000", --E
x"0000", --F
```

```
--A
x"0000", --0
x"0000", --1
x"0000", --2
x"0000", --3
x"0000", --4
x"0000", --5
x"0000", --6
x"0000", --7
x"0000", --8
x"0000", --9
x"0000", --A
x"0000", --B
x"0000", --C
x"0000", --D
x"0000", --E
x"0000", --F
```

```
--B
x"0000", --0
x"0000", --1
x"0000", --2
x"0000", --3
x"0000", --4
x"0000", --5
x"0000", --6
x"0000", --7
x"0000", --8
x"0000", --9
x"0000", --A
```

```

x"0000", --B
x"0000", --C
x"0000", --D
x"0000", --E
x"0000", --F
--C
    x"0000", --0
x"0000", --1
x"0000", --2
x"0000", --3
x"0000", --4
x"0000", --5
x"0000", --6
x"0000", --7
x"0000", --8
x"0000", --9
x"0000", --A
x"0000", --B
x"0000", --C
x"0000", --D
x"0000", --E
x"0000", --F
--D
x"0000", --0
x"0000", --1
x"0000", --2
x"0000", --3
x"0000", --4
x"0000", --5
x"0000", --6
x"0000", --7
x"0000", --8
x"0000", --9
x"0000", --A
x"0000", --B
x"0000", --C
x"0000", --D
x"0000", --E
x"0000", --F

--E
    x"0000", --0
x"0000", --1
x"0000", --2
x"0000", --3
x"0000", --4
x"0000", --5
x"0000", --6
x"0000", --7
x"0000", --8
x"0000", --9
x"0000", --A
x"0000", --B
x"0000", --C
x"0000", --D
x"0000", --E

```

```

x"0000", --F
--F
x"0000", --0
x"0000", --1
x"0000", --2
x"0000", --3
x"0000", --4
x"0000", --5
x"0000", --6
x"0000", --7
x"0000", --8
x"0000", --9
x"0000", --A
x"0000", --B
x"0000", --C
x"0000", --D
x"0000", --E
x"0000", --F

```

```

--0
x"0000", --0
x"0000", --1
x"0000", --2
x"0000", --3
x"0000", --4
x"0000", --5
x"0000", --6
x"0000", --7
x"0000", --8
x"0000", --9
x"0000", --A
x"0000", --B
x"0000", --C
x"0000", --D
x"0000", --E
x"0000", --F
--1
x"0000", --0
x"0000", --1
x"0000", --2
x"0000", --3
x"0000", --4
x"0000", --5
x"0000", --6
x"0000", --7
x"0000", --8
x"0000", --9
x"0000", --A
x"0000", --B
x"0000", --C
x"0000", --D
x"0000", --E
x"0000", --F
--2

```

```

x"0000", --0
x"0000", --1
x"0000", --2
x"0000", --3
x"0000", --4
x"0000", --5
x"0000", --6
x"0000", --7
x"0000", --8
x"0000", --9
x"0000", --A
x"0000", --B
x"0000", --C
x"0000", --D
x"0000", --E
x"0000", --F
--3
x"0000", --0
x"0000", --1
x"0000", --2
x"0000", --3
x"0000", --4
x"0000", --5
x"0000", --6
x"0000", --7
x"0000", --8
x"0000", --9
x"0000", --A
x"0000", --B
x"0000", --C
x"0000", --D
x"0000", --E
x"0000", --F
--4
x"0000", --0
x"0000", --1
x"0000", --2
x"0000", --3
x"0000", --4
x"0000", --5
x"0000", --6
x"0000", --7
x"0000", --8
x"0000", --9
x"0000", --A
x"0000", --B
x"0000", --C
x"0000", --D
x"0000", --E
x"0000", --F
--5
    x"0000", --0
x"0000", --1
x"0000", --2
x"0000", --3
x"0000", --4

```

```

x"0000", --5
x"0000", --6
x"0000", --7
x"0000", --8
x"0000", --9
x"0000", --A
x"0000", --B
x"0000", --C
x"0000", --D
x"0000", --E
x"0000", --F
--6
x"0000", --0
x"0000", --1
x"0000", --2
x"0000", --3
x"0000", --4
x"0000", --5
x"0000", --6
x"0000", --7
x"0000", --8
x"0000", --9
x"0000", --A
x"0000", --B
x"0000", --C
x"0000", --D
x"0000", --E
x"0000", --F

--7
    x"0000", --0
x"0000", --1
x"0000", --2
x"0000", --3
x"0000", --4
x"0000", --5
x"0000", --6
x"0000", --7
x"0000", --8
x"0000", --9
x"0000", --A
x"0000", --B
x"0000", --C
x"0000", --D
x"0000", --E
x"0000", --F
--8
x"0000", --0
x"0000", --1
x"0000", --2
x"0000", --3
x"0000", --4
x"0000", --5
x"0000", --6
x"0000", --7
x"0000", --8

```

```

x"0000", --9
x"0000", --A
x"0000", --B
x"0000", --C
x"0000", --D
x"0000", --E
x"0000", --F

```

```

--9
x"0000", --0
x"0000", --1
x"0000", --2
x"0000", --3
x"0000", --4
x"0000", --5
x"0000", --6
x"0000", --7
x"0000", --8
x"0000", --9
x"0000", --A
x"0000", --B
x"0000", --C
x"0000", --D
x"0000", --E
x"0000", --F
--A
x"0000", --0
x"0000", --1
x"0000", --2
x"0000", --3
x"0000", --4
x"0000", --5
x"0000", --6
x"0000", --7
x"0000", --8
x"0000", --9
x"0000", --A
x"0000", --B
x"0000", --C
x"0000", --D
x"0000", --E
x"0000", --F
--B
x"0000", --0
x"0000", --1
x"0000", --2
x"0000", --3
x"0000", --4
x"0000", --5
x"0000", --6
x"0000", --7
x"0000", --8
x"0000", --9
x"0000", --A
x"0000", --B

```



```

x"0000", --C
x"0000", --D
x"0000", --E
x"0000", --F
--C
    x"0000", --0
x"0000", --1
x"0000", --2
x"0000", --3
x"0000", --4
x"0000", --5
x"0000", --6
x"0000", --7
x"0000", --8
x"0000", --9
x"0000", --A
x"0000", --B
x"0000", --C
x"0000", --D
x"0000", --E
x"0000", --F
--D
x"0000", --0
x"0000", --1
x"0000", --2
x"0000", --3
x"0000", --4
x"0000", --5
x"0000", --6
x"0000", --7
x"0000", --8
x"0000", --9
x"0000", --A
x"0000", --B
x"0000", --C
x"0000", --D
x"0000", --E
x"0000", --F

--E
    x"0000", --0
x"0000", --1
x"0000", --2
x"0000", --3
x"0000", --4
x"0000", --5
x"0000", --6
x"0000", --7
x"0000", --8
x"0000", --9
x"0000", --A
x"0000", --B
x"0000", --C
x"0000", --D
x"0000", --E
x"0000", --F

```

```

--F
x"0000", --0
x"0000", --1
x"0000", --2
x"0000", --3
x"0000", --4
x"0000", --5
x"0000", --6
x"0000", --7
x"0000", --8
x"0000", --9
x"0000", --A
x"0000", --B
x"0000", --C
x"0000", --D
x"0000", --E
x"0000" );

variable addr : integer range 0 to 511;
variable address_out : STD_LOGIC_VECTOR(15 downto 0);
begin
    addr := conv_integer(data_in(8 downto 0));
    address_out := data_mem(addr);
    if mw = '1' then
        data_mem(addr) := address_in;
    else
        data_out <= address_out;
    end if;
end process;
end Behavioral;

```

1.3 Micro-Programmed Control

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity microprogrammed_control is
    Port ( IR_mpc : in STD_LOGIC_VECTOR(15 downto 0);
          status_mpc : in STD_LOGIC_VECTOR(3 downto 0);
          reset_mpc : in STD_LOGIC;
          control_mpc : out STD_LOGIC_VECTOR(17 downto 0);
          PC_mpc : out STD_LOGIC_VECTOR(15 downto 0);
          MC_in_mpc : out STD_LOGIC;
          MC_TD_mpc : out STD_LOGIC;
          MC_TA_mpc : out STD_LOGIC;
          MC_TB_mpc : out STD_LOGIC);
end microprogrammed_control;
architecture Behavioral of microprogrammed_control is

    component mux8_1bit Port (
        in_00 : in STD_LOGIC;
        in_11 : in STD_LOGIC;
        in_C2 : in STD_LOGIC;
        in_V3 : in STD_LOGIC;
        in_Z4 : in STD_LOGIC;
        in_N5 : in STD_LOGIC;
        in_C6 : in STD_LOGIC;
        in_Z7 : in STD_LOGIC;
        in_MS : in STD_LOGIC_VECTOR(2 downto 0);
        MUXS_out : out STD_LOGIC);
    end component;

    component mux2_8bit Port (
        in_0 : in STD_LOGIC_VECTOR(7 downto 0);
        in_1 : in STD_LOGIC_VECTOR(7 downto 0);
        in_MC : in STD_LOGIC;
        MUXC_out : out STD_LOGIC_VECTOR(7 downto 0));
    end component;

    component CAR Port (
        car_in : in STD_LOGIC_VECTOR(7 downto 0);
        muxs_in : in STD_LOGIC;
        res : in STD_LOGIC;
        car_out : out STD_LOGIC_VECTOR(7 downto 0));
    end component;

    component extend Port (
        E_in : in STD_LOGIC_VECTOR(5 downto 0);
        E_out : out STD_LOGIC_VECTOR(15 downto 0));
    end component;

    component IR Port (
        IR_in : in STD_LOGIC_VECTOR(15 downto 0);
```

```

        IL : in STD_LOGIC;
        opcode : out STD_LOGIC_VECTOR(6 downto 0);
        DR : out STD_LOGIC_VECTOR(2 downto 0);
        SA : out STD_LOGIC_VECTOR(2 downto 0);
        SB : out STD_LOGIC_VECTOR(2 downto 0);
    end component;

    component PC Port (
        PC_in : in STD_LOGIC_VECTOR(15 downto 0);
        PL : in STD_LOGIC;
        PI : in STD_LOGIC;
        reset : in STD_LOGIC;
        PC_out : out STD_LOGIC_VECTOR(15 downto 0));
    end component;

    component control_memory Port (
        car_in : in STD_LOGIC_VECTOR(7 downto 0);
        NA : out STD_LOGIC_VECTOR(7 downto 0);
        MSout : out STD_LOGIC_VECTOR(2 downto 0);
        MC : out STD_LOGIC;
        IL : out STD_LOGIC;
        PI : out STD_LOGIC;
        PL : out STD_LOGIC;
        TD : out STD_LOGIC;
        TA : out STD_LOGIC;
        TB : out STD_LOGIC;
        MB : out STD_LOGIC;
        FSout : out STD_LOGIC_VECTOR(4 downto 0);
        MD : out STD_LOGIC;
        RW : out STD_LOGIC;
        MM : out STD_LOGIC;
        MW : out STD_LOGIC);
    end component;

    signal src_mpc_in : STD_LOGIC_VECTOR(5 downto 0);
    signal src_mpc_out : STD_LOGIC_VECTOR(15 downto 0);
    signal src_control : STD_LOGIC_VECTOR(17 downto 0);
    signal src_opcode, src_car_in, src_car_out, src_na : STD_LOGIC_VECTOR(7 downto 0);
    signal src_ms, src_sa, src_sb, src_dr : STD_LOGIC_VECTOR(2 downto 0);
    signal src_mc, src_il, src_car_sig, src_pl, src_pi : STD_LOGIC;

begin
    reg_mux8_1bit: mux8_1bit PORT MAP (
        in_00 => '0',
        in_11 => '1',
        in_C2 => status_mpc(2),
        in_V3 => status_mpc(3),
        in_Z4 => status_mpc(0),
        in_N5 => status_mpc(1),
        in_C6 => not status_mpc(2),
        in_Z7 => not status_mpc(0),
        in_MS => src_ms,
        MUXS_out => src_car_sig);

    reg_mux2_8bit :mux2_8bit PORT MAP (
        in_0 => src_na,

```

```

        in_1 => src_opcode,
        in_MC => src_mc,
        MUXC_out => src_car_out);

reg_CAR: CAR PORT MAP (
    car_in => src_car_out,
    muxs_in => src_car_sig,
    res => reset_mpc,
    car_out => src_car_in);

reg_extend : extend PORT MAP (
    E_in => src_mpc_in,
    E_out => src_mpc_out);

reg_IR : IR PORT MAP (
    IR_in => IR_mpc,
    IL => src_il,
    opcode => src_opcode(6 downto 0),
    DR => src_dr,
    SA => src_sa,
    SB => src_sb);

reg_PC : PC PORT MAP (
    PC_in => src_mpc_out,
    PL => src_pl,
    PI => src_pi,
    reset => reset_mpc,
    PC_out => PC_mpc);

reg_control_memory : control_memory PORT MAP (
    car_in => src_car_in,
    NA => src_na,
    MSout => src_ms,
    MC => src_mc,
    IL => src_il,
    PI => src_pi,
    PL => src_pl,
    TD => MC_TD_mpc,
    TA => MC_TA_mpc,
    TB => MC_TB_mpc,
    MB => src_control(8),
    FSout => src_control(7 downto 3),
    MD => src_control(2),
    RW => src_control(1),
    MM => src_control(0),
    MW => MC_in_mpc);

src_mpc_in(5 downto 3) <= src_dr;
src_mpc_in(2 downto 0) <= src_sb;

src_opcode(7) <= '0';
src_control(17 downto 15) <= src_dr;
src_control(14 downto 12) <= src_sa;
src_control(11 downto 9) <= src_sb;
control_mpc <= src_control;

```

```
end Behavioral;
```

1.3.1 CAR

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity CAR is
    Port ( car_in : in STD_LOGIC_VECTOR(7 downto 0);
          muxs_in : in STD_LOGIC;
          res : in STD_LOGIC;
          car_out : out STD_LOGIC_VECTOR(7 downto 0));
end CAR;
architecture Behavioral of CAR is
begin
    process(res, car_in)
        variable car_now : STD_LOGIC_VECTOR(7 downto 0);
        variable car_temp : integer;
        variable car_next : std_logic_vector(7 downto 0);
    begin
        if(res = '1') then
            car_now := x"C0";
        elsif(muxs_in = '1') then
            car_now := car_in;
        elsif(muxs_in = '0') then
            car_temp := conv_integer(car_now);
            car_temp := car_temp + conv_integer(1);
            car_next := conv_std_logic_vector(car_temp, 8);
            car_now := car_next;
        end if;
        car_out <= car_now after 20ns;
    end process;
end Behavioral;
```

1.3.2 MUX8 TO 1BIT

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity mux8_1bit is
    Port ( in_00 : in STD_LOGIC;
          in_11 : in STD_LOGIC;
          in_C2 : in STD_LOGIC;
          in_V3 : in STD_LOGIC;
          in_Z4 : in STD_LOGIC;
          in_N5 : in STD_LOGIC;
          in_C6 : in STD_LOGIC;
          in_Z7 : in STD_LOGIC;
          in_MS : in STD_LOGIC_VECTOR(2 downto 0);
          MUXS_out : out STD_LOGIC);
end mux8_1bit;

architecture Behavioral of mux8_1bit is
begin
    MUXS_out <= in_00 after 1ns when in_MS = "000" else
                in_11 after 1ns when in_MS = "001" else
                in_C2 after 1ns when in_MS = "010" else
                in_V3 after 1ns when in_MS = "011" else
                in_Z4 after 1ns when in_MS = "100" else
                in_N5 after 1ns when in_MS = "101" else
                in_C6 after 1ns when in_MS = "110" else
                in_Z7 after 1ns when in_MS = "111";
end Behavioral;
```


1.3.3 MUX2 TO 8BIT

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity mux2_8bit is
    Port ( in_0 : in STD_LOGIC_VECTOR(7 downto 0);
          in_1 : in STD_LOGIC_VECTOR(7 downto 0);
          in_MC : in STD_LOGIC;
          MUXC_out : out STD_LOGIC_VECTOR(7 downto 0));
end mux2_8bit;
architecture Behavioral of mux2_8bit is
begin
    MUXC_out <= in_0 after 1ns when in_MC = '0' else
                in_1 after 1ns when in_MC = '1' else
                x"00" after 20ns;
end Behavioral;
```

1.3.4 extend

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity extend is
    Port ( E_in : in STD_LOGIC_VECTOR(5 downto 0);
          E_out : out STD_LOGIC_VECTOR(15 downto 0));
end extend;

architecture Behavioral of extend is
    signal e_src : STD_LOGIC_VECTOR(15 downto 0);
begin
    e_src(5 downto 0) <= E_in;
    e_src(15 downto 6) <= "0000000000" when E_in(5) = '0' else "1111111111";
    E_out <= e_src;
end Behavioral;
```

1.3.5 IR

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity IR is
    Port ( IR_in : in STD_LOGIC_VECTOR(15 downto 0);
          IL : in STD_LOGIC;
          opcode : out STD_LOGIC_VECTOR(6 downto 0);
          DR : out STD_LOGIC_VECTOR(2 downto 0);
          SA : out STD_LOGIC_VECTOR(2 downto 0);
          SB : out STD_LOGIC_VECTOR(2 downto 0));
end IR;
architecture Behavioral of IR is
begin
    opcode <= IR_in(15 downto 9) after 1ns when IL = '1';
    DR <= IR_in(8 downto 6) after 1ns when IL = '1';
    SA <= IR_in(5 downto 3) after 1ns when IL = '1';
    SB <= IR_in(2 downto 0) after 1ns when IL = '1';
end Behavioral;
```

1.3.6 PC

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity PC is
    Port ( PC_in : in STD_LOGIC_VECTOR(15 downto 0);
          PL : in STD_LOGIC;
          PI : in STD_LOGIC;
          reset : in STD_LOGIC;
          PC_out : out STD_LOGIC_VECTOR(15 downto 0));
end PC;
architecture Behavioral of PC is
begin

    process(reset , PL , PI)
        variable PC_now : STD_LOGIC_VECTOR(15 downto 0);
        variable PC_this : integer;
        variable PC_next : STD_LOGIC_VECTOR(15 downto 0);
    begin
        if(reset = '1') then
            PC_now := x"0000";
        elsif(PL = '1') then
            PC_now := PC_now + PC_in;
        elsif(PI = '1') then
            PC_this := conv_integer(PC_now);
            PC_this := PC_this + conv_integer(1);
            PC_next := conv_std_logic_vector(PC_this, 16);
            PC_now := PC_next;
        end if;
        PC_out <= PC_now after 2ns;
    end process;
end Behavioral;
```

1.3.7 Control Memory

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity control_memory is
  Port ( car_in : in STD_LOGIC_VECTOR(7 downto 0);
        NA : out STD_LOGIC_VECTOR(7 downto 0);
        MSout : out STD_LOGIC_VECTOR(2 downto 0);
        MC : out STD_LOGIC;
        IL : out STD_LOGIC;
        PI : out STD_LOGIC;
        PL : out STD_LOGIC;
        TD : out STD_LOGIC;
        TA : out STD_LOGIC;
        TB : out STD_LOGIC;
        MB : out STD_LOGIC;
        FSout : out STD_LOGIC_VECTOR(4 downto 0);
        MD : out STD_LOGIC;
        RW : out STD_LOGIC;
        MM : out STD_LOGIC;
        MW : out STD_LOGIC);
end control_memory;
architecture Behavioral of control_memory is

  type src_memory is array(0 to 255) of STD_LOGIC_VECTOR(27 downto 0);

begin
  memory : process(car_in)
    variable memory : src_memory := (

      x"FOE1D50",
      x"FOE1D51",
      x"FOE1D52",
      x"FOE1D53",
      x"FOE1D54",
      x"FOE1D55",
      x"FOE1D56",
      x"FOE1D57",
      x"FOE1D58",
      x"FOE1D59",
      x"FOE1D5A",
      x"FOE1D5B",
      x"FOE1D5C",
      x"FOE1D5D",
      x"FOE1D5E",
      x"FOE1D5F",

      x"FOE1D50",
      x"FOE1D51",
      x"FOE1D52",
      x"FOE1D53",
      x"FOE1D54",
      x"FOE1D55",
```

```
x"F0E1D56",
x"F0E1D57",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
```

```
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
```

```
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
```

```
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
```

x"0000000",
x"0000000",
x"0000000",
x"0000000",

```
x"0000000",  
x"0000000",  
x"0000000",
```

```
    x"0000000",  
x"0000000",  
x"0000000",  
x"0000000",  
x"0000000",  
x"0000000",  
x"0000000",  
x"0000000",  
x"0000000",  
x"0000000",  
x"0000000",  
x"0000000",  
x"0000000",  
x"0000000",  
x"0000000",  
x"0000000",
```

```
x"0000000",  
x"0000000",  
x"0000000",  
x"0000000",  
x"0000000",  
x"0000000",  
x"0000000",  
x"0000000",  
x"0000000",  
x"0000000",  
x"0000000",  
x"0000000",  
x"0000000",  
x"0000000",  
x"0000000",  
x"0000000",  
x"0000000",
```

```
x"0000000",  
x"0000000",  
x"0000000",  
x"0000000",  
x"0000000",  
x"0000000",  
x"0000000",  
x"0000000",  
x"0000000",  
x"0000000",  
x"0000000",  
x"0000000",  
x"0000000",  
x"0000000",  
x"0000000",  
x"0000000",
```


x"0000000",
x"0000000",
x"0000000",
x"0000000",

```

x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",

x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",
x"0000000",

VARIABLE addr : integer;
variable control_out : STD_LOGIC_VECTOR(27 downto 0);
begin
    addr := conv_integer(car_in);
    control_out := memory(addr);
    NA <= control_out(27 downto 20);
    MSout <= control_out(19 downto 17);
    MC <= control_out(16);
    IL <= control_out(15);
    PI <= control_out(14);
    PL <= control_out(13);
    TD <= control_out(12);
    TA <= control_out(11);
    TB <= control_out(10);
    MB <= control_out(9);
    FSout <= control_out(8 downto 4);
    MD <= control_out(3);
    RW <= control_out(2);
    MM <= control_out(1);
    MW <= control_out(0);
end process;
end Behavioral;

```

1.3.8 zero fill

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity zero_fill is
    Port ( sb : in STD_LOGIC_VECTOR(2 downto 0);
          z_out : out STD_LOGIC_VECTOR(15 downto 0));
end zero_fill;

architecture Behavioral of zero_fill is
    signal src_z : STD_LOGIC_VECTOR(15 downto 0);
begin
    src_z(2 downto 0) <= sb;
    src_z(15 downto 3) <= "0000000000000";
    z_out <= src_z;
end Behavioral;
```

1.4 bit

1.5 DATA PATH

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity datapath is
Port ( data_in : in STD_LOGIC_VECTOR(15 downto 0);
      PC_in : in STD_LOGIC_VECTOR(15 downto 0);
      control_in : in STD_LOGIC_VECTOR(17 downto 0);
      D_Clk : in STD_LOGIC;
      TD : in STD_LOGIC;
      TA : in STD_LOGIC;
      TB : in STD_LOGIC;
      address_out : out STD_LOGIC_VECTOR(15 downto 0);
      data_out : out STD_LOGIC_VECTOR(15 downto 0);
      path_out : out STD_LOGIC_VECTOR(3 downto 0));
end datapath;

architecture Behavioral of datapath is

component mux3_16bit
  Port ( s : in STD_LOGIC;
        In0 : in STD_LOGIC_VECTOR(15 downto 0);
        In1 : in STD_LOGIC_VECTOR(15 downto 0);
        Z : out STD_LOGIC_VECTOR(15 downto 0));
end Component;

Component function_unit
Port ( F_A : in STD_LOGIC_VECTOR(15 downto 0);
      F_B : in STD_LOGIC_VECTOR(15 downto 0);
      F_select : in STD_LOGIC_VECTOR(4 downto 0);
      F_Vout : out STD_LOGIC;
      F_Cout : out STD_LOGIC;
      F_Nout : out STD_LOGIC;
      F_Zout : out STD_LOGIC;
      F_F : out STD_LOGIC_VECTOR(15 downto 0));
end Component;

Component register_file
  Port ( inA : in STD_LOGIC_VECTOR(3 downto 0);
        inB : in STD_LOGIC_VECTOR(3 downto 0);
        inD : in STD_LOGIC_VECTOR(3 downto 0);
        Clk : in STD_LOGIC;
        load_in : in STD_LOGIC;
        data : in STD_LOGIC_VECTOR(15 downto 0);
        outA : out STD_LOGIC_VECTOR(15 downto 0);
        outB : out STD_LOGIC_VECTOR(15 downto 0));
end Component ;

Component zero_fill
  Port ( sb : in STD_LOGIC_VECTOR(2 downto 0);
        z_out : out STD_LOGIC_VECTOR(15 downto 0));
end Component;
```

```

signal src_muxM, src_muxD, src_muxB, src_regA, src_regB, src_out, src_z , src_pc:
    STD_LOGIC_VECTOR(15 downto 0);
signal src_outA, src_outB, src_outD, src_path : STD_LOGIC_VECTOR(3 downto 0);

begin
Dreg_mux3_16bit : mux3_16bit PORT MAP ( s => control_in(2),
    In0 => src_out,
    In1 => data_in,
    Z => src_muxD);

Breg_mux3_16bit : mux3_16bit PORT MAP ( s => control_in(8),
    In0 => src_regB,
    In1 => src_z,
    Z => src_muxB);

src_pc <= PC_in;

Mreg_mux3_16bit : mux3_16bit PORT MAP ( s => control_in(0),
    In0 => src_regA,
    In1 => src_pc,
    Z => src_muxM);

src_outD <= TD & control_in(17 downto 15);
src_outA <= TA & control_in(14 downto 12);
src_outB <= TB & control_in(11 downto 9);

reg_function_unit : function_unit PORT MAP (
    F_A => src_regA,
    F_B => src_muxB,
    F_select => control_in(7 downto 3),
    F_Vout => src_path(3),
    F_Cout => src_path(2),
    F_Nout => src_path(1),
    F_Zout => src_path(0),
    F_F => src_out);


reg_register_file : register_file PORT MAP(
    inA => src_outA,
    inB => src_outB,
    inD => src_outD,
    Clk => D_Clk,
    load_in => control_in(1),
    data => src_muxD,
    outA => src_regA,
    outB => src_regB);

reg_zero_fill : zero_fill PORT MAP(
    sb => control_in(11 downto 9),
    z_out => src_z);

data_out <= src_muxB;
address_out <= src_regA;
path_out <= src_path;

end Behavioral;

```

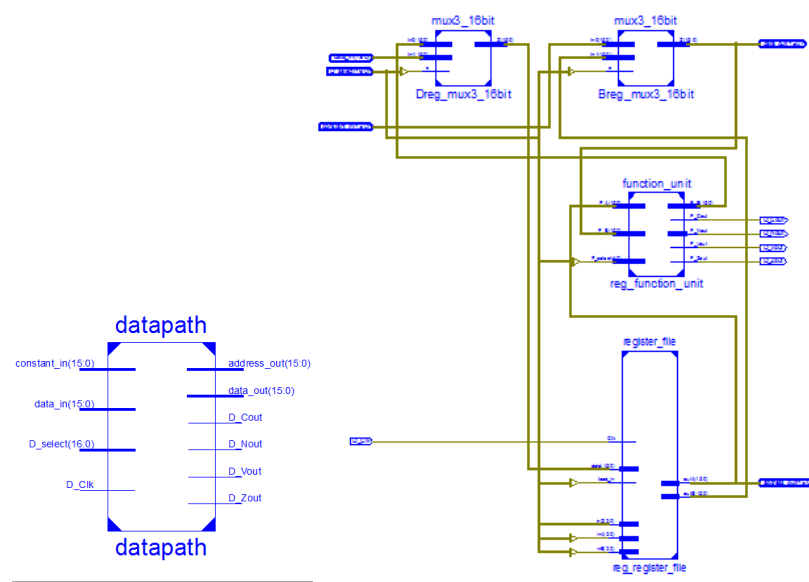

1.6 REGISTER FILE

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity register_file is
  Port (
    inA : in STD_LOGIC_VECTOR(3 downto 0);
    inB : in STD_LOGIC_VECTOR(3 downto 0);
    inD : in STD_LOGIC_VECTOR(3 downto 0);
    Clk : in STD_LOGIC;
    load_in : in STD_LOGIC;
    data : in STD_LOGIC_VECTOR(15 downto 0);
    outA : out STD_LOGIC_VECTOR(15 downto 0);
    outB : out STD_LOGIC_VECTOR(15 downto 0)
  );
end register_file;

architecture Behavioral of register_file is

  Component decoder_3to8
  Port ( A0 : in STD_LOGIC;
    A1 : in STD_LOGIC;
    A2 : in STD_LOGIC;
    A3 : in STD_LOGIC;
    Q0 : out STD_LOGIC;
    Q1 : out STD_LOGIC;
    Q2 : out STD_LOGIC;
    Q3 : out STD_LOGIC;
    Q4 : out STD_LOGIC;
    Q5 : out STD_LOGIC;
    Q6 : out STD_LOGIC;
    Q7 : out STD_LOGIC;
    Q8 : out STD_LOGIC);
  End Component;

  Component mux3_16bit
  Port ( s : in STD_LOGIC;
    In0 : in STD_LOGIC_VECTOR(15 downto 0);
    In1 : in STD_LOGIC_VECTOR(15 downto 0);
    Z : out STD_LOGIC_VECTOR(15 downto 0));
  End Component;

  Component reg8
  Port ( load0 : in STD_LOGIC;
    load1 : in STD_LOGIC;
    Clk : in STD_LOGIC;
    D : in STD_LOGIC_VECTOR(15 downto 0);
    Q : out STD_LOGIC_VECTOR(15 downto 0));
  End Component;
```



```

Component mux8_16bit
Port ( S0 : in STD_LOGIC;
      S1 : in STD_LOGIC;
      S2 : in STD_LOGIC;
      S3 : in STD_LOGIC;
      In0 : in STD_LOGIC_VECTOR(15 downto 0);
      In1 : in STD_LOGIC_VECTOR(15 downto 0);
      In2 : in STD_LOGIC_VECTOR(15 downto 0);
      In3 : in STD_LOGIC_VECTOR(15 downto 0);
      In4 : in STD_LOGIC_VECTOR(15 downto 0);
      In5 : in STD_LOGIC_VECTOR(15 downto 0);
      In6 : in STD_LOGIC_VECTOR(15 downto 0);
      In7 : in STD_LOGIC_VECTOR(15 downto 0);
      In8 : in STD_LOGIC_VECTOR(15 downto 0);
      Z : out STD_LOGIC_VECTOR(15 downto 0));
End Component;

signal load_reg0, load_reg1, load_reg2, load_reg3, load_reg4,
       load_reg5, load_reg6, load_reg7, load_reg8 : STD_LOGIC;
signal reg0_q, reg1_q, reg2_q, reg3_q, reg4_q, reg5_q, reg6_q,
       reg7_q, reg8_q, d_mux, src_reg, src_A, src_B : STD_LOGIC_VECTOR(15 downto 0);

begin
  reg_decoder_3to8 : decoder_3to8 PORT MAP(
    A0 => inD(0),
    A1 => inD(1),
    A2 => inD(2),
    A3 => inD(3),
    Q0 => load_reg0,
    Q1 => load_reg1,
    Q2 => load_reg2,
    Q3 => load_reg3,
    Q4 => load_reg4,
    Q5 => load_reg5,
    Q6 => load_reg6,
    Q7 => load_reg7,
    Q8 => load_reg8
  );

  A_reg_mux8_16bit : mux8_16bit PORT MAP(
    S0 => inA(0),
    S1 => inA(1),
    S2 => inA(2),
    S3 => inA(3),
    In0 => reg0_q,
    In1 => reg1_q,
    In2 => reg2_q,
    In3 => reg3_q,
    In4 => reg4_q,
    In5 => reg5_q,
    In6 => reg6_q,
    In7 => reg7_q,
    In8 => reg8_q,
    Z => src_A
  );

```

```

B_reg_mux8_16bit : mux8_16bit PORT MAP(
    S0 => inB(0),
    S1 => inB(1),
    S2 => inB(2),
    S3 => inB(3),
    In0 => reg0_q,
    In1 => reg1_q,
    In2 => reg2_q,
    In3 => reg3_q,
    In4 => reg4_q,
    In5 => reg5_q,
    In6 => reg6_q,
    In7 => reg7_q,
    In8 => reg8_q,
    Z => src_B
);

reg00 : reg8 PORT MAP(
    load0 => load_reg0,
    load1 => load_in,
    Clk => Clk,
    D => data,
    Q => reg0_q);

reg01 : reg8 PORT MAP(
    load0 => load_reg1,
    load1 => load_in,
    Clk => Clk,
    D => data,
    Q => reg1_q);

reg02 : reg8 PORT MAP(
    load0 => load_reg2,
    load1 => load_in,
    Clk => Clk,
    D => data,
    Q => reg2_q);

reg03 : reg8 PORT MAP(
    load0 => load_reg3,
    load1 => load_in,
    Clk => Clk,
    D => data,
    Q => reg3_q);

reg04 : reg8 PORT MAP(
    load0 => load_reg4,
    load1 => load_in,
    Clk => Clk,
    D => data,
    Q => reg4_q);

reg05 : reg8 PORT MAP(
    load0 => load_reg5,
    load1 => load_in,
    Clk => Clk,

```

```

    D => data,
    Q => reg5_q);

reg06 : reg8 PORT MAP(
    load0 => load_reg6,
    load1 => load_in,
    Clk => Clk,
    D => data,
    Q => reg6_q);


reg07 : reg8 PORT MAP(
    load0 => load_reg7,
    load1 => load_in,
    Clk => Clk,
    D => data,
    Q => reg7_q);

reg08 : reg8 PORT MAP(
    load0 => load_reg8,
    load1 => load_in,
    Clk => Clk,
    D => data,
    Q => reg8_q);

outA <= src_A;
outB <= src_B;

end Behavioral;

```

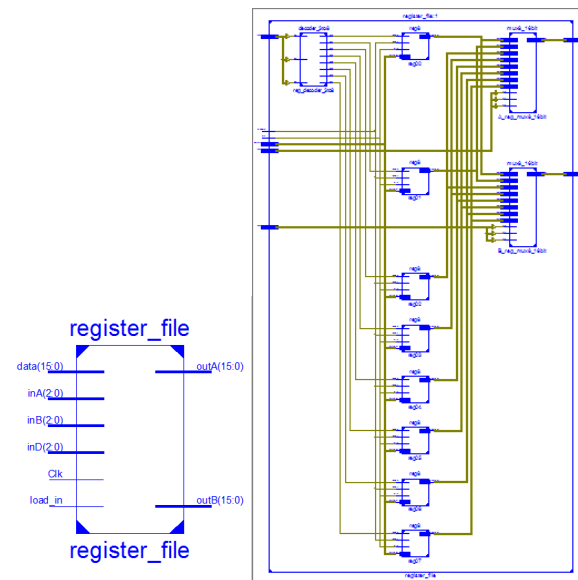


1.6.1 REG8

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity reg8 is
    Port ( load0 : in STD_LOGIC;
          load1 : in STD_LOGIC;
          Clk : in STD_LOGIC;
          D : in STD_LOGIC_VECTOR(15 downto 0);
          Q : out STD_LOGIC_VECTOR(15 downto 0));
end reg8;

architecture Behavioral of reg8 is

 begin
    process(Clk)
    begin
        if(rising_edge(Clk)) then
            if(load0 = '1') and (load1 = '1') then
                Q<= D after 5ns;
            end if;
        end if;
    end process;
end Behavioral;
```




1.6.2 DECODER

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity decoder_3to8 is
    Port ( A0 : in STD_LOGIC;
          A1 : in STD_LOGIC;
          A2 : in STD_LOGIC;
          A3 : in STD_LOGIC;
          Q0 : out STD_LOGIC;
          Q1 : out STD_LOGIC;
          Q2 : out STD_LOGIC;
          Q3 : out STD_LOGIC;
          Q4 : out STD_LOGIC;
          Q5 : out STD_LOGIC;
          Q6 : out STD_LOGIC;
          Q7 : out STD_LOGIC;
          Q8 : out STD_LOGIC);
end decoder_3to8;

architecture Behavioral of decoder_3to8 is
begin
    Q0 <= (( NOT A0) AND (NOT A1) AND (NOT A2) AND (NOT A3)) AFTER 5ns;
    Q1 <= (( NOT A0) AND (NOT A1) AND A2 AND (NOT A2)) AFTER 5ns;
    Q2 <= (( NOT A0) AND A1 AND (NOT A2) AND (NOT A2)) AFTER 5ns;
    Q3 <= (( NOT A0) AND A1 AND A2 AND (NOT A2)) AFTER 5ns;
    Q4 <= (A0 AND (NOT A1) AND (NOT A2) AND (NOT A2)) AFTER 5ns;
    Q5 <= (A0 AND (NOT A1) AND A2 AND (NOT A2)) AFTER 5ns;
    Q6 <= (A0 AND A1 AND (NOT A2) AND (NOT A2)) AFTER 5ns;
    Q7 <= (A0 AND A1 AND A2 AND (NOT A2)) AFTER 5ns;
    Q8 <= A3 AFTER 5ns;
end Behavioral;
```

 

1.6.3 MUX3 TO 16BIT


```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity mux3_16bit is
    Port ( s : in STD_LOGIC;
          In0 : in STD_LOGIC_VECTOR(15 downto 0);
          In1 : in STD_LOGIC_VECTOR(15 downto 0);
          Z : out STD_LOGIC_VECTOR(15 downto 0));
end mux3_16bit;

architecture Behavioral of mux3_16bit is

begin
    Z <= In0 after 5ns when s = '0' else
        In1 after 5ns when s = '1' else
        x"0000" after 5ns;

end Behavioral;
```

 


1.6.4 MUX8 TO 16BIT

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity mux8_16bit is
    Port ( S0 : in STD_LOGIC;
          S1 : in STD_LOGIC;
          S2 : in STD_LOGIC;
          In0 : in STD_LOGIC_VECTOR(15 downto 0);
          In1 : in STD_LOGIC_VECTOR(15 downto 0);
          In2 : in STD_LOGIC_VECTOR(15 downto 0);
          In3 : in STD_LOGIC_VECTOR(15 downto 0);
          In4 : in STD_LOGIC_VECTOR(15 downto 0);
          In5 : in STD_LOGIC_VECTOR(15 downto 0);
          In6 : in STD_LOGIC_VECTOR(15 downto 0);
          In7 : in STD_LOGIC_VECTOR(15 downto 0);
          Z : out STD_LOGIC_VECTOR(15 downto 0));
end mux8_16bit;

architecture Behavioral of mux8_16bit is

begin
    Z <= In0 after 5ns when S0 = '0' and S1 = '0' and S2 = '0' else
        In1 after 5ns when S0 = '0' and S1 = '0' and S2 = '1' else
        In2 after 5ns when S0 = '0' and S1 = '1' and S2 = '0' else
        In3 after 5ns when S0 = '0' and S1 = '1' and S2 = '1' else
        In4 after 5ns when S0 = '1' and S1 = '0' and S2 = '0' else
        In5 after 5ns when S0 = '1' and S1 = '0' and S2 = '1' else
        In6 after 5ns when S0 = '1' and S1 = '1' and S2 = '0' else
        In7 after 5ns when S0 = '1' and S1 = '1' and S2 = '1' else
        x"0000" after 5ns;
end Behavioral;
```

 1.7 FUNCTION UNIT

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity function_unit is
Port ( F_A : in STD_LOGIC_VECTOR(15 downto 0);
      F_B : in STD_LOGIC_VECTOR(15 downto 0);
      F_select : in STD_LOGIC_VECTOR(4 downto 0);
      F_Vout : out STD_LOGIC;
      F_Cout : out STD_LOGIC;
      F_Nout : out STD_LOGIC;
      F_Zout : out STD_LOGIC;
      F_F : out STD_LOGIC_VECTOR(15 downto 0));
end function_unit;

architecture Behavioral of function_unit is

Component arithmetic_logic_unit
  Port ( ALU_A : in STD_LOGIC_VECTOR(15 downto 0);
        ALU_B : in STD_LOGIC_VECTOR(15 downto 0);
        ALU_select : in STD_LOGIC_VECTOR(3 downto 0);
        ALU_Cout : out STD_LOGIC;
        ALU_Vout : out STD_LOGIC;
        ALU_G : out STD_LOGIC_VECTOR(15 downto 0));
end Component;

Component shifter Port ( B : in STD_LOGIC_VECTOR(15 downto 0);
  S : in STD_LOGIC_VECTOR(1 downto 0);
  IR : in STD_LOGIC;
  IL : in STD_LOGIC;
  H : out STD_LOGIC_VECTOR(15 downto 0));
end Component;

Component mux3_16bit Port ( s : in STD_LOGIC;
  In0 : in STD_LOGIC_VECTOR(15 downto 0);
  In1 : in STD_LOGIC_VECTOR(15 downto 0);
  Z : out STD_LOGIC_VECTOR(15 downto 0));
end Component;

signal src_ALU, src_shift, src_mux : STD_LOGIC_VECTOR(15 downto 0);

begin

reg_arithmetic_logic_unit : arithmetic_logic_unit
  Port MAP ( ALU_A => F_A,
            ALU_B => F_B,
            ALU_select => F_select(3 downto 0),
            ALU_Cout => F_Cout,
            ALU_Vout => F_Vout,
            ALU_G => src_ALU);

reg_shifter : shifter Port MAP ( B => F_B,
  S => F_select(3 downto 2),
```

```


IR => '0',
IL => '0',
H => src_shift);

reg_mux3_16bit : mux3_16bit Port MAP ( s => F_select(4),
    In0 => src_ALU,
    In1 => src_shift,
    Z => src_mux);

F_F <= src_mux;
F_Nout <= src_mux(15);
F_Zout <= ((src_mux(15)) or (src_mux(14)) or (src_mux(13)) or
    (src_mux(12)) or (src_mux(11)) or (src_mux(10)) or
    (src_mux(9)) or (src_mux(8)) or (src_mux(7)) or
    (src_mux(6)) or (src_mux(5)) or (src_mux(4)) or
    (src_mux(3)) or (src_mux(2)) or
    (src_mux(1)) or (src_mux(0)));

end Behavioral;

```

 

1.8 SHIFTER

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity shifter is
    Port ( B : in STD_LOGIC_VECTOR(15 downto 0);
          S : in STD_LOGIC_VECTOR(1 downto 0);
          IR : in STD_LOGIC;
          IL : in STD_LOGIC;
          H : out STD_LOGIC_VECTOR(15 downto 0));
end shifter;

architecture Behavioral of shifter is

    component mux3_1bit Port ( In0 : in STD_LOGIC;
                              In1 : in STD_LOGIC;
                              In2 : in STD_LOGIC;
                              S0 : in STD_LOGIC;
                              S1 : in STD_LOGIC;
                              Z : out STD_LOGIC);
    end component;

begin

    mux3_1bit00 : mux3_1bit PORT MAP ( In0 =>B(0) ,
                                       In1 => B(1),
                                       In2 => IL,
                                       S0 => S(0),
                                       S1 => S(1),
                                       Z  => H(0));

    mux3_1bit01 : mux3_1bit PORT MAP ( In0 =>B(1) ,
                                       In1 => B(2),
                                       In2 => B(0),
                                       S0 => S(0),
                                       S1 => S(1),
                                       Z  => H(1));

    mux3_1bit02 : mux3_1bit PORT MAP ( In0 =>B(2) ,
                                       In1 => B(3),
                                       In2 => B(1),
                                       S0 => S(0),
                                       S1 => S(1),
                                       Z  => H(2));

    mux3_1bit03 : mux3_1bit PORT MAP ( In0 =>B(3) ,
                                       In1 => B(4),
                                       In2 => B(2),
                                       S0 => S(0),
                                       S1 => S(1),
                                       Z  => H(3));
```

```

mux3_1bit04 : mux3_1bit PORT MAP ( In0 =>B(4) ,
    In1 => B(5),
    In2 => B(3),
    S0 => S(0),
    S1 => S(1),
    Z  => H(4));

mux3_1bit05 : mux3_1bit PORT MAP ( In0 =>B(5) ,
    In1 => B(6),
    In2 => B(4),
    S0 => S(0),
    S1 => S(1),
    Z  => H(5));

mux3_1bit06 : mux3_1bit PORT MAP ( In0 =>B(6) ,
    In1 => B(7),
    In2 => B(5),
    S0 => S(0),
    S1 => S(1),
    Z  => H(6));

mux3_1bit07 : mux3_1bit PORT MAP ( In0 =>B(7) ,
    In1 => B(8),
    In2 => B(6),
    S0 => S(0),
    S1 => S(1),
    Z  => H(7));

mux3_1bit08 : mux3_1bit PORT MAP ( In0 =>B(8) ,
    In1 => B(9),
    In2 => B(7),
    S0 => S(0),
    S1 => S(1),
    Z  => H(8));

mux3_1bit09 : mux3_1bit PORT MAP ( In0 =>B(9) ,
    In1 => B(10),
    In2 => B(8),
    S0 => S(0),
    S1 => S(1),
    Z  => H(9));

mux3_1bit10 : mux3_1bit PORT MAP ( In0 =>B(10) ,
    In1 => B(11),
    In2 => B(9),
    S0 => S(0),
    S1 => S(1),
    Z  => H(10));

mux3_1bit11 : mux3_1bit PORT MAP ( In0 =>B(11) ,
    In1 => B(12),
    In2 => B(10),
    S0 => S(0),
    S1 => S(1),
    Z  => H(11));

```

```


mux3_1bit12 : mux3_1bit PORT MAP ( In0 =>B(12) ,
    In1 => B(13),
    In2 => B(11),
    S0 => S(0),
    S1 => S(1),
    Z  => H(12));

mux3_1bit13 : mux3_1bit PORT MAP ( In0 =>B(13) ,
    In1 => B(14),
    In2 => B(12),
    S0 => S(0),
    S1 => S(1),
    Z  => H(13));

mux3_1bit14 : mux3_1bit PORT MAP ( In0 =>B(14) ,
    In1 => B(15),
    In2 => B(13),
    S0 => S(0),
    S1 => S(1),
    Z  => H(14));

mux3_1bit15 : mux3_1bit PORT MAP ( In0 =>B(15) ,
    In1 => IR,
    In2 => B(14),
    S0 => S(0),
    S1 => S(1),
    Z  => H(15));
end Behavioral;

```

 

1.8.1 MUX3 TO 1BIT

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity mux3_1bit is
    Port ( In0 : in STD_LOGIC;
          In1 : in STD_LOGIC;
          In2 : in STD_LOGIC;
          S0 : in STD_LOGIC;
          S1 : in STD_LOGIC;
          Z : out STD_LOGIC);
end mux3_1bit;

architecture Behavioral of mux3_1bit is

begin
    Z <= In0 after 1ns when S0 = '0' and S1='0' else
        In1 after 1ns when S0 ='0' and S1= '1' else
        In2 after 1ns when S0 ='0' and S1 = '0' else
        '0' after 1ns;

end Behavioral;
```

1.9 ALU

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity arithmetic_logic_unit is
    Port ( ALU_A : in STD_LOGIC_VECTOR(15 downto 0);
          ALU_B : in STD_LOGIC_VECTOR(15 downto 0);
          ALU_select : in STD_LOGIC_VECTOR(3 downto 0);
          ALU_Cout : out STD_LOGIC;
          ALU_Vout : out STD_LOGIC;
          ALU_G : out STD_LOGIC_VECTOR(15 downto 0));
end arithmetic_logic_unit;

architecture Behavioral of arithmetic_logic_unit is

    component ripple_adder Port ( A : in STD_LOGIC_VECTOR(15 downto 0);
                                B : in STD_LOGIC_VECTOR(15 downto 0);
                                Cin : in STD_LOGIC;
                                Cout : out STD_LOGIC;
                                Gout : out STD_LOGIC_VECTOR(15 downto 0);
                                Vout : out STD_LOGIC);
    End Component;

    component mux3_16bit Port ( s : in STD_LOGIC;
                               In0 : in STD_LOGIC_VECTOR(15 downto 0);
                               In1 : in STD_LOGIC_VECTOR(15 downto 0);
                               Z : out STD_LOGIC_VECTOR(15 downto 0));
    End Component;

    component B_input_logic Port ( B : in STD_LOGIC_VECTOR(15 downto 0);
                                  S : in STD_LOGIC_VECTOR(1 downto 0);
                                  Y : out STD_LOGIC_VECTOR(15 downto 0));
    End Component;

    Component logic_circuit Port ( A : in STD_LOGIC_VECTOR(15 downto 0);
                                   B : in STD_LOGIC_VECTOR(15 downto 0);
                                   Cin : in STD_LOGIC_VECTOR(1 downto 0);
                                   Cout : out STD_LOGIC_VECTOR(15 downto 0));
    End Component;

    signal src_logic , src_B_input_logic, src_ripple : STD_LOGIC_VECTOR(15 downto 0);

begin

    reg_ripple_adder : ripple_adder PORT MAP ( A => ALU_A,
        B => src_logic,
        Cin => ALU_select(0),
        Cout => ALU_Cout,
        Gout => src_ripple,
        Vout => ALU_Vout);
```



```

reg_mux3_16bit :mux3_16bit PORT MAP ( s => ALU_select(3),
    In0 => src_ripple,
    In1 => src_B_input_logic,
    Z =>ALU_G);

```

```

reg_B_input_logic : B_input_logic PORT MAP ( B => ALU_B,
    S => ALU_SELECT(2 downto 1),
    Y => src_logic);

```

```


reg_logic_circuit : logic_circuit PORT MAP( A => ALU_A ,
    B => ALU_B,
    Cin => ALU_select(2 downto 1),
    Cout => src_B_input_logic);

```

```

end Behavioral;

```

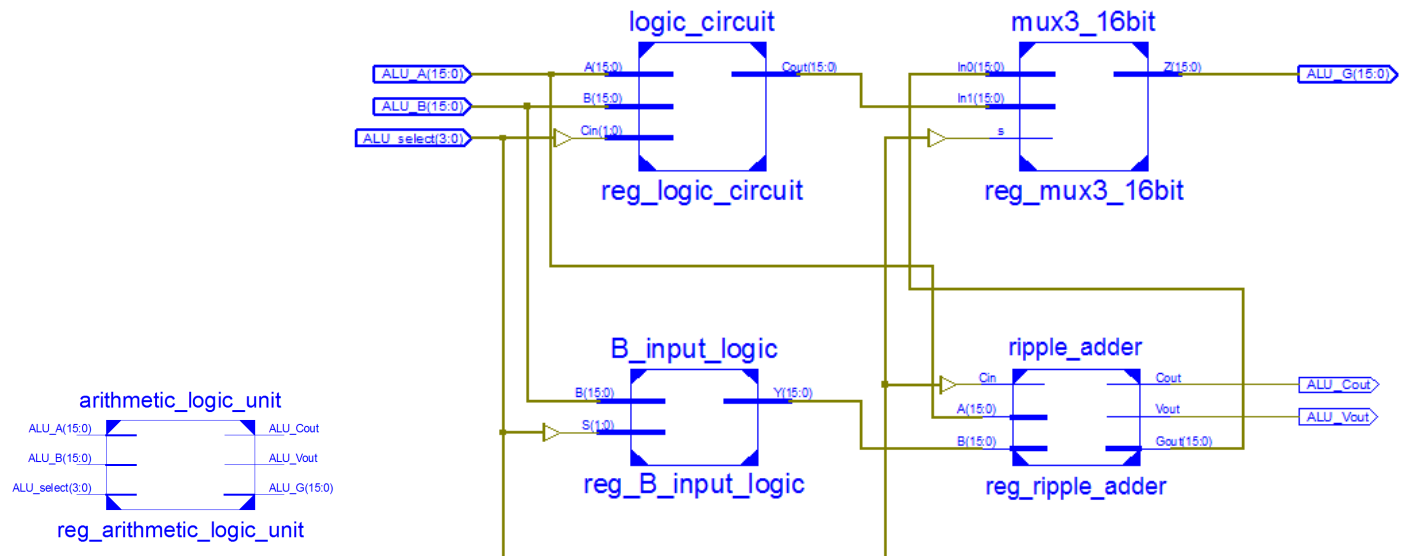


LOGIC

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity logic_circuit is
    Port ( A : in STD_LOGIC_VECTOR(15 downto 0);
          B : in STD_LOGIC_VECTOR(15 downto 0);
          Cin : in STD_LOGIC_VECTOR(1 downto 0);
          Cout : out STD_LOGIC_VECTOR(15 downto 0));
end logic_circuit;

architecture Behavioral of logic_circuit is

 begin
    Cout <= (A and B) after 1ns when Cin = "00" else
            (A or B) after 1ns when Cin = "01" else
            (A xor B) after 1ns when Cin = "10" else
            (not (A)) after 1ns;
end Behavioral;
```



1.9.1 B LOGIC

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity B_input_logic is
    Port ( B : in STD_LOGIC_VECTOR(15 downto 0);
          S : in STD_LOGIC_VECTOR(1 downto 0);
          Y : out STD_LOGIC_VECTOR(15 downto 0));
end B_input_logic;

architecture Behavioral of B_input_logic is

    component mux2_1bit Port ( S0 : in STD_LOGIC;
                              S1 : in STD_LOGIC;
                              Cin : in STD_LOGIC;
                              Res : out STD_LOGIC);

    End Component;

begin
    mux2_1bit00 : mux2_1bit PORT MAP( S0 => S(0),
                                       S1 => S(1),
                                       Cin => B(0),
                                       Res => Y(0));

    mux2_1bit01 : mux2_1bit PORT MAP( S0 => S(0),
                                       S1 => S(1),
                                       Cin => B(1),
                                       Res => Y(1));

    mux2_1bit02 : mux2_1bit PORT MAP( S0 => S(0),
                                       S1 => S(1),
                                       Cin => B(2),
                                       Res => Y(2));

    mux2_1bit03 : mux2_1bit PORT MAP( S0 => S(0),
                                       S1 => S(1),
                                       Cin => B(3),
                                       Res => Y(3));

    mux2_1bit04 : mux2_1bit PORT MAP( S0 => S(0),
                                       S1 => S(1),
                                       Cin => B(4),
                                       Res => Y(4));

    mux2_1bit05 : mux2_1bit PORT MAP( S0 => S(0),
                                       S1 => S(1),
                                       Cin => B(5),
                                       Res => Y(5));

    mux2_1bit06 : mux2_1bit PORT MAP( S0 => S(0),
                                       S1 => S(1),
                                       Cin => B(6),
                                       Res => Y(6));
```

```

mux2_1bit07 : mux2_1bit PORT MAP( S0 => S(0),
                                   S1 => S(1),
                                   Cin =>B(7),
                                   Res => Y(7));

mux2_1bit08 : mux2_1bit PORT MAP( S0 => S(0),
                                   S1 => S(1),
                                   Cin =>B(8),
                                   Res => Y(8));

mux2_1bit09 : mux2_1bit PORT MAP( S0 => S(0),
                                   S1 => S(1),
                                   Cin =>B(9),
                                   Res => Y(9));

mux2_1bit10 : mux2_1bit PORT MAP( S0 => S(0),
                                   S1 => S(1),
                                   Cin =>B(10),
                                   Res => Y(10));

mux2_1bit11 : mux2_1bit PORT MAP( S0 => S(0),
                                   S1 => S(1),
                                   Cin =>B(11),
                                   Res => Y(11));

mux2_1bit12 : mux2_1bit PORT MAP( S0 => S(0),
                                   S1 => S(1),
                                   Cin =>B(12),
                                   Res => Y(12));


mux2_1bit13 : mux2_1bit PORT MAP( S0 => S(0),
                                   S1 => S(1),
                                   Cin =>B(13),
                                   Res => Y(13));

mux2_1bit14 : mux2_1bit PORT MAP( S0 => S(0),
                                   S1 => S(1),
                                   Cin =>B(14),
                                   Res => Y(14));

mux2_1bit15 : mux2_1bit PORT MAP( S0 => S(0),
                                   S1 => S(1),
                                   Cin =>B(15),
                                   Res => Y(15));

end Behavioral;

```

 

1.9.2 MUX2 TO 1BIT


```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity mux2_1bit is
    Port ( S0 : in STD_LOGIC;
          S1 : in STD_LOGIC;
          Cin : in STD_LOGIC;
          Res : out STD_LOGIC);
end mux2_1bit;

architecture Behavioral of mux2_1bit is

begin
    Res <= S0 after 1ns when Cin = '1' else
           S1 after 1ns when Cin = '1' else
           '0' after 1ns;

end Behavioral;
```

 

1.9.3 RIPPLE

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity ripple_adder is
    Port ( A : in STD_LOGIC_VECTOR(15 downto 0);
          B : in STD_LOGIC_VECTOR(15 downto 0);
          Cin : in STD_LOGIC;
          Cout : out STD_LOGIC;
          Gout : out STD_LOGIC_VECTOR(15 downto 0);
          Vout : out STD_LOGIC);
end ripple_adder;

architecture Behavioral of ripple_adder is

    Component full_adder
    PORT(X: in STD_LOGIC;
         Y: in STD_LOGIC;
         S: out STD_LOGIC;
         Cin: in STD_LOGIC;
         Cout: out STD_LOGIC);
    End Component;

    signal src_sig0, src_sig1, src_sig2, src_sig3, src_sig4,
           src_sig5, src_sig6, src_sig7, src_sig8, src_sig9, src_sig10,
           src_sig11, src_sig12, src_sig13, src_sig14, src_sig15,
           src_out: STD_LOGIC;
    begin
        full_adder00 : full_adder PORT MAP(X => A(0),
                                           Y => B(0),
                                           S => Gout(0),
                                           Cin => Cin,
                                           Cout =>src_sig0 );

        full_adder01 : full_adder PORT MAP(X => A(1),
                                           Y => B(1),
                                           S => Gout(1),
                                           Cin => Cin,
                                           Cout =>src_sig1);

        full_adder02 : full_adder PORT MAP(X => A(2),
                                           Y => B(2),
                                           S => Gout(2),
                                           Cin => Cin,
                                           Cout =>src_sig2);

        full_adder03 : full_adder PORT MAP(X => A(3),
                                           Y => B(3),
                                           S => Gout(3),
                                           Cin => Cin,
                                           Cout =>src_sig3);
```

```

full_adder04 : full_adder PORT MAP(X => A(4),
                                   Y => B(4),
                                   S => Gout(4),
                                   Cin => Cin,
                                   Cout =>src_sig4);

full_adder05 : full_adder PORT MAP(X => A(5),
                                   Y => B(5),
                                   S => Gout(5),
                                   Cin => Cin,
                                   Cout =>src_sig5);

full_adder06 : full_adder PORT MAP(X => A(6),
                                   Y => B(6),
                                   S => Gout(6),
                                   Cin => Cin,
                                   Cout =>src_sig6);

full_adder07 : full_adder PORT MAP(X => A(7),
                                   Y => B(7),
                                   S => Gout(7),
                                   Cin => Cin,
                                   Cout =>src_sig7);

full_adder08 : full_adder PORT MAP(X => A(8),
                                   Y => B(8),
                                   S => Gout(8),
                                   Cin => Cin,
                                   Cout =>src_sig8);

full_adder09 : full_adder PORT MAP(X => A(9),
                                   Y => B(9),
                                   S => Gout(9),
                                   Cin => Cin,
                                   Cout =>src_sig9);

full_adder10 : full_adder PORT MAP(X => A(10),
                                   Y => B(10),
                                   S => Gout(10),
                                   Cin => Cin,
                                   Cout =>src_sig10);

full_adder11 : full_adder PORT MAP(X => A(11),
                                   Y => B(11),
                                   S => Gout(11),
                                   Cin => Cin,
                                   Cout =>src_sig11);

full_adder12 : full_adder PORT MAP(X => A(12),
                                   Y => B(12),
                                   S => Gout(12),
                                   Cin => Cin,
                                   Cout =>src_sig12);

full_adder13 : full_adder PORT MAP(X => A(13),
                                   Y => B(13),

```



```


        S => Gout(13),
        Cin => Cin,
        Cout =>src_sig13);

full_adder14 : full_adder PORT MAP(X => A(14),
        Y => B(14),
        S => Gout(14),
        Cin => Cin,
        Cout =>src_sig14);

full_adder15 : full_adder PORT MAP(X => A(15),
        Y => B(15),
        S => Gout(15),
        Cin => Cin,
        Cout =>src_sig15);

end Behavioral;

```

 

1.9.4 FULL ADDER


```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity full_adder is
PORT(X: in STD_LOGIC;
     Y: in STD_LOGIC;
     S: out STD_LOGIC;
     Cin: in STD_LOGIC;
     Cout: out STD_LOGIC);
end full_adder;

architecture Behavioral of full_adder is

    signal S1, S2, S3: STD_LOGIC;
begin
    S1 <= (X xor Y) after 1ns;
    S2 <= (Cin and S1) after 1ns;
    S3 <= (X and Y) after 1ns;
    S <= (S1 xor Cin) after 1ns;
    Cout <= (S2 or S3) after 1ns;

end Behavioral;
```

 

2 TESTBENCHES

2.1 Microcoded Instruction Set Processor

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY test_misp IS
END test_misp;
ARCHITECTURE behavior OF test_misp IS

    COMPONENT microcoded_instruction_set_processor
    PORT(
        misp_clk : IN std_logic;
        misp_reset : IN std_logic
    );
    END COMPONENT;


    --Inputs
    signal misp_clk : std_logic := '0';
    signal misp_reset : std_logic := '0';

    -- Clock period definitions
    constant misp_clk_period : time := 10 ns;

BEGIN
    -- Instantiate the Unit Under Test (UUT)
    uut: microcoded_instruction_set_processor PORT MAP (
        misp_clk => misp_clk,
        misp_reset => misp_reset
    );

    -- Clock process definitions
    misp_clk_process : process
    begin
        misp_clk <= '0';
        wait for misp_clk_period/2;
        misp_clk <= '1';
        wait for misp_clk_period/2;
    end process;

     -- Stimulus process
    stim_proc: process
    begin
        misp_reset <= '1';
        wait for 20 ns;
        misp_reset <= '0';
        wait;
    end process;
END;
```



2.2 Memory M

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY test_memory_m IS
END test_memory_m;

ARCHITECTURE behavior OF test_memory_m IS

    COMPONENT memory_m
    PORT(
        data_in : IN std_logic_vector(15 downto 0);
        mw : IN std_logic;
        address_in : IN std_logic_vector(15 downto 0);
        data_out : OUT std_logic_vector(15 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal data_in : std_logic_vector(15 downto 0) := (others => '0');
    signal mw : std_logic := '0';
    signal address_in : std_logic_vector(15 downto 0) := (others => '0');

    --Outputs
    signal data_out : std_logic_vector(15 downto 0);

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: memory_m PORT MAP (
        data_in => data_in,
        mw => mw,
        address_in => address_in,
        data_out => data_out);

    -- Stimulus process
    stim_proc: process
    begin
        wait for 10 ns;
        address_in <= x"0000";

        wait for 10 ns;
        address_in <= x"0001";

        wait for 10 ns;
        address_in <= x"0009";

        wait for 10 ns;
        address_in <= x"000A";

        wait for 10 ns;
        address_in <= x"0000";

        wait for 10 ns;
    end process;
END;
```

```


data_in <= x"00B0";

wait for 10 ns;
data_in <= x"0000";

wait;
end process;

END;

```

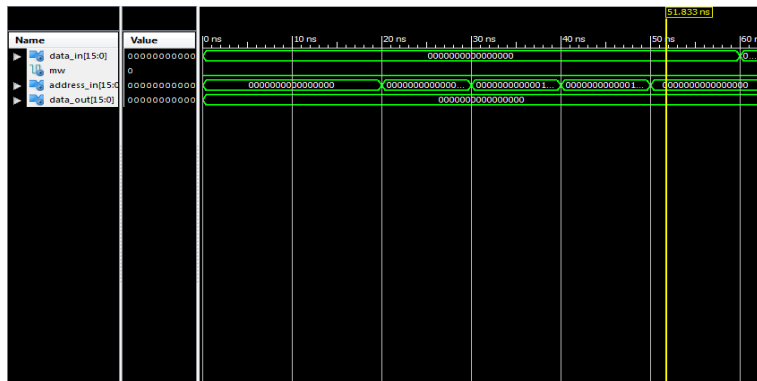

2.3 Micro Programmed Control

2.3.1 CAR

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY test_CAR IS
END test_CAR;

ARCHITECTURE behavior OF test_CAR IS

    COMPONENT CAR
    PORT(
        car_in : IN std_logic_vector(7 downto 0);
        muxs_in : IN std_logic;
        res : IN std_logic;
        car_out : OUT std_logic_vector(7 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal car_in : std_logic_vector(7 downto 0) := (others => '0');
    signal muxs_in : std_logic := '0';
    signal res : std_logic := '0';

    --Outputs
    signal car_out : std_logic_vector(7 downto 0);

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: CAR PORT MAP (
        car_in => car_in,
        muxs_in => muxs_in,
        res => res,
        car_out => car_out
    );

    -- Stimulus process
    stim_proc: process
    begin

        wait for 10ns;
        res <='0';


        wait for 10ns;
        res <='1';

        wait for 10ns;
        muxs_in <='0';

        wait for 10ns;
        muxs_in <='1';

        wait;
    end process;
```


END;

 

2.3.2 MUX8 TO 1BIT

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY test_mux8_1bit IS
END test_mux8_1bit;
ARCHITECTURE behavior OF test_mux8_1bit IS
    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT mux8_1bit
    PORT(
        in_00 : IN std_logic;
        in_11 : IN std_logic;
        in_C2 : IN std_logic;
        in_V3 : IN std_logic;
        in_Z4 : IN std_logic;
        in_N5 : IN std_logic;
        in_C6 : IN std_logic;
        in_Z7 : IN std_logic;
        in_MS : IN std_logic_vector(2 downto 0);
        MUXS_out : OUT std_logic
    );
    END COMPONENT;

    --Inputs
    signal in_00 : std_logic := '0';
    signal in_11 : std_logic := '0';
    signal in_C2 : std_logic := '0';
    signal in_V3 : std_logic := '0';
    signal in_Z4 : std_logic := '0';
    signal in_N5 : std_logic := '0';
    signal in_C6 : std_logic := '0';
    signal in_Z7 : std_logic := '0';
    signal in_MS : std_logic_vector(2 downto 0) := (others => '0');

    --Outputs
    signal MUXS_out : std_logic;
BEGIN
    -- Instantiate the Unit Under Test (UUT)
    uut: mux8_1bit PORT MAP (
        in_00 => in_00,
        in_11 => in_11,
        in_C2 => in_C2,
        in_V3 => in_V3,
        in_Z4 => in_Z4,
        in_N5 => in_N5,
        in_C6 => in_C6,
        in_Z7 => in_Z7,
        in_MS => in_MS,
        MUXS_out => MUXS_out
    );

    -- Stimulus process
    stim_proc: process
    begin
        in_11 <= '1';
    end process;
end behavior;
```

```

in_C2 <= '1';
in_V3 <= '1';
in_Z7 <= '1';

wait for 10 ns;
in_MS <= "000";

wait for 10 ns;
in_MS <= "001";

wait for 10 ns;
in_MS <= "010";

wait for 10 ns;
in_MS <= "011";


wait for 10 ns;
in_MS <= "100";

wait for 10 ns;
in_MS <= "001";

wait for 10 ns;
in_MS <= "010";

wait for 10 ns;
in_MS <= "111";
wait;
end process;
END;

```

 

2.3.3 MUX2 TO 8BIT

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY test_mux2_8bit IS
END test_mux2_8bit;

ARCHITECTURE behavior OF test_mux2_8bit IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT mux2_8bit
    PORT(
        in_0 : IN std_logic_vector(7 downto 0);
        in_1 : IN std_logic_vector(7 downto 0);
        in_MC : IN std_logic;
        MUXC_out : OUT std_logic_vector(7 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal in_0 : std_logic_vector(7 downto 0) := (others => '0');
    signal in_1 : std_logic_vector(7 downto 0) := (others => '0');
    signal in_MC : std_logic := '0';

    --Outputs
    signal MUXC_out : std_logic_vector(7 downto 0);

BEGIN


    -- Instantiate the Unit Under Test (UUT)
    uut: mux2_8bit PORT MAP (
        in_0 => in_0,
        in_1 => in_1,
        in_MC => in_MC,
        MUXC_out => MUXC_out
    );

    -- Stimulus process
    stim_proc: process
    begin
        in_0 <= x"FF";
        in_1 <= x"AA";

        wait for 10ns;
        in_MC <= '1';

        wait;
    end process;

END;
```

 

2.3.4 extend

```


LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY test_extend IS
END test_extend;
ARCHITECTURE behavior OF test_extend IS
    -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT extend
    PORT(
        E_in : IN std_logic_vector(5 downto 0);
        E_out : OUT std_logic_vector(15 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal E_in : std_logic_vector(5 downto 0) := (others => '0');

    --Outputs
    signal E_out : std_logic_vector(15 downto 0);
BEGIN
    -- Instantiate the Unit Under Test (UUT)
    uut: extend PORT MAP (
        E_in => E_in,
        E_out => E_out);

    -- Stimulus process
    stim_proc: process
    begin
        wait for 10 ns;
        E_in <="010101";
        wait for 10 ns;
        E_in <="101010";
        wait;
    end process;
END;

```

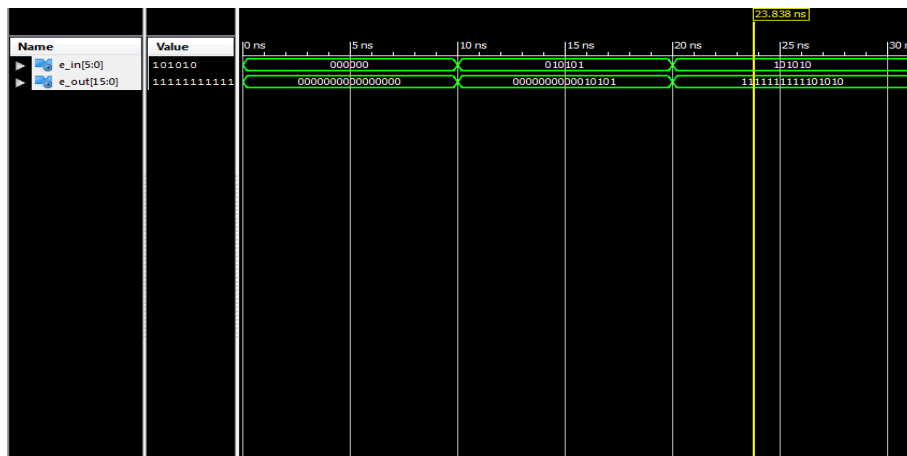

2.3.5 IR

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY test_IR IS
END test_IR;

ARCHITECTURE behavior OF test_IR IS

    COMPONENT IR
    PORT(
        IR_in : IN std_logic_vector(15 downto 0);
        IL : IN std_logic;
        opcode : OUT std_logic_vector(6 downto 0);
        DR : OUT std_logic_vector(2 downto 0);
        SA : OUT std_logic_vector(2 downto 0);
        SB : OUT std_logic_vector(2 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal IR_in : std_logic_vector(15 downto 0) := (others => '0');
    signal IL : std_logic := '0';

    --Outputs
    signal opcode : std_logic_vector(6 downto 0);
    signal DR : std_logic_vector(2 downto 0);
    signal SA : std_logic_vector(2 downto 0);
    signal SB : std_logic_vector(2 downto 0);

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: IR PORT MAP (
        IR_in => IR_in,
        IL => IL,
        opcode => opcode,
        DR => DR,
        SA => SA,
        SB => SB );

    -- Stimulus process
    stim_proc: process
    begin
        wait for 10ns;
        IR_in <= "1111000011110101";

        wait for 5ns;
        IL <= '1';

        wait for 10ns;
        IR_in <= "0000000011110101";
        IL <= '0';


        wait for 5ns;
```

```

        IL <= '1';
        wait;
    end process;

END;

```

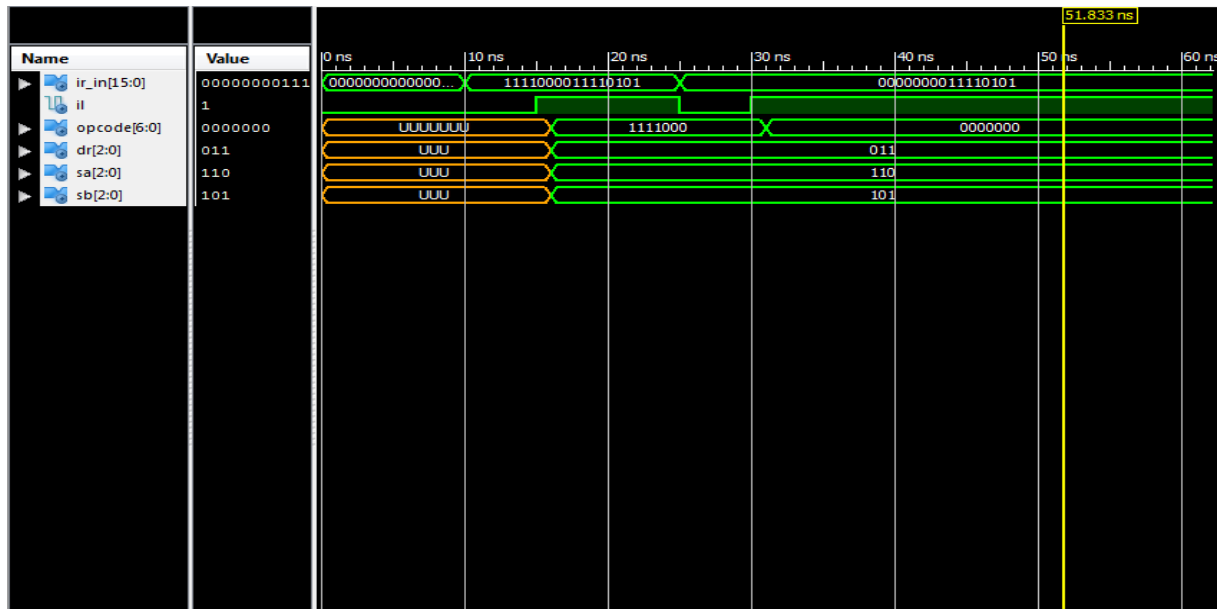

2.3.6 PC

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY test_PC IS
END test_PC;

ARCHITECTURE behavior OF test_PC IS

    COMPONENT PC
    PORT(
        PC_in : IN std_logic_vector(15 downto 0);
        PL : IN std_logic;
        PI : IN std_logic;
        reset : IN std_logic;
        PC_out : OUT std_logic_vector(15 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal PC_in : std_logic_vector(15 downto 0) := (others => '0');
    signal PL : std_logic := '0';
    signal PI : std_logic := '0';
    signal reset : std_logic := '0';

    --Outputs
    signal PC_out : std_logic_vector(15 downto 0);

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: PC PORT MAP (
        PC_in => PC_in,
        PL => PL,
        PI => PI,
        reset => reset,
        PC_out => PC_out
    );

    -- Stimulus process
    stim_proc: process
    begin
        wait for 10ns;
        reset <= '1';
        PC_in <= x"0000";

        wait for 10ns;
        reset <= '0';

        wait for 10ns;
        PI <= '1';
        PC_in <= x"000A";

        wait for 10ns;
```

```

reset <= '0';

wait for 10ns;
PI <= '0';
PL <= '1';
PC_in <= x"FFFF";

    wait;
end process;

END;

```



2.3.7 Control Memory

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY test_control_memory IS
END test_control_memory;
ARCHITECTURE behavior OF test_control_memory IS
    -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT control_memory
    PORT(
        car_in : IN std_logic_vector(7 downto 0);
        NA : OUT std_logic_vector(7 downto 0);
        MSout : OUT std_logic_vector(2 downto 0);
        MC : OUT std_logic;
        IL : OUT std_logic;
        PI : OUT std_logic;
        PL : OUT std_logic;
        TD : OUT std_logic;
        TA : OUT std_logic;
        TB : OUT std_logic;
        MB : OUT std_logic;
        FSout : OUT std_logic_vector(4 downto 0);
        MD : OUT std_logic;
        RW : OUT std_logic;
        MM : OUT std_logic;
        MW : OUT std_logic
    );
    END COMPONENT;
    --Inputs
    signal car_in : std_logic_vector(7 downto 0) := (others => '0');
    --Outputs
    signal NA : std_logic_vector(7 downto 0);
    signal MSout : std_logic_vector(2 downto 0);
    signal MC : std_logic;
    signal IL : std_logic;
    signal PI : std_logic;
    signal PL : std_logic;
    signal TD : std_logic;
    signal TA : std_logic;
    signal TB : std_logic;
    signal MB : std_logic;
    signal FSout : std_logic_vector(4 downto 0);
    signal MD : std_logic;
    signal RW : std_logic;
    signal MM : std_logic;
    signal MW : std_logic;
BEGIN
    -- Instantiate the Unit Under Test (UUT)
    uut: control_memory PORT MAP (
        car_in => car_in,
        NA => NA,
        MSout => MSout,
        MC => MC,
        IL => IL,
        PI => PI,
        PL => PL,
```

```

        TD => TD,
        TA => TA,
        TB => TB,
        MB => MB,
        FSout => FSout,
        MD => MD,
        RW => RW,
        MM => MM,
        MW => MW
    );
-- Stimulus process
stim_proc: process
begin
    wait for 10ns;
    car_in <=x"00";

    wait for 10ns;
    car_in <=x"0A";

    wait for 10ns;
    car_in <=x"FO";
    wait;
end process;
END;

```




2.3.8 zero fill

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY test_zero_fill IS
END test_zero_fill;
ARCHITECTURE behavior OF test_zero_fill IS
    COMPONENT zero_fill
    PORT(
        sb : IN std_logic_vector(2 downto 0);
        z_out : OUT std_logic_vector(15 downto 0)
    );
    END COMPONENT;
--Inputs
signal sb : std_logic_vector(2 downto 0) := (others => '0');
--Outputs
signal z_out : std_logic_vector(15 downto 0);
BEGIN
    -- Instantiate the Unit Under Test (UUT)
    uut: zero_fill PORT MAP (
        sb => sb,
        z_out => z_out
    );
    -- Stimulus process
    stim_proc: process
    begin
        wait for 10ns;
        sb <= "110";
        wait for 10ns;
        sb <= "000";
        wait;
    end process;
END;

```

 

2.4 DATA PATH

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY test_datapath IS
END test_datapath;

ARCHITECTURE behavior OF test_datapath IS

    COMPONENT datapath
    PORT(
        data_in : IN std_logic_vector(15 downto 0);
        constant_in : IN std_logic_vector(15 downto 0);
        D_select : IN std_logic_vector(16 downto 0);
        D_Clk : IN std_logic;
        D_Vout : OUT std_logic;
        D_Cout : OUT std_logic;
        D_Nout : OUT std_logic;
        D_Zout : OUT std_logic;
        address_out : OUT std_logic_vector(15 downto 0);
        data_out : OUT std_logic_vector(15 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal data_in : std_logic_vector(15 downto 0) := (others => '0');
    signal constant_in : std_logic_vector(15 downto 0) := (others => '0');
    signal D_select : std_logic_vector(16 downto 0) := (others => '0');
    signal D_Clk : std_logic := '0';

    --Outputs
    signal D_Vout : std_logic;
    signal D_Cout : std_logic;
    signal D_Nout : std_logic;
    signal D_Zout : std_logic;
    signal address_out : std_logic_vector(15 downto 0);
    signal data_out : std_logic_vector(15 downto 0);

    -- Clock period definitions
    constant D_Clk_period : time := 10 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: datapath PORT MAP (
        data_in => data_in,
        constant_in => constant_in,
        D_select => D_select,
        D_Clk => D_Clk,
        D_Vout => D_Vout,
        D_Cout => D_Cout,
        D_Nout => D_Nout,
```

```

        D_Zout => D_Zout,
        address_out => address_out,
        data_out => data_out
    );

-- Clock process definitions
D_Clk_process :process
begin
    D_Clk <= '0';
    wait for D_Clk_period/2;
    D_Clk <= '1';
    wait for D_Clk_period/2;
end process;

-- Stimulus process
stim_proc: process
begin
    data_in <= x"FFFF";
    constant_in <= x"0000";
    D_select <= "00000000100000011";


    wait for 20ns;
    data_in <= x"AAAA";
    D_select <= "00000000100000011";

    wait for 20ns;
    D_select <= "00000000100110001";

    wait for 20ns;
    D_select <= "01001001001000000";

    wait;
end process;

END;
```

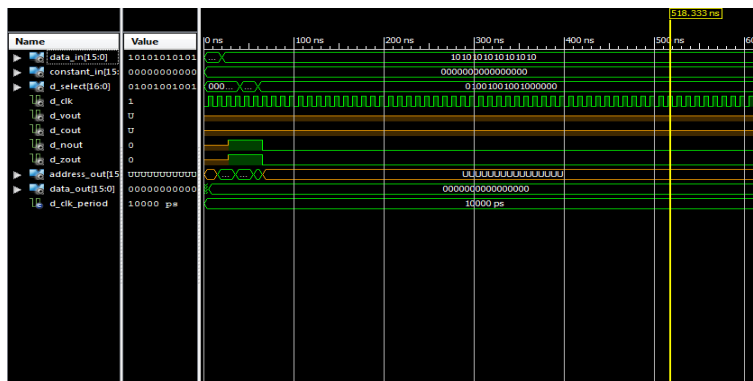

2.5 REGISTER FILE

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY test_register_file IS
END test_register_file;

ARCHITECTURE behavior OF test_register_file IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT register_file
    PORT(
        inA : IN std_logic_vector(3 downto 0);
        inB : IN std_logic_vector(3 downto 0);
        inD : IN std_logic_vector(3 downto 0);
        Clk : IN std_logic;
        load_in : IN std_logic;
        data : IN std_logic_vector(15 downto 0);
        outA : OUT std_logic_vector(15 downto 0);
        outB : OUT std_logic_vector(15 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal inA : std_logic_vector(3 downto 0) := (others => '0');
    signal inB : std_logic_vector(3 downto 0) := (others => '0');
    signal inD : std_logic_vector(3 downto 0) := (others => '0');
    signal Clk : std_logic := '0';
    signal load_in : std_logic := '0';
    signal data : std_logic_vector(15 downto 0) := (others => '0');

    --Outputs
    signal outA : std_logic_vector(15 downto 0);
    signal outB : std_logic_vector(15 downto 0);

    -- Clock period definitions
    constant Clk_period : time := 10 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: register_file PORT MAP (
        inA => inA,
        inB => inB,
        inD => inD,
        Clk => Clk,
        load_in => load_in,
        data => data,
        outA => outA,
        outB => outB
    );

    -- Clock process definitions
```



```

Clk_process :process
begin
    Clk <= '0';
    wait for Clk_period/2;
    Clk <= '1';
    wait for Clk_period/2;
end process;

```

```

-- Stimulus process

```

```

stim_proc: process
begin

```

```

    load_in <= '1';
    inD <= "0000";
    data <= x"FFFF";

```

```

    wait for 10ns;
    inD <= "0001";
    data <= x"EEEE";

```

```

    wait for 10ns;
    inD <= "0010";
    data <= x"DDDD";

```

```

    wait for 10ns;
    inD <= "0011";
    data <= x"CCCC";

```

```

    wait for 10ns;
    inD <= "0100";
    data <= x"BBBB";

```

```

        wait for 10ns;
    inD <= "0101";
    data <= x"AAAA";

```

```

    wait for 10ns;
    inD <= "0110";
    data <= x"9999";

```

```

    wait for 10ns;
    inD <= "0111";
    data <= x"8888";

```

```

    wait for 10ns;
    load_in <= '0';
    inA <= "0000";
    inB <= "0111";

```

```

    wait for 5ns;
    inA <= "0001";
    inB <= "0110";

```

```

    wait for 5ns;
    inA <= "0010";
    inB <= "0101";

```

```

wait for 5ns;
inA <= "0011";
inB <= "0100";

    wait;
end process;

END;

```



2.5.1 REG8

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY test_reg8 IS
END test_reg8;

ARCHITECTURE behavior OF test_reg8 IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT reg8
    PORT(
        load0 : IN std_logic;
        load1 : IN std_logic;
        Clk : IN std_logic;
        D : IN std_logic_vector(15 downto 0);
        Q : OUT std_logic_vector(15 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal load0 : std_logic := '0';
    signal load1 : std_logic := '0';
    signal Clk : std_logic := '0';
    signal D : std_logic_vector(15 downto 0) := (others => '0');

    --Outputs
    signal Q : std_logic_vector(15 downto 0);

    -- Clock period definitions
    constant Clk_period : time := 10 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: reg8 PORT MAP (
        load0 => load0,
        load1 => load1,
        Clk => Clk,
        D => D,
        Q => Q
    );

    -- Clock process definitions
    Clk_process :process
    begin
        Clk <= '0';
        wait for Clk_period/2;
        Clk <= '1';
        wait for Clk_period/2;
    end process;
```

```

-- Stimulus process
stim_proc: process
begin
    D <= x"FFFF";
    load0 <= '1';
    load1 <= '1';

    wait for 15ns;
    D <= x"AAAA";
    load0 <= '0';


    wait for 10ns;
    load1 <= '0';

    wait for 10ns;
    load0 <= '1';
    load1 <= '1';

    wait;
end process;

END;

```

 

2.5.2 DECODER

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY test_decoder_3to8 IS
END test_decoder_3to8;

ARCHITECTURE behavior OF test_decoder_3to8 IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT decoder_3to8
    PORT(
        A0 : IN std_logic;
        A1 : IN std_logic;
        A2 : IN std_logic;
        A3 : IN std_logic;
        Q0 : OUT std_logic;
        Q1 : OUT std_logic;
        Q2 : OUT std_logic;
        Q3 : OUT std_logic;
        Q4 : OUT std_logic;
        Q5 : OUT std_logic;
        Q6 : OUT std_logic;
        Q7 : OUT std_logic;
        Q8 : OUT std_logic
    );
    END COMPONENT;

    --Inputs
    signal A0 : std_logic := '0';
    signal A1 : std_logic := '0';
    signal A2 : std_logic := '0';
    signal A3 : std_logic := '0';

    --Outputs
    signal Q0 : std_logic;
    signal Q1 : std_logic;
    signal Q2 : std_logic;
    signal Q3 : std_logic;
    signal Q4 : std_logic;
    signal Q5 : std_logic;
    signal Q6 : std_logic;
    signal Q7 : std_logic;
    signal Q8 : std_logic;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: decoder_3to8 PORT MAP (
        A0 => A0,
        A1 => A1,
```

```

        A2 => A2,
        A3 => A3,
        Q0 => Q0,
        Q1 => Q1,
        Q2 => Q2,
        Q3 => Q3,
        Q4 => Q4,
        Q5 => Q5,
        Q6 => Q6,
        Q7 => Q7,
        Q8 => Q8
    );

stim_proc: process
begin

    wait for 5ns;
    A0 <= '0';
    A1 <= '0';
    A2 <= '0';
    A3 <= '1';

    wait for 5ns;
    A0 <= '1';
    A1 <= '0';
    A2 <= '0';
    A3 <= '0';

    wait for 5ns;
    A0 <= '0';
    A1 <= '1';
    A2 <= '0';
    A3 <= '1';

    wait for 5ns;
    A0 <= '1';
    A1 <= '1';
    A2 <= '0';
    A3 <= '0';

    wait for 5ns;
    A0 <= '0';
    A1 <= '0';
    A2 <= '1';
    A3 <= '1';

    wait for 5ns;
    A0 <= '1';
    A1 <= '0';
    A2 <= '1';
    A3 <= '0';

    wait for 5ns;
    A0 <= '0';
    A1 <= '1';

```

```


        A2 <= '1';
        A3 <= '0';

    wait for 5ns;
    A0 <= '1';
    A1 <= '1';
    A2 <= '1';
    A3 <= '0';

    wait;
end process;

END;

```

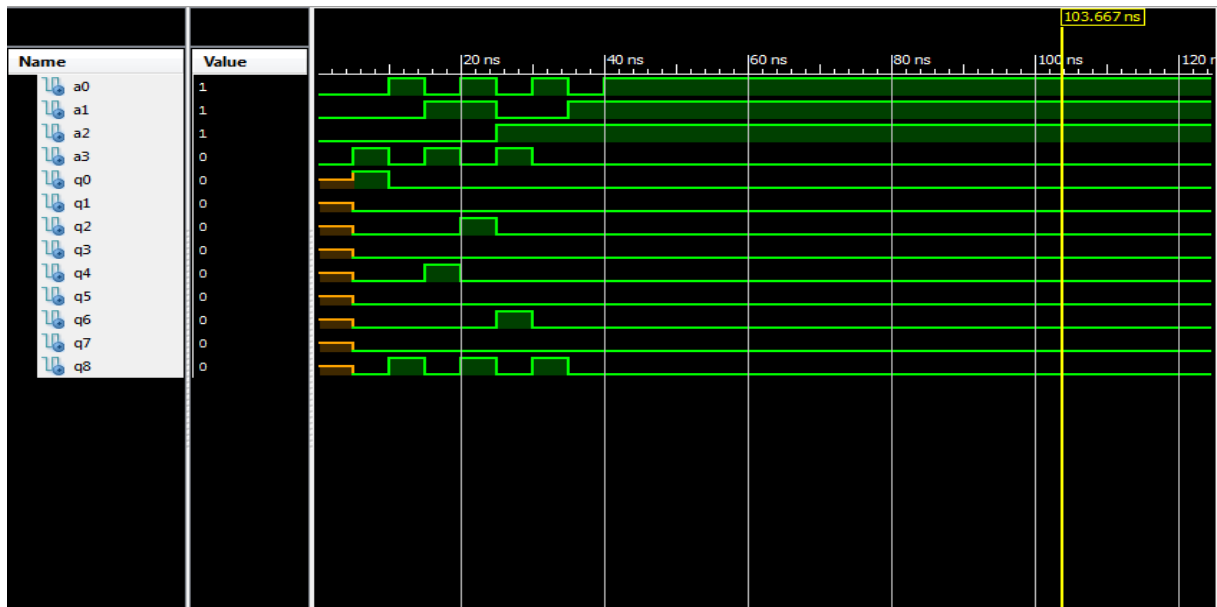

2.5.3 MUX3 TO 16BIT

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY test_mux3_16bit IS
END test_mux3_16bit;

ARCHITECTURE behavior OF test_mux3_16bit IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT mux3_16bit
    PORT(
        s : IN std_logic;
        In0 : IN std_logic_vector(15 downto 0);
        In1 : IN std_logic_vector(15 downto 0);
        Z : OUT std_logic_vector(15 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal s : std_logic := '0';
    signal In0 : std_logic_vector(15 downto 0) := (others => '0');
    signal In1 : std_logic_vector(15 downto 0) := (others => '0');

    --Outputs
    signal Z : std_logic_vector(15 downto 0);
    -- No clocks detected in port list. Replace <clock> below with
    -- appropriate port name

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: mux3_16bit PORT MAP (
        s => s,
        In0 => In0,
        In1 => In1,
        Z => Z
    );

    -- Stimulus process
    stim_proc: process
    begin
        In0 <= x"FFFF";
        In1 <= x"AAAA";

        wait for 10ns;
        s <= '1';
        wait for 10ns;
        s <= '0';
        wait for 10ns;
```




```

        s <= '1';
    wait;
end process;

END;

```

 

2.5.4 MUX8 TO 16BIT

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY test_mux8_16bit IS
END test_mux8_16bit;

ARCHITECTURE behavior OF test_mux8_16bit IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT mux8_16bit
    PORT(
        S0 : IN std_logic;
        S1 : IN std_logic;
        S2 : IN std_logic;
        S3 : IN std_logic;
        In0 : IN std_logic_vector(15 downto 0);
        In1 : IN std_logic_vector(15 downto 0);
        In2 : IN std_logic_vector(15 downto 0);
        In3 : IN std_logic_vector(15 downto 0);
        In4 : IN std_logic_vector(15 downto 0);
        In5 : IN std_logic_vector(15 downto 0);
        In6 : IN std_logic_vector(15 downto 0);
        In7 : IN std_logic_vector(15 downto 0);
        In8 : IN std_logic_vector(15 downto 0);
        Z : OUT std_logic_vector(15 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal S0 : std_logic := '0';
    signal S1 : std_logic := '0';
    signal S2 : std_logic := '0';
    signal S3 : std_logic := '0';
    signal In0 : std_logic_vector(15 downto 0) := (others => '0');
    signal In1 : std_logic_vector(15 downto 0) := (others => '0');
    signal In2 : std_logic_vector(15 downto 0) := (others => '0');
    signal In3 : std_logic_vector(15 downto 0) := (others => '0');
    signal In4 : std_logic_vector(15 downto 0) := (others => '0');
    signal In5 : std_logic_vector(15 downto 0) := (others => '0');
    signal In6 : std_logic_vector(15 downto 0) := (others => '0');
    signal In7 : std_logic_vector(15 downto 0) := (others => '0');
    signal In8 : std_logic_vector(15 downto 0) := (others => '0');

    --Outputs
    signal Z : std_logic_vector(15 downto 0);

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: mux8_16bit PORT MAP (
        S0 => S0,
```

```

        S1 => S1,
        S2 => S2,
        S3 => S3,
        In0 => In0,
        In1 => In1,
        In2 => In2,
        In3 => In3,
        In4 => In4,
        In5 => In5,
        In6 => In6,
        In7 => In7,
        In8 => In8,
        Z => Z
    );

stim_proc: process
begin
    In0 <= x"FFFF";
    In1 <= x"EEEE";
    In2 <= x"DDDD";
    In3 <= x"CCCC";
    In4 <= x"BBBB";
    In5 <= x"AAAA";
    In6 <= x"9999";
    In7 <= x"8888";
    In8 <= x"7777";

    wait for 10ns;
    S0 <='0';
    S1 <='0';
    S2 <='0';
    S3 <='0';

    wait for 10ns;
    S0 <='1';
    S1 <='0';
    S2 <='0';
    S3 <='1';

    wait for 10ns;
    S0 <='0';
    S1 <='1';
    S2 <='0';
    S3 <='0';

    wait for 10ns;
    S0 <='1';
    S1 <='1';
    S2 <='0';
    S3 <='1';

    wait for 10ns;
    S0 <='0';
    S1 <='0';
    S2 <='1';
    S3 <='0';

```

```

wait for 10ns;
S0 <='1';
S1 <='0';
S2 <='1';
S3 <='0';


wait for 10ns;
S0 <='0';
S1 <='1';
S2 <='1';
S3 <='0';

wait for 10ns;
S0 <='1';
S1 <='1';
S2 <='1';
S3 <='0';

wait;
end process;

END;

```

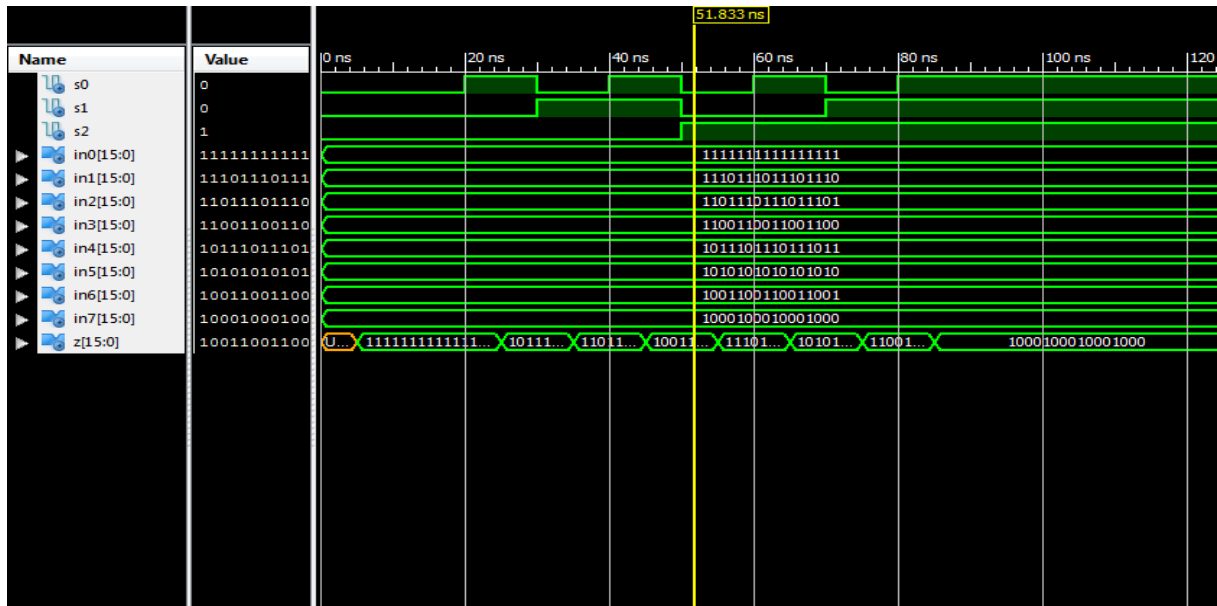

2.6 FUNCTION UNIT

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY test_function_unit IS
END test_function_unit;

ARCHITECTURE behavior OF test_function_unit IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT function_unit
    PORT(
        F_A : IN std_logic_vector(15 downto 0);
        F_B : IN std_logic_vector(15 downto 0);
        F_select : IN std_logic_vector(4 downto 0);
        F_Vout : OUT std_logic;
        F_Cout : OUT std_logic;
        F_Nout : OUT std_logic;
        F_Zout : OUT std_logic;
        F_F : OUT std_logic_vector(15 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal F_A : std_logic_vector(15 downto 0) := (others => '0');
    signal F_B : std_logic_vector(15 downto 0) := (others => '0');
    signal F_select : std_logic_vector(4 downto 0) := (others => '0');

    --Outputs
    signal F_Vout : std_logic;
    signal F_Cout : std_logic;
    signal F_Nout : std_logic;
    signal F_Zout : std_logic;
    signal F_F : std_logic_vector(15 downto 0);
    -- No clocks detected in port list. Replace <clock> below with
    -- appropriate port name

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: function_unit PORT MAP (
        F_A => F_A,
        F_B => F_B,
        F_select => F_select,
        F_Vout => F_Vout,
        F_Cout => F_Cout,
        F_Nout => F_Nout,
        F_Zout => F_Zout,
        F_F => F_F
    );
```

```

-- Stimulus process
stim_proc: process
begin

    F_A <= x"AAAA";
    F_B <= x"BBBB";

    wait for 20ns;
    F_select <= "00000";

    wait for 10ns;
    F_select <= "00001";
    wait for 10ns;
    F_select <= "00010";
    wait for 10ns;
    F_select <= "00011";
    wait for 20ns;
    F_select <= "00100";

    wait for 20ns;
    F_select <= "00101";
    wait for 20ns;
    F_select <= "00110";

    wait for 10ns;
    F_select <= "00111";
    wait for 10ns;
    F_select <= "01000";

    wait for 10ns;
    F_select <= "01001";
    wait for 10ns;
    F_select <= "01010";

    wait for 10ns;
    F_select <= "01011";
    wait for 10ns;
    F_select <= "01100";

    wait for 10ns;
    F_select <= "01101";
    wait for 10ns;
    F_select <= "01110";

    wait for 10ns;
    F_select <= "01111";
    wait for 10ns;
    F_select <= "10000";

    wait for 10ns;
    F_select <= "10001";
    wait for 10ns;
    F_select <= "10010";

```

```

    wait for 10ns;
    F_select <= "10011";
    wait for 10ns;
    F_select <= "10100";

    wait for 10ns;
    F_select <= "10101";
    wait for 10ns;
    F_select <= "10110";

    wait for 10ns;
    F_select <= "10111";
    wait for 10ns;
    F_select <= "11000";

    wait for 10ns;
    F_select <= "11001";
    wait for 10ns;
    F_select <= "11010";


    wait for 10ns;
    F_select <= "11011";
    wait for 10ns;
    F_select <= "11100";

    wait for 10ns;
    F_select <= "11101";
    wait for 10ns;
    F_select <= "11110";
    wait for 10ns;
    F_select <= "11111";

    wait;
end process;

END;

```

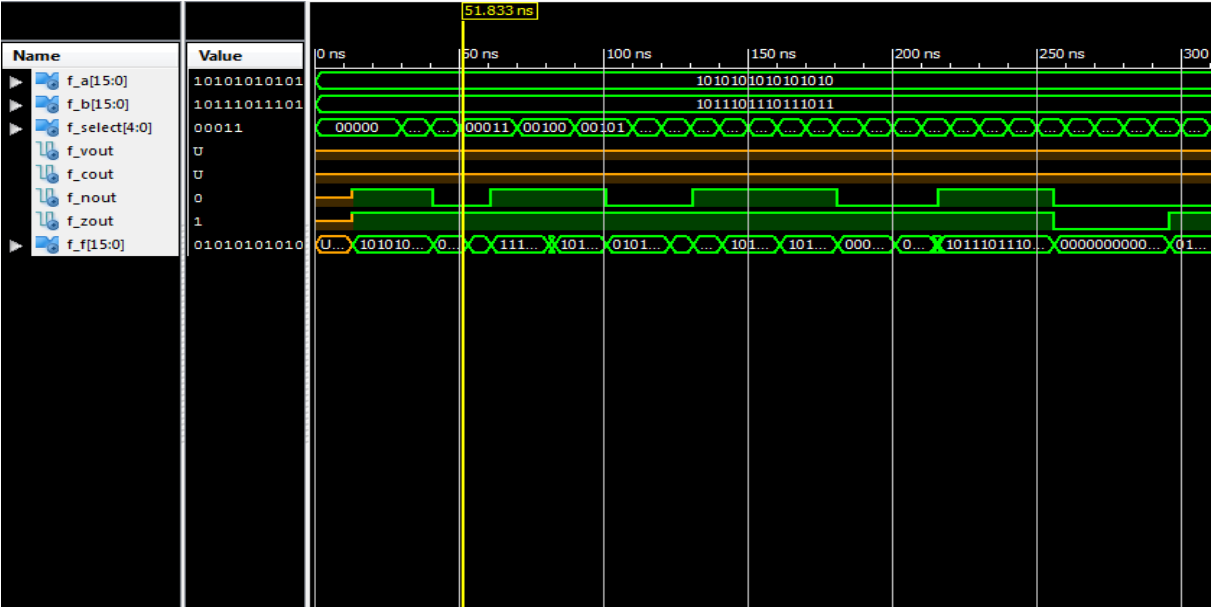

2.7 SHIFTER

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY test_shifter IS
END test_shifter;

ARCHITECTURE behavior OF test_shifter IS

    COMPONENT shifter
    PORT(
        B : IN std_logic_vector(15 downto 0);
        S : IN std_logic_vector(1 downto 0);
        IR : IN std_logic;
        IL : IN std_logic;
        H : OUT std_logic_vector(15 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal B : std_logic_vector(15 downto 0) := (others => '0');
    signal S : std_logic_vector(1 downto 0) := (others => '0');
    signal IR : std_logic := '0';
    signal IL : std_logic := '0';

    --Outputs
    signal H : std_logic_vector(15 downto 0);

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: shifter PORT MAP (
        B => B,
        S => S,
        IR => IR,
        IL => IL,
        H => H
    );

    stim_proc: process
    begin

        wait for 10ns;
        B <= x"FFFF";
        S <= "00";

        wait for 15ns;
        S <= "01";

        wait for 15ns;
        B <= H;

        wait for 15ns;
```


```

B <= H;
S <= "10";

    wait;
end process;

END;

```

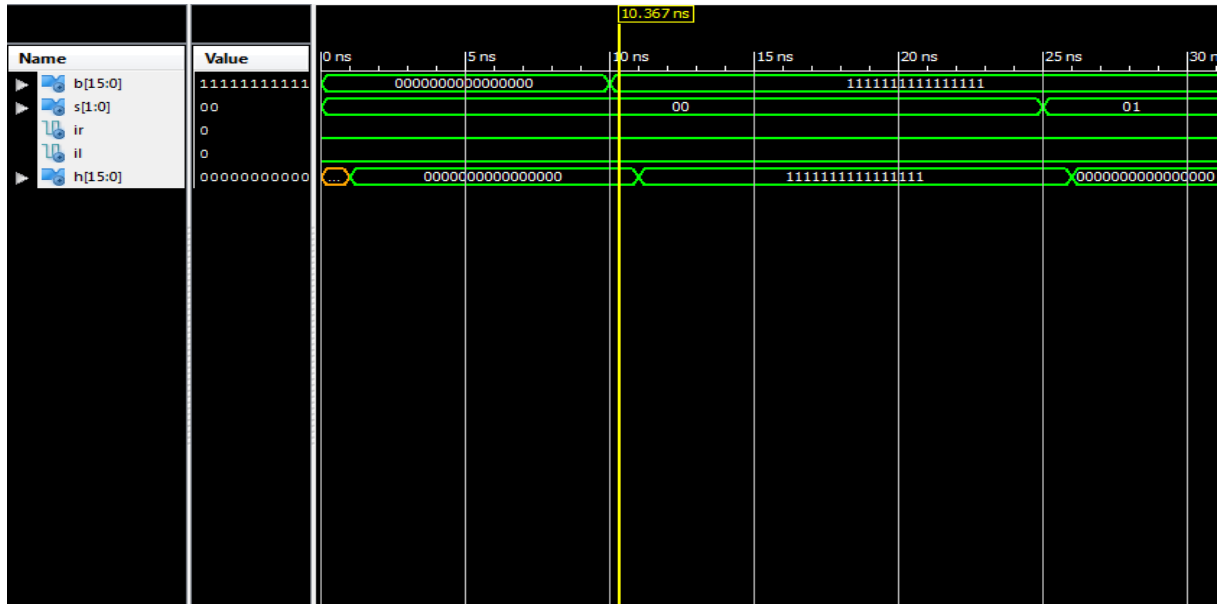

2.7.1 MUX3 TO 1BIT

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY test_mux3_1bit IS
END test_mux3_1bit;

ARCHITECTURE behavior OF test_mux3_1bit IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT mux3_1bit
    PORT(
        In0 : IN std_logic;
        In1 : IN std_logic;
        In2 : IN std_logic;
        S0 : IN std_logic;
        S1 : IN std_logic;
        Z : OUT std_logic
    );
    END COMPONENT;

    --Inputs
    signal In0 : std_logic := '0';
    signal In1 : std_logic := '0';
    signal In2 : std_logic := '0';
    signal S0 : std_logic := '0';
    signal S1 : std_logic := '0';

    --Outputs
    signal Z : std_logic;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: mux3_1bit PORT MAP (
        In0 => In0,
        In1 => In1,
        In2 => In2,
        S0 => S0,
        S1 => S1,
        Z => Z
    );

    stim_proc: process
    begin
        wait for 10ns;
        In0 <= '0';
        In1 <= '0';
        In2 <= '0';

        wait for 10ns;
```

```

In0 <= '1';
In1 <= '0';
In2 <= '1';

wait for 5ns;
S0 <= '0';
S1 <= '0';


wait for 5ns;
S0 <= '0';
S1 <= '1';

wait for 5ns;
S0 <= '1';
S1 <= '0';

wait for 5ns;
S0 <= '1';
S1 <= '1';
wait;
end process;

```

END;

 

2.8 ALU

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY test_alu IS
END test_alu;

ARCHITECTURE behavior OF test_alu IS

    COMPONENT arithmetic_logic_unit
    PORT(
        ALU_A : IN std_logic_vector(15 downto 0);
        ALU_B : IN std_logic_vector(15 downto 0);
        ALU_select : IN std_logic_vector(3 downto 0);
        ALU_Cout : OUT std_logic;
        ALU_Vout : OUT std_logic;
        ALU_G : OUT std_logic_vector(15 downto 0)
    );
    END COMPONENT;

--Inputs
signal ALU_A : std_logic_vector(15 downto 0) := (others => '0');
signal ALU_B : std_logic_vector(15 downto 0) := (others => '0');
signal ALU_select : std_logic_vector(3 downto 0) := (others => '0');

--Outputs
signal ALU_Cout : std_logic;
signal ALU_Vout : std_logic;
signal ALU_G : std_logic_vector(15 downto 0);

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: arithmetic_logic_unit PORT MAP (
        ALU_A => ALU_A,
        ALU_B => ALU_B,
        ALU_select => ALU_select,
        ALU_Cout => ALU_Cout,
        ALU_Vout => ALU_Vout,
        ALU_G => ALU_G
    );

    stim_proc: process
    begin
        ALU_A <= x"FFAA";
        ALU_B <= x"000F";
        ALU_select <= "0000";

        wait for 10ns;
        ALU_select <= "0000";

        wait for 10ns;
        ALU_select <= "0001";
```

```

    wait for 10ns;
    ALU_select <= "0010";

    wait for 10ns;
    ALU_select <= "0011";

    wait for 10ns;
    ALU_select <= "0100";

    wait for 10ns;
    ALU_select <= "0101";

    wait for 10ns;
    ALU_select <= "0110";

    wait for 10ns;
    ALU_select <= "0111";

    wait for 10ns;
    ALU_select <= "1000";

    wait for 10ns;
    ALU_select <= "1001";

    wait for 10ns;
    ALU_select <= "1010";

    wait for 10ns;
    ALU_select <= "1011";

    wait for 10ns;
    ALU_select <= "1100";

    wait for 10ns;
    ALU_select <= "1101";


    wait for 10ns;
    ALU_select <= "1110";

    wait for 10ns;
    ALU_select <= "1111";

    wait;
end process;

END;

```

 

2.8.1 LOGIC

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY test_logic IS
END test_logic;

ARCHITECTURE behavior OF test_logic IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT logic_circuit
    PORT(
        A : IN std_logic_vector(15 downto 0);
        B : IN std_logic_vector(15 downto 0);
        Cin : IN std_logic_vector(1 downto 0);
        Cout : OUT std_logic_vector(15 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal A : std_logic_vector(15 downto 0) := (others => '0');
    signal B : std_logic_vector(15 downto 0) := (others => '0');
    signal Cin : std_logic_vector(1 downto 0) := (others => '0');

    --Outputs
    signal Cout : std_logic_vector(15 downto 0);

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: logic_circuit PORT MAP (
        A => A,
        B => B,
        Cin => Cin,
        Cout => Cout
    );

    stim_proc: process
    begin
        wait for 10ns;
        A <= x"FFFF";
        B <= x"9999";
        Cin <= "00";

        wait for 10ns;
        Cin <= "01";

        wait for 10ns;
        Cin <= "10";

        wait for 10ns;
        Cin <= "11";
```




```

        wait;
    end process;

END;

```

 

2.8.2 B LOGIC

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY test_Blogic IS
END test_Blogic;

ARCHITECTURE behavior OF test_Blogic IS

    COMPONENT B_input_logic
    PORT(
        B : IN std_logic_vector(15 downto 0);
        S : IN std_logic_vector(1 downto 0);
        Y : OUT std_logic_vector(15 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal B : std_logic_vector(15 downto 0) := (others => '0');
    signal S : std_logic_vector(1 downto 0) := (others => '0');

    --Outputs
    signal Y : std_logic_vector(15 downto 0);

BEGIN


    -- Instantiate the Unit Under Test (UUT)
    uut: B_input_logic PORT MAP (
        B => B,
        S => S,
        Y => Y
    );

    stim_proc: process
    begin
        B <=x"AAAA";
        S <= "00";

        wait for 5ns;
        S <= "00";
        wait for 5ns;
        S <= "01";
        wait for 5ns;
        S <= "10";
        wait for 5ns;
        S <= "11";

        wait;
    end process;

END;
```

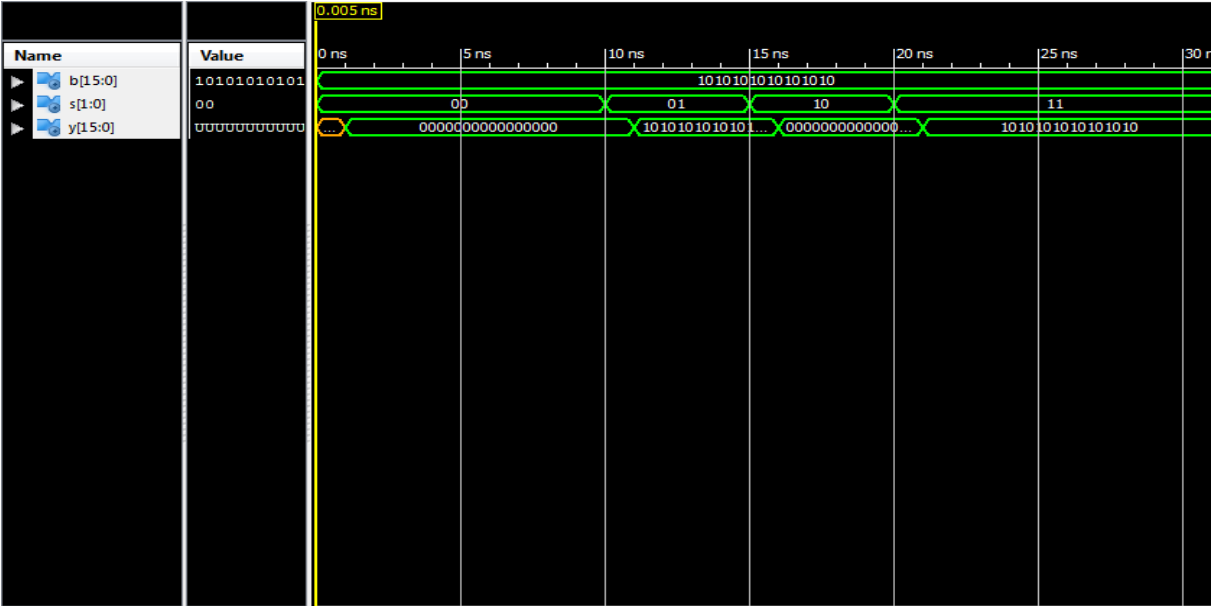

2.8.3 MUX2 TO 1BIT

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY test_mux2_1bit IS
END test_mux2_1bit;

ARCHITECTURE behavior OF test_mux2_1bit IS

    COMPONENT mux2_1bit
    PORT(
        S0 : IN std_logic;
        S1 : IN std_logic;
        Cin : IN std_logic;
        Res : OUT std_logic
    );
    END COMPONENT;

    --Inputs
    signal S0 : std_logic := '0';
    signal S1 : std_logic := '0';
    signal Cin : std_logic := '0';

    --Outputs
    signal Res : std_logic;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: mux2_1bit PORT MAP (
        S0 => S0,
        S1 => S1,
        Cin => Cin,
        Res => Res
    );


    stim_proc: process
    begin
        S0 <= '1';
        S1 <= '0';

        wait for 10ns;
        Cin <= '1';

        wait for 10ns;
        Cin <= '0';

        wait;
    end process;

END;
```

 

2.8.4 RIPPLE

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY test_ripple IS
END test_ripple;

ARCHITECTURE behavior OF test_ripple IS

    COMPONENT ripple_adder
    PORT(
        A : IN std_logic_vector(15 downto 0);
        B : IN std_logic_vector(15 downto 0);
        Cin : IN std_logic;
        Cout : OUT std_logic;
        Gout : OUT std_logic_vector(15 downto 0);
        Vout : OUT std_logic
    );
    END COMPONENT;

    --Inputs
    signal A : std_logic_vector(15 downto 0) := (others => '0');
    signal B : std_logic_vector(15 downto 0) := (others => '0');
    signal Cin : std_logic := '0';

    --Outputs
    signal Cout : std_logic;
    signal Gout : std_logic_vector(15 downto 0);
    signal Vout : std_logic;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: ripple_adder PORT MAP (
        A => A,
        B => B,
        Cin => Cin,
        Cout => Cout,
        Gout => Gout,
        Vout => Vout
    );

    stim_proc: process
    begin

        A <=x"AAAA";
        B <=x"FBAA";
        Cin <= '1';

        wait for 10ns;
        A <=x"FFFF";
        B <=x"0000";
        Cin <= '1';
```

```

        wait;
    end process;

END;

```



2.8.5 FULL ADDER

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY test_full_adder IS
END test_full_adder;

ARCHITECTURE behavior OF test_full_adder IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT full_adder
    PORT(
        X : IN std_logic;
        Y : IN std_logic;
        S : OUT std_logic;
        Cin : IN std_logic;
        Cout : OUT std_logic
    );
    END COMPONENT;

    --Inputs
    signal X : std_logic := '0';
    signal Y : std_logic := '0';
    signal Cin : std_logic := '0';

    --Outputs
    signal S : std_logic;
    signal Cout : std_logic;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: full_adder PORT MAP (
        X => X,
        Y => Y,
        S => S,
        Cin => Cin,
        Cout => Cout
    );

    stim_proc: process
    begin

        wait for 10ns;
        X <= '0';
        Y <= '0';

        wait for 10ns;
        X <= '0';
        Y <= '1';

        wait for 10ns;
```



```

X <= '1';
Y <= '0';

wait for 10ns;
X <= '1';
Y <= '1';

wait for 10ns;
Cin <= '1';

wait;
end process;

END;

```

