



Datapath Design

LABORATORY 1

CS2022 COMPUTER ARCHITECTURE

ALEXANDRU SULEA
D STREAM
#12315152
19 FEBRURARY 2015

Contents

List of Tables	1
1 CODE	1
1.1 DATA PATH	1
1.2 REGISTER FILE	3
1.2.1 REG8	7
1.2.2 DECODER	8
1.2.3 MUX3 TO 16BIT	9
1.2.4 MUX8 TO 16BIT	10
1.3 FUNCTION UNIT	12
1.4 SHIFTER	14
1.4.1 MUX3 TO 1BIT	17
1.5 ALU	18
1.5.1 B LOGIC	21
1.5.2 MUX2 TO 1BIT	24
1.5.3 RIPPLE	25
1.5.4 FULL ADDER	28
2 TESTBENCHES	29
2.1 DATA PATH	29
2.2 REGISTER FILE	30
2.2.1 REG8	31
2.2.2 DECODER	32
2.2.3 MUX3 TO 16BIT	33
2.2.4 MUX8 TO 16BIT	34
2.3 FUNCTION UNIT	35
2.4 SHIFTER	36
2.4.1 MUX3 TO 1BIT	37
2.5 ALU	38
2.5.1 LOGIC	39
2.5.2 B LOGIC	40
2.5.3 MUX2 TO 1BIT	41
2.5.4 RIPPLE	42
2.5.5 FULL ADDER	43

List of Tables

1 CODE

1.1 DATA PATH

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity datapath is
Port ( data_in : in STD_LOGIC_VECTOR(15 downto 0);
      constant_in : in STD_LOGIC_VECTOR(15 downto 0);
      D_select : in STD_LOGIC_VECTOR(16 downto 0);
      D_Clk : in STD_LOGIC;
      D_Vout : out STD_LOGIC;
      D_Cout : out STD_LOGIC;
      D_Nout : out STD_LOGIC;
      D_Zout : out STD_LOGIC;
      address_out : out STD_LOGIC_VECTOR(15 downto 0);
      data_out : out STD_LOGIC_VECTOR(15 downto 0));

end datapath;

architecture Behavioral of datapath is
component mux3_16bit
  Port ( s : in STD_LOGIC;
        In0 : in STD_LOGIC_VECTOR(15 downto 0);
        In1 : in STD_LOGIC_VECTOR(15 downto 0);
        Z : out STD_LOGIC_VECTOR(15 downto 0));
end Component;

Component function_unit
Port ( F_A : in STD_LOGIC_VECTOR(15 downto 0);
      F_B : in STD_LOGIC_VECTOR(15 downto 0);
      F_select : in STD_LOGIC_VECTOR(4 downto 0);
      F_Vout : out STD_LOGIC;
      F_Cout : out STD_LOGIC;
      F_Nout : out STD_LOGIC;
      F_Zout : out STD_LOGIC;
      F_F : out STD_LOGIC_VECTOR(15 downto 0));
end Component;

Component register_file
  Port ( inA : in STD_LOGIC_VECTOR(2 downto 0);
        inB : in STD_LOGIC_VECTOR(2 downto 0);
        inD : in STD_LOGIC_VECTOR(2 downto 0);
        Clk : in STD_LOGIC;
        load_in : in STD_LOGIC;
        data : in STD_LOGIC_VECTOR(15 downto 0);
        outA : out STD_LOGIC_VECTOR(15 downto 0);
        outB : out STD_LOGIC_VECTOR(15 downto 0));
end Component ;

signal src_muxD, src_muxB, src_regA, src_regB, src_out : STD_LOGIC_VECTOR(15 downto 0);

begin
Dreg_mux3_16bit : mux3_16bit PORT MAP ( s => D_select(1),
```

```

In0 => src_out,
In1 => data_in,
Z => src_muxD);


Breg_mux3_16bit : mux3_16bit PORT MAP ( s => D_select(7),
In0 => constant_in,
In1 => src_regB,
Z => src_muxB);

reg_function_unit: function_unit PORT MAP ( F_A => src_regA,
F_B => src_muxB,
F_select => D_select(6 downto 2),
F_Vout => D_Vout,
F_Cout => D_Cout,
F_Nout => D_Nout,
F_Zout => D_Zout,
F_F => src_out);

reg_register_file : register_file PORT MAP( inA => D_select(13 downto 11),
inB => D_select(10 downto 8),
inD => D_select(16 downto 14),
Clk => D_Clk,
load_in => D_select(0),
data => src_muxD,
outA => src_regA,
outB => src_regB);

data_out <= src_muxB;
address_out <= src_regA;
end Behavioral;

```

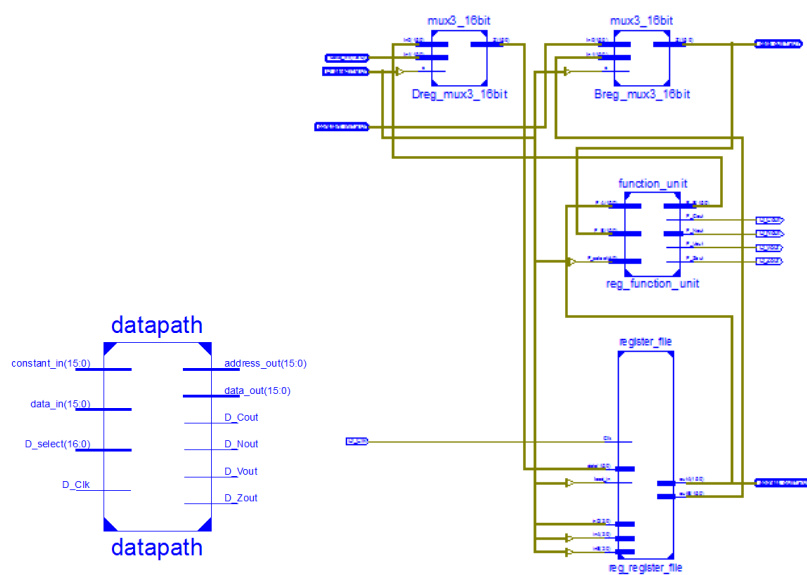

1.2 REGISTER FILE

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity register_file is
    Port (
        inA : in STD_LOGIC_VECTOR(2 downto 0);
        inB : in STD_LOGIC_VECTOR(2 downto 0);
        inD : in STD_LOGIC_VECTOR(2 downto 0);
        Clk : in STD_LOGIC;
        load_in : in STD_LOGIC;
        data : in STD_LOGIC_VECTOR(15 downto 0);
        outA : out STD_LOGIC_VECTOR(15 downto 0);
        outB : out STD_LOGIC_VECTOR(15 downto 0)
    );
end register_file;

architecture Behavioral of register_file is

    Component decoder_3to8
    Port ( A0 : in STD_LOGIC;
          A1 : in STD_LOGIC;
          A2 : in STD_LOGIC;
          Q0 : out STD_LOGIC;
          Q1 : out STD_LOGIC;
          Q2 : out STD_LOGIC;
          Q3 : out STD_LOGIC;
          Q4 : out STD_LOGIC;
          Q5 : out STD_LOGIC;
          Q6 : out STD_LOGIC;
          Q7 : out STD_LOGIC);
    End Component;

    Component mux3_16bit
    Port ( s : in STD_LOGIC;
          In0 : in STD_LOGIC_VECTOR(15 downto 0);
          In1 : in STD_LOGIC_VECTOR(15 downto 0);
          Z : out STD_LOGIC_VECTOR(15 downto 0));
    End Component;

    Component reg8
    Port ( load0 : in STD_LOGIC;
          load1 : in STD_LOGIC;
          Clk : in STD_LOGIC;
          D : in STD_LOGIC_VECTOR(15 downto 0);
          Q : out STD_LOGIC_VECTOR(15 downto 0));
    End Component;

    Component mux8_16bit
    Port ( S0 : in STD_LOGIC;
          S1 : in STD_LOGIC;
```

```

        S2 : in STD_LOGIC;
        In0 : in STD_LOGIC_VECTOR(15 downto 0);
        In1 : in STD_LOGIC_VECTOR(15 downto 0);
        In2 : in STD_LOGIC_VECTOR(15 downto 0);
        In3 : in STD_LOGIC_VECTOR(15 downto 0);
        In4 : in STD_LOGIC_VECTOR(15 downto 0);
        In5 : in STD_LOGIC_VECTOR(15 downto 0);
        In6 : in STD_LOGIC_VECTOR(15 downto 0);
        In7 : in STD_LOGIC_VECTOR(15 downto 0);
        Z : out STD_LOGIC_VECTOR(15 downto 0));
End Component;

signal load_reg0, load_reg1, load_reg2, load_reg3, load_reg4,
        load_reg5, load_reg6, load_reg7 : STD_LOGIC;
signal reg0_q, reg1_q, reg2_q, reg3_q, reg4_q, reg5_q, reg6_q,
        reg7_q, d_mux, src_reg, src_A, src_B : STD_LOGIC_VECTOR(15 downto 0);

begin
    reg_decoder_3to8 : decoder_3to8 PORT MAP(
        A0 => inD(0),
        A1 => inD(1),
        A2 => inD(2),
        Q0 => load_reg0,
        Q1 => load_reg1,
        Q2 => load_reg2,
        Q3 => load_reg3,
        Q4 => load_reg4,
        Q5 => load_reg5,
        Q6 => load_reg6,
        Q7 => load_reg7
    );

    A_reg_mux8_16bit : mux8_16bit PORT MAP(
        S0 => inA(0),
        S1 => inA(1),
        S2 => inA(2),
        In0 => reg0_q,
        In1 => reg1_q,
        In2 => reg2_q,
        In3 => reg3_q,
        In4 => reg4_q,
        In5 => reg5_q,
        In6 => reg6_q,
        In7 => reg7_q,
        Z => src_A
    );

    B_reg_mux8_16bit : mux8_16bit PORT MAP(
        S0 => inB(0),
        S1 => inB(1),
        S2 => inB(2),
        In0 => reg0_q,
        In1 => reg1_q,
        In2 => reg2_q,
        In3 => reg3_q,
        In4 => reg4_q,

```

```

    In5 => reg5_q,
    In6 => reg6_q,
    In7 => reg7_q,
    Z => src_B
);

reg00 : reg8 PORT MAP(
    load0 => load_reg0,
    load1 => load_in,
    Clk => Clk,
    D => data,
    Q => reg0_q);

reg01 : reg8 PORT MAP(
    load0 => load_reg1,
    load1 => load_in,
    Clk => Clk,
    D => data,
    Q => reg1_q);

reg02 : reg8 PORT MAP(
    load0 => load_reg2,
    load1 => load_in,
    Clk => Clk,
    D => data,
    Q => reg2_q);

reg03 : reg8 PORT MAP(
    load0 => load_reg3,
    load1 => load_in,
    Clk => Clk,
    D => data,
    Q => reg3_q);

reg04 : reg8 PORT MAP(
    load0 => load_reg4,
    load1 => load_in,
    Clk => Clk,
    D => data,
    Q => reg4_q);

reg05 : reg8 PORT MAP(
    load0 => load_reg5,
    load1 => load_in,
    Clk => Clk,
    D => data,
    Q => reg5_q);

reg06 : reg8 PORT MAP(
    load0 => load_reg6,
    load1 => load_in,
    Clk => Clk,
    D => data,
    Q => reg6_q);

reg07 : reg8 PORT MAP(

```


```

    load0 => load_reg7,
    load1 => load_in,
    Clk => Clk,
    D => data,
    Q => reg7_q);

    outA <= src_A;
    outB <= src_B;

end Behavioral;

```

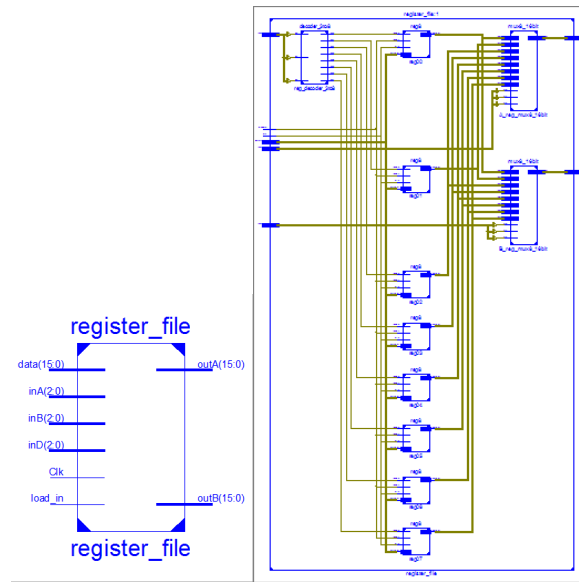


1.2.1 REG8

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity reg8 is
    Port ( load0 : in STD_LOGIC;
          load1 : in STD_LOGIC;
          Clk : in STD_LOGIC;
          D : in STD_LOGIC_VECTOR(15 downto 0);
          Q : out STD_LOGIC_VECTOR(15 downto 0));
end reg8;

architecture Behavioral of reg8 is

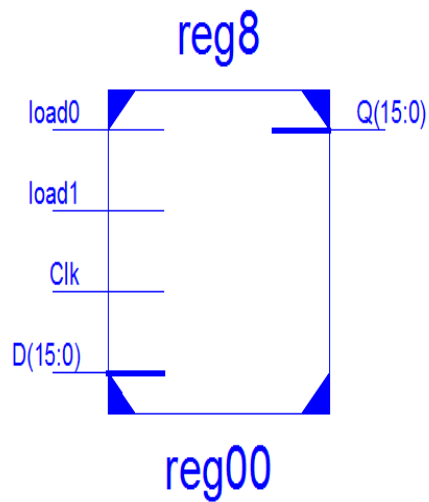begin
    process(Clk)
    begin
        if(rising_edge(Clk)) then
            if(load0 = '1') and (load1 = '1') then
                Q<= D after 5ns;
            end if;
        end if;
    end process;
end Behavioral;
```



1.2.2 DECODER


```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity decoder_3to8 is
    Port ( A0 : in STD_LOGIC;
          A1 : in STD_LOGIC;
          A2 : in STD_LOGIC;
          Q0 : out STD_LOGIC;
          Q1 : out STD_LOGIC;
          Q2 : out STD_LOGIC;
          Q3 : out STD_LOGIC;
          Q4 : out STD_LOGIC;
          Q5 : out STD_LOGIC;
          Q6 : out STD_LOGIC;
          Q7 : out STD_LOGIC);
end decoder_3to8;

architecture Behavioral of decoder_3to8 is

begin
    Q0 <= (( NOT A0) AND (NOT A1) AND (NOT A2)) AFTER 5ns;
    Q1 <= (( NOT A0) AND (NOT A1) AND A2) AFTER 5ns;
    Q2 <= (( NOT A0) AND A1 AND (NOT A2)) AFTER 5ns;
    Q3 <= (( NOT A0) AND A1 AND A2) AFTER 5ns;
    Q4 <= (A0 AND (NOT A1) AND (NOT A2)) AFTER 5ns;
    Q5 <= (A0 AND (NOT A1) AND A2) AFTER 5ns;
    Q6 <= (A0 AND A1 AND (NOT A2)) AFTER 5ns;
    Q7 <= (A0 AND A1 AND A2) AFTER 5ns;

end Behavioral;
```

 

1.2.3 MUX3 TO 16BIT


```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity mux3_16bit is
    Port ( s : in STD_LOGIC;
          In0 : in STD_LOGIC_VECTOR(15 downto 0);
          In1 : in STD_LOGIC_VECTOR(15 downto 0);
          Z : out STD_LOGIC_VECTOR(15 downto 0));
end mux3_16bit;

architecture Behavioral of mux3_16bit is

begin
    Z <= In0 after 5ns when s = '0' else
        In1 after 5ns when s = '1' else
        x"0000" after 5ns;

end Behavioral;
```

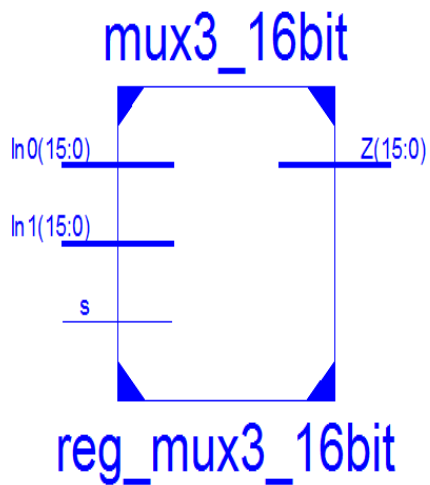

1.2.4 MUX8 TO 16BIT

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity mux8_16bit is
    Port ( S0 : in STD_LOGIC;
          S1 : in STD_LOGIC;
          S2 : in STD_LOGIC;
          In0 : in STD_LOGIC_VECTOR(15 downto 0);
          In1 : in STD_LOGIC_VECTOR(15 downto 0);
          In2 : in STD_LOGIC_VECTOR(15 downto 0);
          In3 : in STD_LOGIC_VECTOR(15 downto 0);
          In4 : in STD_LOGIC_VECTOR(15 downto 0);
          In5 : in STD_LOGIC_VECTOR(15 downto 0);
          In6 : in STD_LOGIC_VECTOR(15 downto 0);
          In7 : in STD_LOGIC_VECTOR(15 downto 0);
          Z : out STD_LOGIC_VECTOR(15 downto 0));
end mux8_16bit;

architecture Behavioral of mux8_16bit is
begin
    Z <= In0 after 5ns when S0 = '0' and S1 = '0' and S2 = '0' else
        In1 after 5ns when S0 = '0' and S1 = '0' and S2 = '1' else
        In2 after 5ns when S0 = '0' and S1 = '1' and S2 = '0' else
        In3 after 5ns when S0 = '0' and S1 = '1' and S2 = '1' else
        In4 after 5ns when S0 = '1' and S1 = '0' and S2 = '0' else
        In5 after 5ns when S0 = '1' and S1 = '0' and S2 = '1' else
        In6 after 5ns when S0 = '1' and S1 = '1' and S2 = '0' else
        In7 after 5ns when S0 = '1' and S1 = '1' and S2 = '1' else
        x"0000" after 5ns;
end Behavioral;
```



1.3 FUNCTION UNIT

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity function_unit is
Port ( F_A : in STD_LOGIC_VECTOR(15 downto 0);
      F_B : in STD_LOGIC_VECTOR(15 downto 0);
      F_select : in STD_LOGIC_VECTOR(4 downto 0);
      F_Vout : out STD_LOGIC;
      F_Cout : out STD_LOGIC;
      F_Nout : out STD_LOGIC;
      F_Zout : out STD_LOGIC;
      F_F : out STD_LOGIC_VECTOR(15 downto 0));
end function_unit;

architecture Behavioral of function_unit is

Component arithmetic_logic_unit
  Port ( ALU_A : in STD_LOGIC_VECTOR(15 downto 0);
        ALU_B : in STD_LOGIC_VECTOR(15 downto 0);
        ALU_select : in STD_LOGIC_VECTOR(3 downto 0);
        ALU_Cout : out STD_LOGIC;
        ALU_Vout : out STD_LOGIC;
        ALU_G : out STD_LOGIC_VECTOR(15 downto 0));
end Component;

Component shifter Port ( B : in STD_LOGIC_VECTOR(15 downto 0);
  S : in STD_LOGIC_VECTOR(1 downto 0);
  IR : in STD_LOGIC;
  IL : in STD_LOGIC;
  H : out STD_LOGIC_VECTOR(15 downto 0));
end Component;

Component mux3_16bit Port ( s : in STD_LOGIC;
  In0 : in STD_LOGIC_VECTOR(15 downto 0);
  In1 : in STD_LOGIC_VECTOR(15 downto 0);
  Z : out STD_LOGIC_VECTOR(15 downto 0));
end Component;

signal src_ALU, src_shift, src_mux : STD_LOGIC_VECTOR(15 downto 0);

begin

reg_arithmetic_logic_unit : arithmetic_logic_unit
  Port MAP ( ALU_A => F_A,
            ALU_B => F_B,
            ALU_select => F_select(3 downto 0),
            ALU_Cout => F_Cout,
            ALU_Vout => F_Vout,
            ALU_G => src_ALU);

reg_shifter : shifter Port MAP ( B => F_B,
  S => F_select(3 downto 2),
```

```


        IR => '0',
        IL => '0',
        H => src_shift);

reg_mux3_16bit : mux3_16bit Port MAP ( s => F_select(4),
        In0 => src_ALU,
        In1 => src_shift,
        Z => src_mux);

F_F <= src_mux;
F_Nout <= src_mux(15);
F_Zout <= ((src_mux(15)) or (src_mux(14)) or (src_mux(13)) or
        (src_mux(12)) or (src_mux(11)) or (src_mux(10)) or
        (src_mux(9)) or (src_mux(8)) or (src_mux(7)) or
        (src_mux(6)) or (src_mux(5)) or (src_mux(4)) or
        (src_mux(3)) or (src_mux(2)) or
        (src_mux(1)) or (src_mux(0)));

end Behavioral;

```

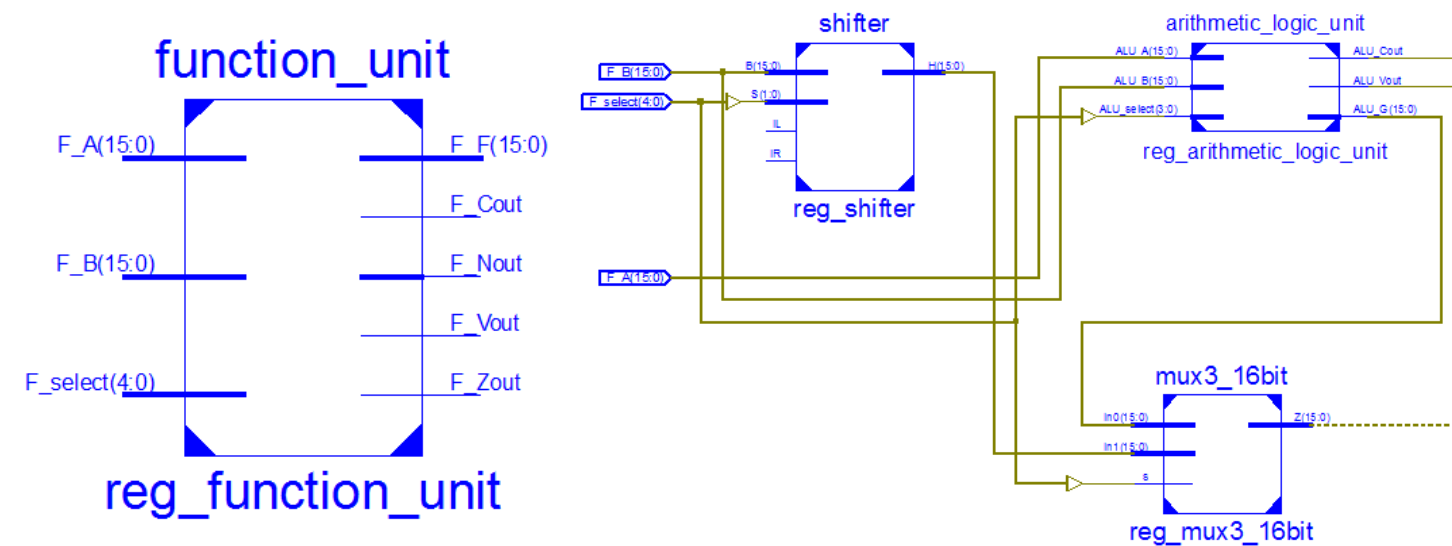

1.4 SHIFTER

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity shifter is
    Port ( B : in STD_LOGIC_VECTOR(15 downto 0);
          S : in STD_LOGIC_VECTOR(1 downto 0);
          IR : in STD_LOGIC;
          IL : in STD_LOGIC;
          H : out STD_LOGIC_VECTOR(15 downto 0));
end shifter;

architecture Behavioral of shifter is

    component mux3_1bit Port ( In0 : in STD_LOGIC;
                              In1 : in STD_LOGIC;
                              In2 : in STD_LOGIC;
                              S0 : in STD_LOGIC;
                              S1 : in STD_LOGIC;
                              Z : out STD_LOGIC);
    end component;

begin

    mux3_1bit00 : mux3_1bit PORT MAP ( In0 =>B(0) ,
                                       In1 => B(1),
                                       In2 => IL,
                                       S0 => S(0),
                                       S1 => S(1),
                                       Z  => H(0));

    mux3_1bit01 : mux3_1bit PORT MAP ( In0 =>B(1) ,
                                       In1 => B(2),
                                       In2 => B(0),
                                       S0 => S(0),
                                       S1 => S(1),
                                       Z  => H(1));

    mux3_1bit02 : mux3_1bit PORT MAP ( In0 =>B(2) ,
                                       In1 => B(3),
                                       In2 => B(1),
                                       S0 => S(0),
                                       S1 => S(1),
                                       Z  => H(2));

    mux3_1bit03 : mux3_1bit PORT MAP ( In0 =>B(3) ,
                                       In1 => B(4),
                                       In2 => B(2),
                                       S0 => S(0),
                                       S1 => S(1),
                                       Z  => H(3));
```



```

mux3_1bit04 : mux3_1bit PORT MAP ( In0 =>B(4) ,
    In1 => B(5),
    In2 => B(3),
    S0 => S(0),
    S1 => S(1),
    Z  => H(4));

mux3_1bit05 : mux3_1bit PORT MAP ( In0 =>B(5) ,
    In1 => B(6),
    In2 => B(4),
    S0 => S(0),
    S1 => S(1),
    Z  => H(5));

mux3_1bit06 : mux3_1bit PORT MAP ( In0 =>B(6) ,
    In1 => B(7),
    In2 => B(5),
    S0 => S(0),
    S1 => S(1),
    Z  => H(6));

mux3_1bit07 : mux3_1bit PORT MAP ( In0 =>B(7) ,
    In1 => B(8),
    In2 => B(6),
    S0 => S(0),
    S1 => S(1),
    Z  => H(7));

mux3_1bit08 : mux3_1bit PORT MAP ( In0 =>B(8) ,
    In1 => B(9),
    In2 => B(7),
    S0 => S(0),
    S1 => S(1),
    Z  => H(8));

mux3_1bit09 : mux3_1bit PORT MAP ( In0 =>B(9) ,
    In1 => B(10),
    In2 => B(8),
    S0 => S(0),
    S1 => S(1),
    Z  => H(9));

mux3_1bit10 : mux3_1bit PORT MAP ( In0 =>B(10) ,
    In1 => B(11),
    In2 => B(9),
    S0 => S(0),
    S1 => S(1),
    Z  => H(10));

mux3_1bit11 : mux3_1bit PORT MAP ( In0 =>B(11) ,
    In1 => B(12),
    In2 => B(10),
    S0 => S(0),
    S1 => S(1),
    Z  => H(11));

```

```


mux3_1bit12 : mux3_1bit PORT MAP ( In0 =>B(12) ,
    In1 => B(13),
    In2 => B(11),
    S0 => S(0),
    S1 => S(1),
    Z  => H(12));

mux3_1bit13 : mux3_1bit PORT MAP ( In0 =>B(13) ,
    In1 => B(14),
    In2 => B(12),
    S0 => S(0),
    S1 => S(1),
    Z  => H(13));

mux3_1bit14 : mux3_1bit PORT MAP ( In0 =>B(14) ,
    In1 => B(15),
    In2 => B(13),
    S0 => S(0),
    S1 => S(1),
    Z  => H(14));

mux3_1bit15 : mux3_1bit PORT MAP ( In0 =>B(15) ,
    In1 => IR,
    In2 => B(14),
    S0 => S(0),
    S1 => S(1),
    Z  => H(15));
end Behavioral;

```

 

1.4.1 MUX3 TO 1BIT

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity mux3_1bit is
    Port ( In0 : in STD_LOGIC;
          In1 : in STD_LOGIC;
          In2 : in STD_LOGIC;
          S0 : in STD_LOGIC;
          S1 : in STD_LOGIC;
          Z : out STD_LOGIC);
end mux3_1bit;

architecture Behavioral of mux3_1bit is

begin
    Z <= In0 after 1ns when S0 = '0' and S1='0' else
        In1 after 1ns when S0 ='0' and S1= '1' else
        In2 after 1ns when S0 ='0' and S1 = '0' else
        '0' after 1ns;

end Behavioral;
```

1.5 ALU

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity arithmetic_logic_unit is
    Port ( ALU_A : in STD_LOGIC_VECTOR(15 downto 0);
          ALU_B : in STD_LOGIC_VECTOR(15 downto 0);
          ALU_select : in STD_LOGIC_VECTOR(3 downto 0);
          ALU_Cout : out STD_LOGIC;
          ALU_Vout : out STD_LOGIC;
          ALU_G : out STD_LOGIC_VECTOR(15 downto 0));
end arithmetic_logic_unit;

architecture Behavioral of arithmetic_logic_unit is

    component ripple_adder Port ( A : in STD_LOGIC_VECTOR(15 downto 0);
                                B : in STD_LOGIC_VECTOR(15 downto 0);
                                Cin : in STD_LOGIC;
                                Cout : out STD_LOGIC;
                                Gout : out STD_LOGIC_VECTOR(15 downto 0);
                                Vout : out STD_LOGIC);
    End Component;

    component mux3_16bit Port ( s : in STD_LOGIC;
                               In0 : in STD_LOGIC_VECTOR(15 downto 0);
                               In1 : in STD_LOGIC_VECTOR(15 downto 0);
                               Z : out STD_LOGIC_VECTOR(15 downto 0));
    End Component;

    component B_input_logic Port ( B : in STD_LOGIC_VECTOR(15 downto 0);
                                  S : in STD_LOGIC_VECTOR(1 downto 0);
                                  Y : out STD_LOGIC_VECTOR(15 downto 0));
    End Component;

    Component logic_circuit Port ( A : in STD_LOGIC_VECTOR(15 downto 0);
                                   B : in STD_LOGIC_VECTOR(15 downto 0);
                                   Cin : in STD_LOGIC_VECTOR(1 downto 0);
                                   Cout : out STD_LOGIC_VECTOR(15 downto 0));
    End Component;

    signal src_logic , src_B_input_logic, src_ripple : STD_LOGIC_VECTOR(15 downto 0);

begin

    reg_ripple_adder : ripple_adder PORT MAP ( A => ALU_A,
        B => src_logic,
        Cin => ALU_select(0),
        Cout => ALU_Cout,
        Gout => src_ripple,
        Vout => ALU_Vout);
```

```

reg_mux3_16bit :mux3_16bit PORT MAP ( s => ALU_select(3),
    In0 => src_ripple,
    In1 => src_B_input_logic,
    Z =>ALU_G);

```

```

reg_B_input_logic : B_input_logic PORT MAP ( B => ALU_B,
    S => ALU_SELECT(2 downto 1),
    Y => src_logic);

```

```


reg_logic_circuit : logic_circuit PORT MAP( A => ALU_A ,
    B => ALU_B,
    Cin => ALU_select(2 downto 1),
    Cout => src_B_input_logic);

```

```

end Behavioral;

```

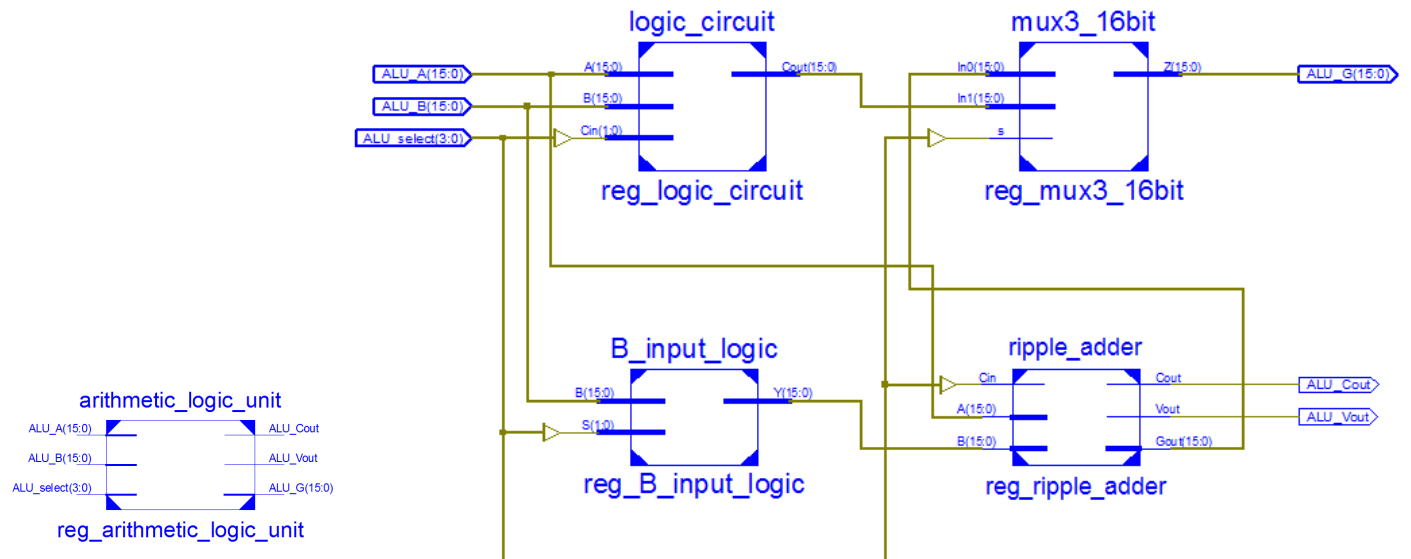


LOGIC

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity logic_circuit is
    Port ( A : in STD_LOGIC_VECTOR(15 downto 0);
          B : in STD_LOGIC_VECTOR(15 downto 0);
          Cin : in STD_LOGIC_VECTOR(1 downto 0);
          Cout : out STD_LOGIC_VECTOR(15 downto 0));
end logic_circuit;

architecture Behavioral of logic_circuit is

 begin
    Cout <= (A and B) after 1ns when Cin = "00" else
            (A or B) after 1ns when Cin = "01" else
            (A xor B) after 1ns when Cin = "10" else
            (not (A)) after 1ns;
end Behavioral;
```



1.5.1 B LOGIC

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity B_input_logic is
    Port ( B : in STD_LOGIC_VECTOR(15 downto 0);
          S : in STD_LOGIC_VECTOR(1 downto 0);
          Y : out STD_LOGIC_VECTOR(15 downto 0));
end B_input_logic;

architecture Behavioral of B_input_logic is

    component mux2_1bit Port ( S0 : in STD_LOGIC;
                              S1 : in STD_LOGIC;
                              Cin : in STD_LOGIC;
                              Res : out STD_LOGIC);

    End Component;

begin
    mux2_1bit00 : mux2_1bit PORT MAP( S0 => S(0),
                                      S1 => S(1),
                                      Cin => B(0),
                                      Res => Y(0));

    mux2_1bit01 : mux2_1bit PORT MAP( S0 => S(0),
                                      S1 => S(1),
                                      Cin => B(1),
                                      Res => Y(1));

    mux2_1bit02 : mux2_1bit PORT MAP( S0 => S(0),
                                      S1 => S(1),
                                      Cin => B(2),
                                      Res => Y(2));

    mux2_1bit03 : mux2_1bit PORT MAP( S0 => S(0),
                                      S1 => S(1),
                                      Cin => B(3),
                                      Res => Y(3));

    mux2_1bit04 : mux2_1bit PORT MAP( S0 => S(0),
                                      S1 => S(1),
                                      Cin => B(4),
                                      Res => Y(4));

    mux2_1bit05 : mux2_1bit PORT MAP( S0 => S(0),
                                      S1 => S(1),
                                      Cin => B(5),
                                      Res => Y(5));

    mux2_1bit06 : mux2_1bit PORT MAP( S0 => S(0),
                                      S1 => S(1),
                                      Cin => B(6),
                                      Res => Y(6));
```

```

mux2_1bit07 : mux2_1bit PORT MAP( S0 => S(0),
                                   S1 => S(1),
                                   Cin =>B(7),
                                   Res => Y(7));

mux2_1bit08 : mux2_1bit PORT MAP( S0 => S(0),
                                   S1 => S(1),
                                   Cin =>B(8),
                                   Res => Y(8));

mux2_1bit09 : mux2_1bit PORT MAP( S0 => S(0),
                                   S1 => S(1),
                                   Cin =>B(9),
                                   Res => Y(9));

mux2_1bit10 : mux2_1bit PORT MAP( S0 => S(0),
                                   S1 => S(1),
                                   Cin =>B(10),
                                   Res => Y(10));

mux2_1bit11 : mux2_1bit PORT MAP( S0 => S(0),
                                   S1 => S(1),
                                   Cin =>B(11),
                                   Res => Y(11));

mux2_1bit12 : mux2_1bit PORT MAP( S0 => S(0),
                                   S1 => S(1),
                                   Cin =>B(12),
                                   Res => Y(12));


mux2_1bit13 : mux2_1bit PORT MAP( S0 => S(0),
                                   S1 => S(1),
                                   Cin =>B(13),
                                   Res => Y(13));

mux2_1bit14 : mux2_1bit PORT MAP( S0 => S(0),
                                   S1 => S(1),
                                   Cin =>B(14),
                                   Res => Y(14));

mux2_1bit15 : mux2_1bit PORT MAP( S0 => S(0),
                                   S1 => S(1),
                                   Cin =>B(15),
                                   Res => Y(15));

end Behavioral;

```

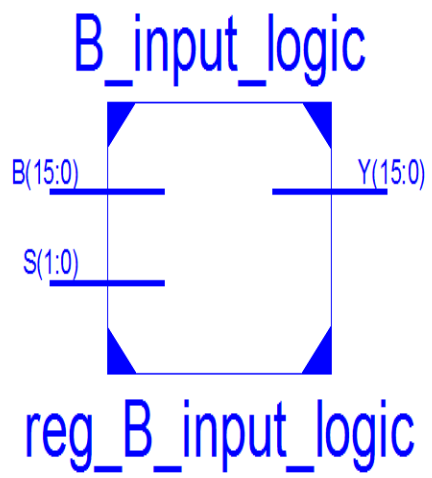1.5.2 MUX2 TO 1BIT


```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity mux2_1bit is
    Port ( S0 : in STD_LOGIC;
          S1 : in STD_LOGIC;
          Cin : in STD_LOGIC;
          Res : out STD_LOGIC);
end mux2_1bit;

architecture Behavioral of mux2_1bit is

begin
    Res <= S0 after 1ns when Cin = '1' else
           S1 after 1ns when Cin = '1' else
           '0' after 1ns;

end Behavioral;
```

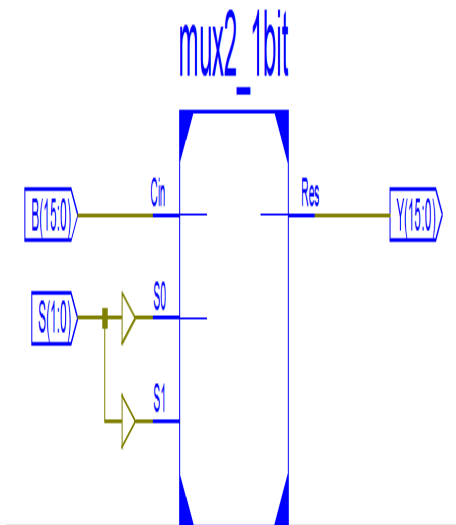

1.5.3 RIPPLE

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity ripple_adder is
    Port ( A : in STD_LOGIC_VECTOR(15 downto 0);
          B : in STD_LOGIC_VECTOR(15 downto 0);
          Cin : in STD_LOGIC;
          Cout : out STD_LOGIC;
          Gout : out STD_LOGIC_VECTOR(15 downto 0);
          Vout : out STD_LOGIC);
end ripple_adder;

architecture Behavioral of ripple_adder is

    Component full_adder
    PORT(X: in STD_LOGIC;
         Y: in STD_LOGIC;
         S: out STD_LOGIC;
         Cin: in STD_LOGIC;
         Cout: out STD_LOGIC);
    End Component;

    signal src_sig0, src_sig1, src_sig2, src_sig3, src_sig4,
           src_sig5, src_sig6, src_sig7, src_sig8, src_sig9, src_sig10,
           src_sig11, src_sig12, src_sig13, src_sig14, src_sig15,
           src_out: STD_LOGIC;
    begin
        full_adder00 : full_adder PORT MAP(X => A(0),
                                           Y => B(0),
                                           S => Gout(0),
                                           Cin => Cin,
                                           Cout =>src_sig0 );

        full_adder01 : full_adder PORT MAP(X => A(1),
                                           Y => B(1),
                                           S => Gout(1),
                                           Cin => Cin,
                                           Cout =>src_sig1);

        full_adder02 : full_adder PORT MAP(X => A(2),
                                           Y => B(2),
                                           S => Gout(2),
                                           Cin => Cin,
                                           Cout =>src_sig2);

        full_adder03 : full_adder PORT MAP(X => A(3),
                                           Y => B(3),
                                           S => Gout(3),
                                           Cin => Cin,
                                           Cout =>src_sig3);
```

```

full_adder04 : full_adder PORT MAP(X => A(4),
                                   Y => B(4),
                                   S => Gout(4),
                                   Cin => Cin,
                                   Cout =>src_sig4);

full_adder05 : full_adder PORT MAP(X => A(5),
                                   Y => B(5),
                                   S => Gout(5),
                                   Cin => Cin,
                                   Cout =>src_sig5);

full_adder06 : full_adder PORT MAP(X => A(6),
                                   Y => B(6),
                                   S => Gout(6),
                                   Cin => Cin,
                                   Cout =>src_sig6);

full_adder07 : full_adder PORT MAP(X => A(7),
                                   Y => B(7),
                                   S => Gout(7),
                                   Cin => Cin,
                                   Cout =>src_sig7);

full_adder08 : full_adder PORT MAP(X => A(8),
                                   Y => B(8),
                                   S => Gout(8),
                                   Cin => Cin,
                                   Cout =>src_sig8);

full_adder09 : full_adder PORT MAP(X => A(9),
                                   Y => B(9),
                                   S => Gout(9),
                                   Cin => Cin,
                                   Cout =>src_sig9);

full_adder10 : full_adder PORT MAP(X => A(10),
                                   Y => B(10),
                                   S => Gout(10),
                                   Cin => Cin,
                                   Cout =>src_sig10);

full_adder11 : full_adder PORT MAP(X => A(11),
                                   Y => B(11),
                                   S => Gout(11),
                                   Cin => Cin,
                                   Cout =>src_sig11);

full_adder12 : full_adder PORT MAP(X => A(12),
                                   Y => B(12),
                                   S => Gout(12),
                                   Cin => Cin,
                                   Cout =>src_sig12);

full_adder13 : full_adder PORT MAP(X => A(13),
                                   Y => B(13),

```

```


        S => Gout(13),
        Cin => Cin,
        Cout =>src_sig13);

full_adder14 : full_adder PORT MAP(X => A(14),
        Y => B(14),
        S => Gout(14),
        Cin => Cin,
        Cout =>src_sig14);

full_adder15 : full_adder PORT MAP(X => A(15),
        Y => B(15),
        S => Gout(15),
        Cin => Cin,
        Cout =>src_sig15);

end Behavioral;

```

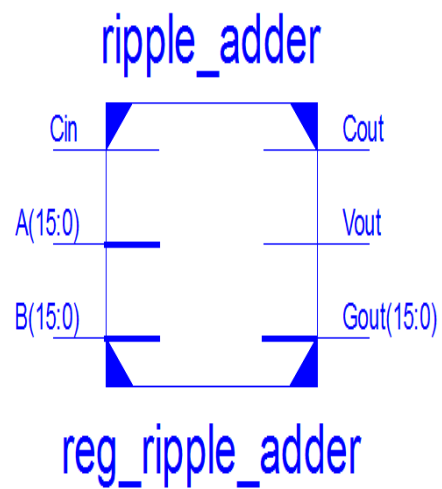

1.5.4 FULL ADDER


```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity full_adder is
PORT(X: in STD_LOGIC;
      Y: in STD_LOGIC;
      S: out STD_LOGIC;
      Cin: in STD_LOGIC;
      Cout: out STD_LOGIC);
end full_adder;

architecture Behavioral of full_adder is


    signal S1, S2, S3: STD_LOGIC;
begin
    S1 <= (X xor Y) after 1ns;
    S2 <= (Cin and S1) after 1ns;
    S3 <= (X and Y) after 1ns;
    S <= (S1 xor Cin) after 1ns;
    Cout <= (S2 or S3) after 1ns;

end Behavioral;
```

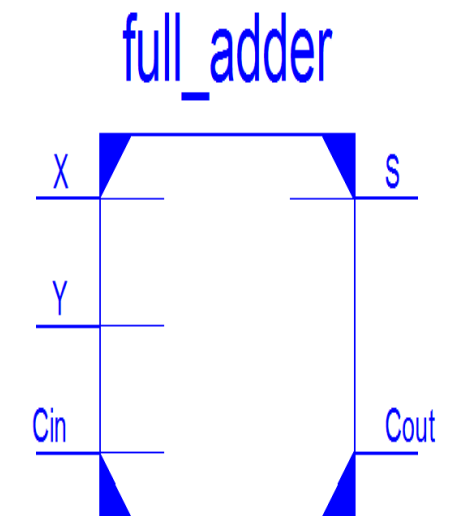


2 TESTBENCHES


2.1 DATA PATH

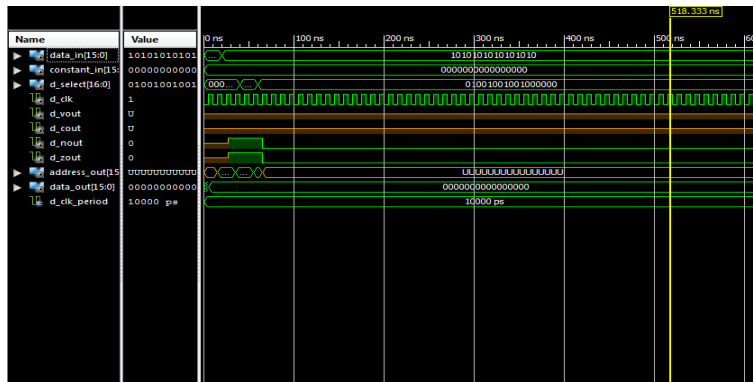


2.2 REGISTER FILE

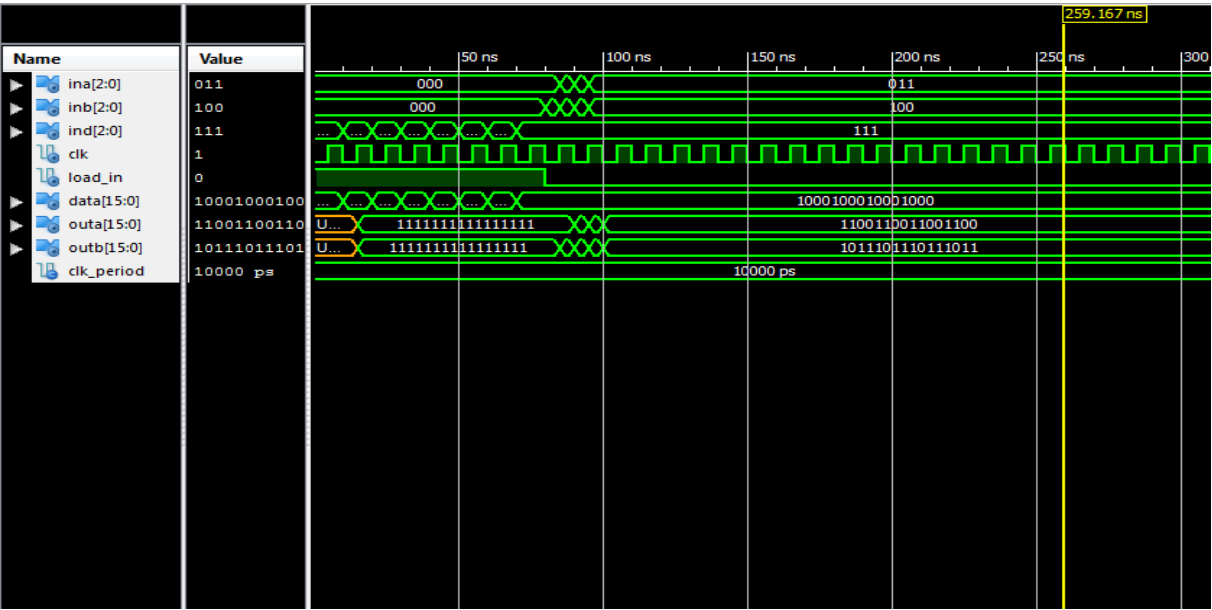


2.2.1 REG8

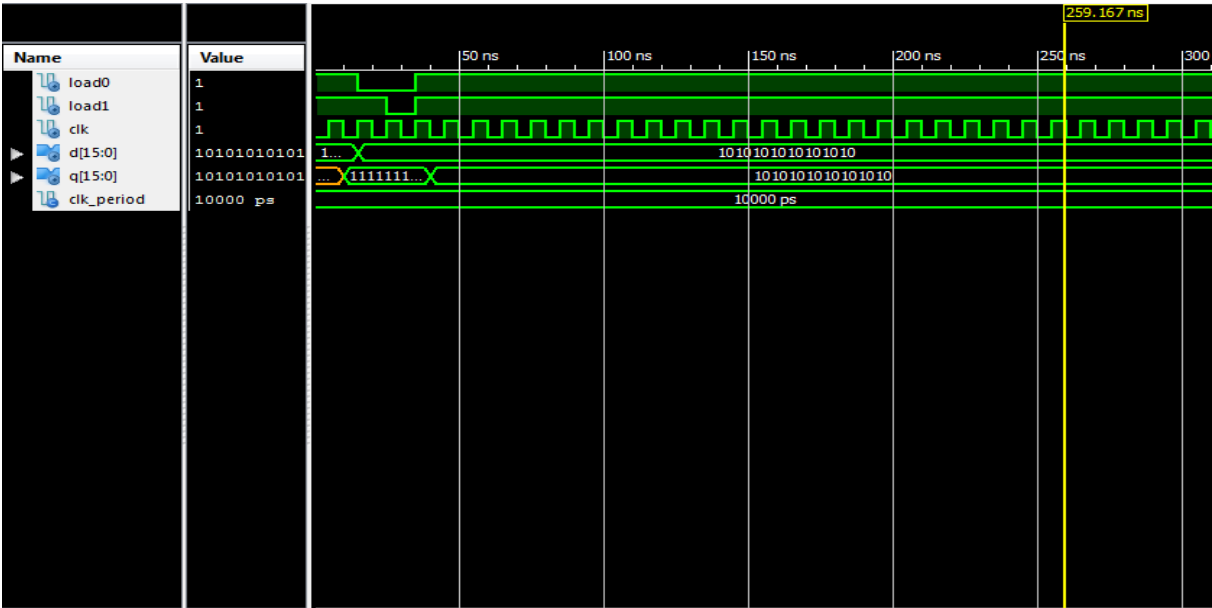

2.2.2 DECODER

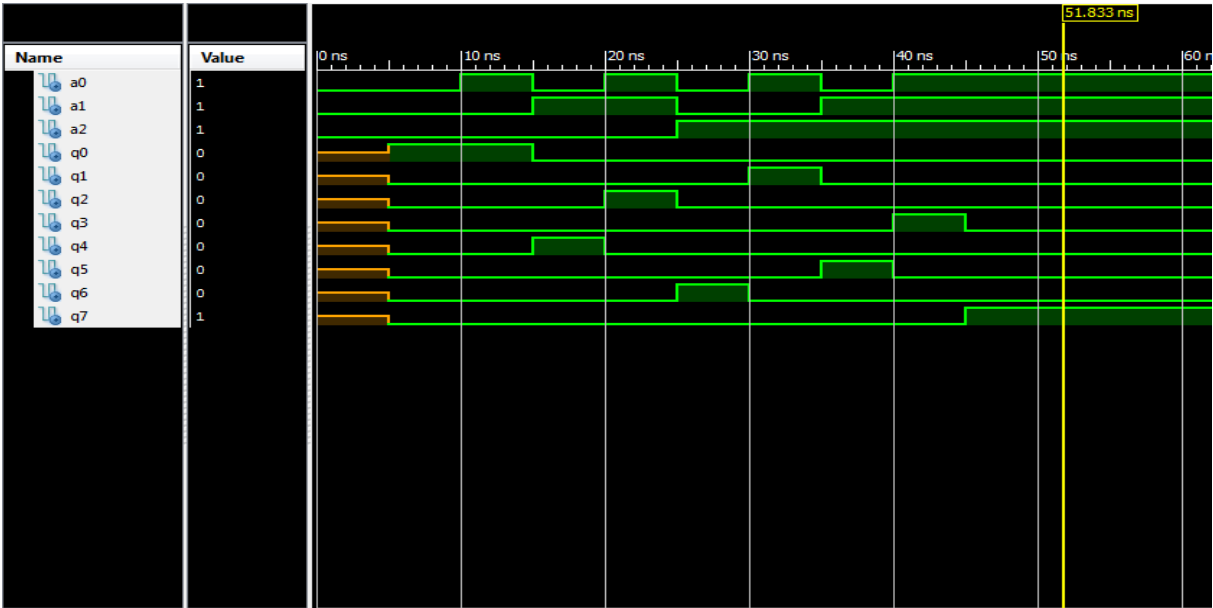

2.2.3 MUX3 TO 16BIT

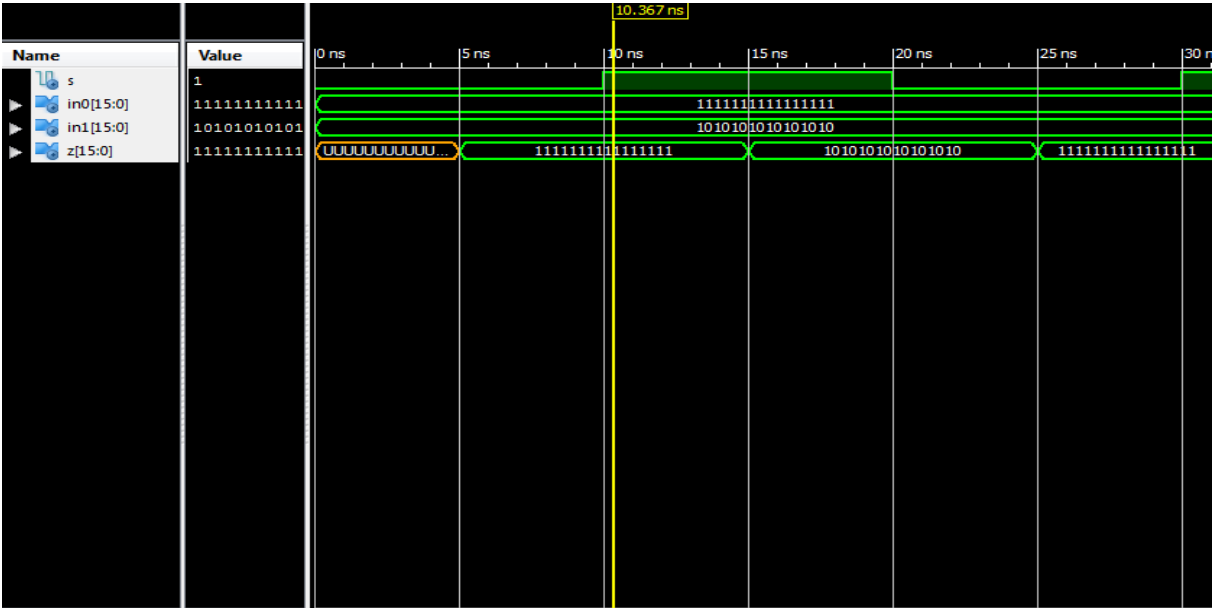


2.2.4 MUX8 TO 16BIT




2.3 FUNCTION UNIT




2.4 SHIFTER

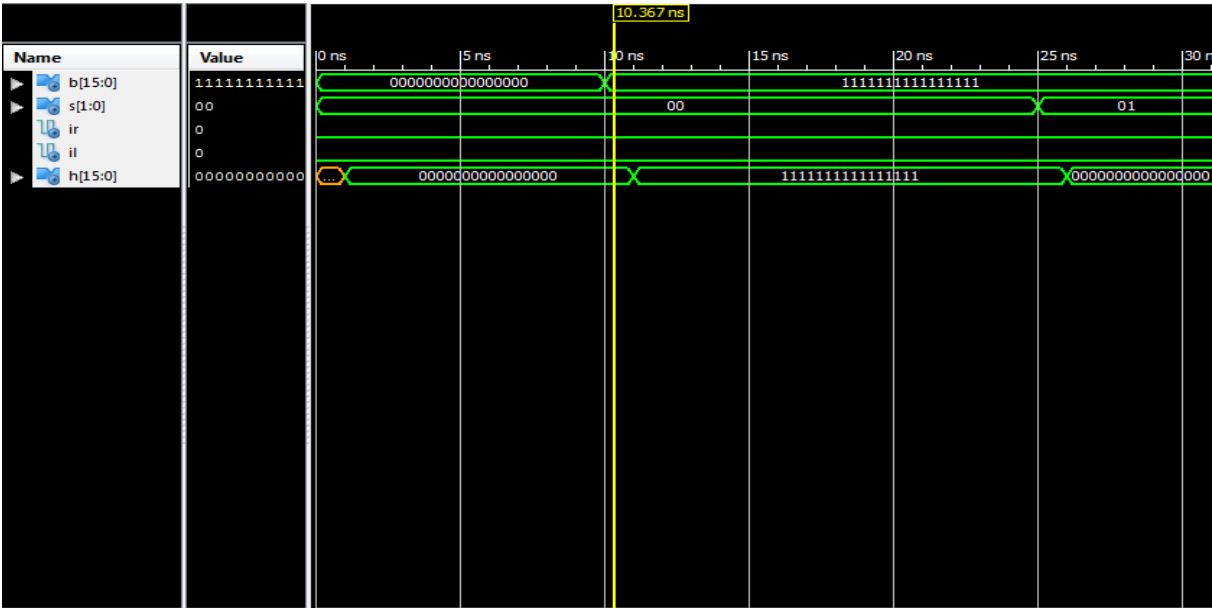


2.4.1 MUX3 TO 1BIT

 


2.5 ALU

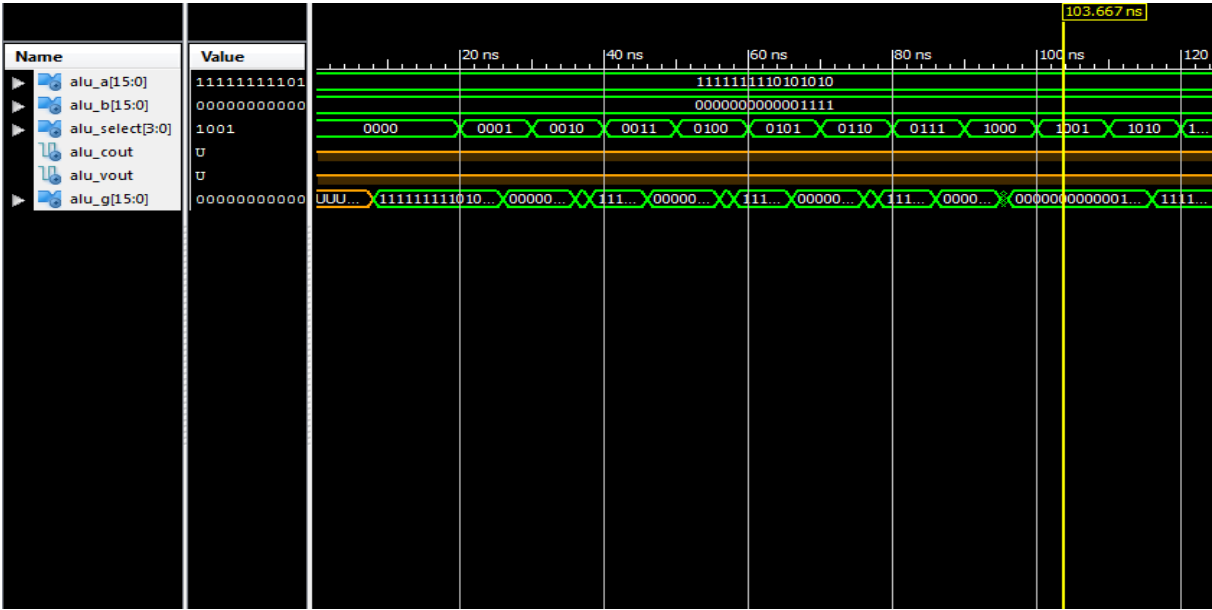


2.5.1 LOGIC

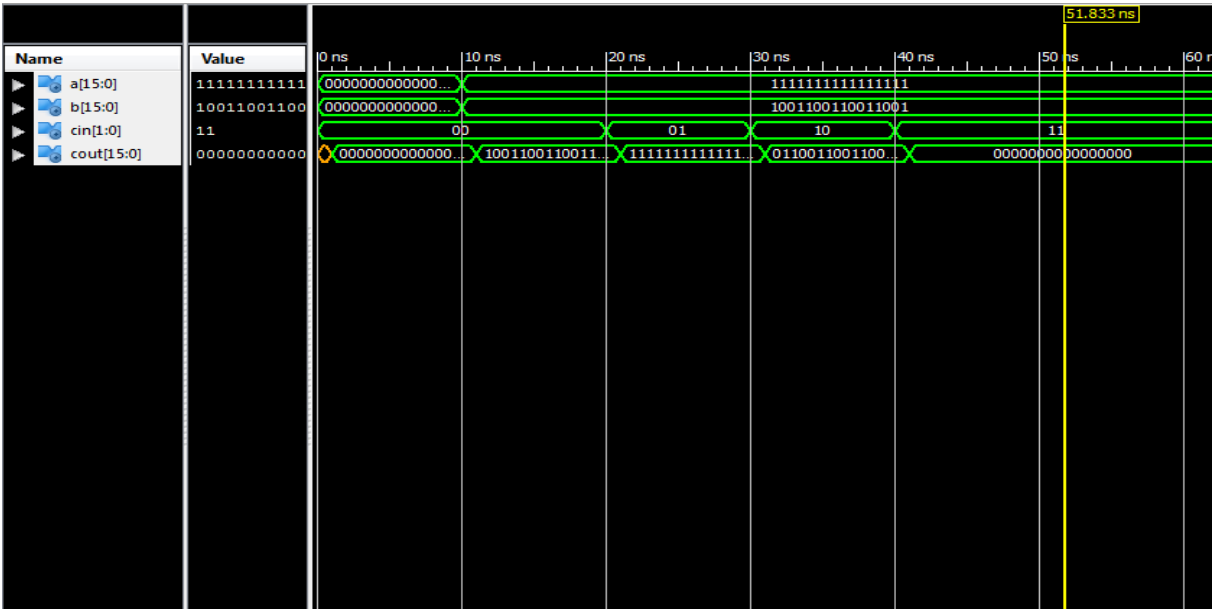


2.5.2 B LOGIC

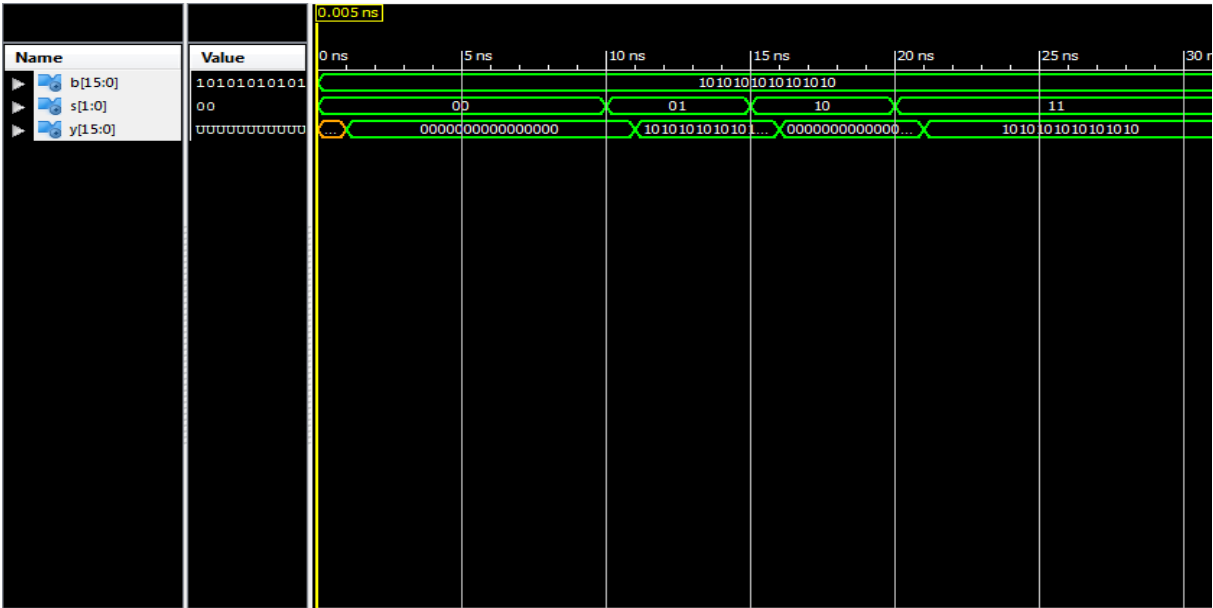

2.5.3 MUX2 TO 1BIT

 

2.5.4 RIPPLE

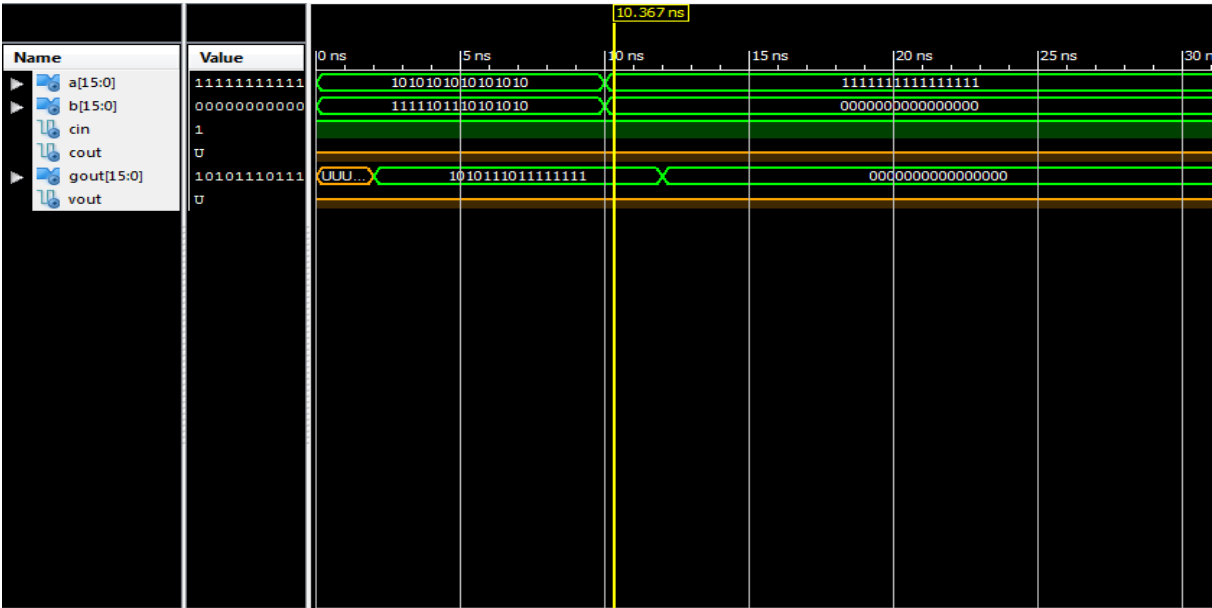

2.5.5 FULL ADDER

