



Datapath Design

LABORATORY 1

CS2022 COMPUTER ARCHITECTURE

ALEXANDRU SULEA
D STREAM
#12315152
19 FEBRUARY 2015

Contents

List of Tables	1
1 CODE	1
1.1 REGISTER FILE	1
1.2 REG8	5
1.3 DECODER	6
1.4 MUX3	7
1.5 MUX8	8
2 TESTBENCHES	10
2.1 REGISTER FILE 1	10
2.2 REGISTER FILE 2	13
2.3 REG8	17
2.4 DECODER	19
2.5 MUX3	22
2.6 MUX8	24

List of Tables

1 CODE

1.1 REGISTER FILE

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity register_file is
    Port ( src_S0 : in STD_LOGIC;
          src_S1 : in STD_LOGIC;
          src_S2 : in STD_LOGIC;
          des_A0 : in STD_LOGIC;
          des_A1 : in STD_LOGIC;
          des_A2 : in STD_LOGIC;
          Clk : in STD_LOGIC;
          data_src : in STD_LOGIC;
          data : in STD_LOGIC_VECTOR(15 downto 0);
          reg0 : out STD_LOGIC_VECTOR(15 downto 0);
          reg1 : out STD_LOGIC_VECTOR(15 downto 0);
          reg2 : out STD_LOGIC_VECTOR(15 downto 0);
          reg3 : out STD_LOGIC_VECTOR(15 downto 0);
          reg4 : out STD_LOGIC_VECTOR(15 downto 0);
          reg5 : out STD_LOGIC_VECTOR(15 downto 0);
          reg6 : out STD_LOGIC_VECTOR(15 downto 0);
          reg7 : out STD_LOGIC_VECTOR(15 downto 0));
end register_file;

architecture Behavioral of register_file is

    Component decoder_3to8
    Port ( A0 : in STD_LOGIC;
          A1 : in STD_LOGIC;
          A2 : in STD_LOGIC;
          Q0 : out STD_LOGIC;
          Q1 : out STD_LOGIC;
          Q2 : out STD_LOGIC;
          Q3 : out STD_LOGIC;
          Q4 : out STD_LOGIC;
          Q5 : out STD_LOGIC;
          Q6 : out STD_LOGIC;
          Q7 : out STD_LOGIC);
    End Component;

    Component mux3_16bit
    Port ( s : in STD_LOGIC;
          In0 : in STD_LOGIC_VECTOR(15 downto 0);
          In1 : in STD_LOGIC_VECTOR(15 downto 0);
          Z : out STD_LOGIC_VECTOR(15 downto 0));
    End Component;

    Component reg8
    Port ( load : in STD_LOGIC;
```

```

        Clk : in STD_LOGIC;
        D : in STD_LOGIC_VECTOR(15 downto 0);
        Q : out STD_LOGIC_VECTOR(15 downto 0));
End Component;

Component mux8_16bit
Port ( S0 : in STD_LOGIC;
       S1 : in STD_LOGIC;
       S2 : in STD_LOGIC;
       In0 : in STD_LOGIC_VECTOR(15 downto 0);
       In1 : in STD_LOGIC_VECTOR(15 downto 0);
       In2 : in STD_LOGIC_VECTOR(15 downto 0);
       In3 : in STD_LOGIC_VECTOR(15 downto 0);
       In4 : in STD_LOGIC_VECTOR(15 downto 0);
       In5 : in STD_LOGIC_VECTOR(15 downto 0);
       In6 : in STD_LOGIC_VECTOR(15 downto 0);
       In7 : in STD_LOGIC_VECTOR(15 downto 0);
       Z : out STD_LOGIC_VECTOR(15 downto 0));
End Component;

signal load_reg0, load_reg1, load_reg2, load_reg3, load_reg4,
        load_reg5, load_reg6, load_reg7 : STD_LOGIC;
signal reg0_q, reg1_q, reg2_q, reg3_q, reg4_q, reg5_q, reg6_q,
        reg7_q, d_mux, src_reg : STD_LOGIC_VECTOR(15 downto 0);

begin
reg_decoder_3to8 : decoder_3to8 PORT MAP(
    A0 => des_A0,
    A1 => des_A1,
    A2 => des_A2,
    Q0 => load_reg0,
    Q1 => load_reg1,
    Q2 => load_reg2,
    Q3 => load_reg3,
    Q4 => load_reg4,
    Q5 => load_reg5,
    Q6 => load_reg6,
    Q7 => load_reg7
);
reg_mux3_16bit : mux3_16bit PORT MAP(
    s => data_src,
    In0 => data,
    In1 => src_reg,
    Z => d_mux
);
reg_mux8_16bit : mux8_16bit PORT MAP(
    S0 => src_s0,
    S1 => src_s1,
    S2 => src_s2,
    In0 => reg0_q,
    In1 => reg1_q,
    In2 => reg2_q,
    In3 => reg3_q,
    In4 => reg4_q,
    In5 => reg5_q,
    In6 => reg6_q,

```

```

    In7 => reg7_q,
    Z => src_reg
);

reg00 : reg8 PORT MAP(
    load => load_reg0,
    Clk => Clk,
    D => d_mux,
    Q => reg0_q);

reg01 : reg8 PORT MAP(
    load => load_reg1,
    Clk => Clk,
    D => d_mux,
    Q => reg1_q);

reg02 : reg8 PORT MAP(
    load => load_reg2,
    Clk => Clk,
    D => d_mux,
    Q => reg2_q);

reg03 : reg8 PORT MAP(
    load => load_reg3,
    Clk => Clk,
    D => d_mux,
    Q => reg3_q);

reg04 : reg8 PORT MAP(
    load => load_reg4,
    Clk => Clk,
    D => d_mux,
    Q => reg4_q);

reg05 : reg8 PORT MAP(
    load => load_reg5,
    Clk => Clk,
    D => d_mux,
    Q => reg5_q);

reg06 : reg8 PORT MAP(
    load => load_reg6,
    Clk => Clk,
    D => d_mux,
    Q => reg6_q);

reg07 : reg8 PORT MAP(
    load => load_reg7,
    Clk => Clk,
    D => d_mux,
    Q => reg7_q);

reg0 <= reg0_q;
reg1 <= reg1_q;
reg2 <= reg2_q;
reg3 <= reg3_q;

```

```


reg4 <= reg4_q;
reg5 <= reg5_q;
reg6 <= reg6_q;
reg7 <= reg7_q;

```

```

end Behavioral;

```

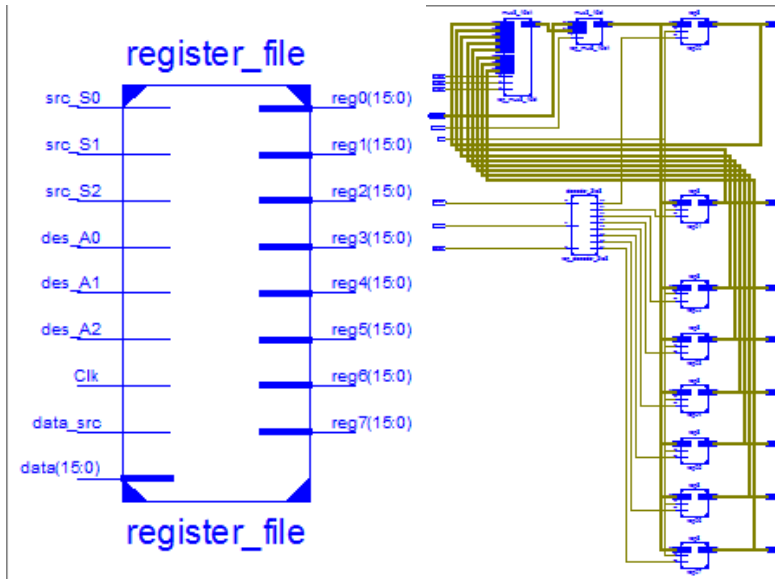


1.2 REG8

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity reg8 is
    Port ( load : in STD_LOGIC;
          Clk : in STD_LOGIC;
          D : in STD_LOGIC_VECTOR(15 downto 0);
          Q : out STD_LOGIC_VECTOR(15 downto 0));
end reg8;

architecture Behavioral of reg8 is

 begin
process(Clk)
begin
    if(rising_edge(Clk)) then
        if(load = '1') then
            Q<= D after 5ns;
        end if;
    end if;
end process;
end Behavioral;
```



1.3 DECODER


```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity decoder_3to8 is
    Port ( A0 : in STD_LOGIC;
          A1 : in STD_LOGIC;
          A2 : in STD_LOGIC;
          Q0 : out STD_LOGIC;
          Q1 : out STD_LOGIC;
          Q2 : out STD_LOGIC;
          Q3 : out STD_LOGIC;
          Q4 : out STD_LOGIC;
          Q5 : out STD_LOGIC;
          Q6 : out STD_LOGIC;
          Q7 : out STD_LOGIC);
end decoder_3to8;

architecture Behavioral of decoder_3to8 is

begin
    Q0 <= (( NOT A0) AND (NOT A1) AND (NOT A2)) AFTER 5ns;
    Q1 <= (( NOT A0) AND (NOT A1) AND A2) AFTER 5ns;
    Q2 <= (( NOT A0) AND A1 AND (NOT A2)) AFTER 5ns;
    Q3 <= (( NOT A0) AND A1 AND A2) AFTER 5ns;
    Q4 <= (A0 AND (NOT A1) AND (NOT A2)) AFTER 5ns;
    Q5 <= (A0 AND (NOT A1) AND A2) AFTER 5ns;
    Q6 <= (A0 AND A1 AND (NOT A2)) AFTER 5ns;
    Q7 <= (A0 AND A1 AND A2) AFTER 5ns;

end Behavioral;
```

 

1.4 MUX3


```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity mux3_16bit is
    Port ( s : in STD_LOGIC;
          In0 : in STD_LOGIC_VECTOR(15 downto 0);
          In1 : in STD_LOGIC_VECTOR(15 downto 0);
          Z : out STD_LOGIC_VECTOR(15 downto 0));
end mux3_16bit;

architecture Behavioral of mux3_16bit is

begin
    Z <= In0 after 5ns when s = '0' else
        In1 after 5ns when s = '1' else
        x"0000" after 5ns;

end Behavioral;
```

 

1.5 MUX8


```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity mux8_16bit is
    Port ( S0 : in STD_LOGIC;
          S1 : in STD_LOGIC;
          S2 : in STD_LOGIC;
          In0 : in STD_LOGIC_VECTOR(15 downto 0);
          In1 : in STD_LOGIC_VECTOR(15 downto 0);
          In2 : in STD_LOGIC_VECTOR(15 downto 0);
          In3 : in STD_LOGIC_VECTOR(15 downto 0);
          In4 : in STD_LOGIC_VECTOR(15 downto 0);
          In5 : in STD_LOGIC_VECTOR(15 downto 0);
          In6 : in STD_LOGIC_VECTOR(15 downto 0);
          In7 : in STD_LOGIC_VECTOR(15 downto 0);
          Z : out STD_LOGIC_VECTOR(15 downto 0));
end mux8_16bit;

architecture Behavioral of mux8_16bit is
begin
    Z <= In0 after 5ns when S0 = '0' and S1 = '0' and S2 = '0' else
        In1 after 5ns when S0 = '0' and S1 = '0' and S2 = '1' else
        In2 after 5ns when S0 = '0' and S1 = '1' and S2 = '0' else
        In3 after 5ns when S0 = '0' and S1 = '1' and S2 = '1' else
        In4 after 5ns when S0 = '1' and S1 = '0' and S2 = '0' else
        In5 after 5ns when S0 = '1' and S1 = '0' and S2 = '1' else
        In6 after 5ns when S0 = '1' and S1 = '1' and S2 = '0' else
        In7 after 5ns when S0 = '1' and S1 = '1' and S2 = '1' else
        x"0000" after 5ns;
end Behavioral;

```

 

2 TESTBENCHES

2.1 REGISTER FILE 1

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--USE ieee.numeric_std.ALL;

ENTITY test_register_file IS
END test_register_file;

ARCHITECTURE behavior OF test_register_file IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT register_file
    PORT(
        src_S0 : IN std_logic;
        src_S1 : IN std_logic;
        src_S2 : IN std_logic;
        des_A0 : IN std_logic;
        des_A1 : IN std_logic;
        des_A2 : IN std_logic;
        Clk : IN std_logic;
        data_src : IN std_logic;
        data : IN std_logic_vector(15 downto 0);
        reg0 : OUT std_logic_vector(15 downto 0);
        reg1 : OUT std_logic_vector(15 downto 0);
        reg2 : OUT std_logic_vector(15 downto 0);
        reg3 : OUT std_logic_vector(15 downto 0);
        reg4 : OUT std_logic_vector(15 downto 0);
        reg5 : OUT std_logic_vector(15 downto 0);
        reg6 : OUT std_logic_vector(15 downto 0);
        reg7 : OUT std_logic_vector(15 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal src_S0 : std_logic := '0';
    signal src_S1 : std_logic := '0';
    signal src_S2 : std_logic := '0';
    signal des_A0 : std_logic := '0';
    signal des_A1 : std_logic := '0';
    signal des_A2 : std_logic := '0';
    signal Clk : std_logic := '0';
    signal data_src : std_logic := '0';
    signal data : std_logic_vector(15 downto 0) := (others => '0');

    --Outputs
    signal reg0 : std_logic_vector(15 downto 0);
    signal reg1 : std_logic_vector(15 downto 0);
```

```

signal reg2 : std_logic_vector(15 downto 0);
signal reg3 : std_logic_vector(15 downto 0);
signal reg4 : std_logic_vector(15 downto 0);
signal reg5 : std_logic_vector(15 downto 0);
signal reg6 : std_logic_vector(15 downto 0);
signal reg7 : std_logic_vector(15 downto 0);

-- Clock period definitions
constant Clk_period : time := 10 ns;

BEGIN

-- Instantiate the Unit Under Test (UUT)
 uut: register_file PORT MAP (
    src_S0 => src_S0,
    src_S1 => src_S1,
    src_S2 => src_S2,
    des_A0 => des_A0,
    des_A1 => des_A1,
    des_A2 => des_A2,
    Clk => Clk,
    data_src => data_src,
    data => data,
    reg0 => reg0,
    reg1 => reg1,
    reg2 => reg2,
    reg3 => reg3,
    reg4 => reg4,
    reg5 => reg5,
    reg6 => reg6,
    reg7 => reg7
  );

-- Clock process definitions
Clk_process :process
begin
  Clk <= '0';
  wait for Clk_period/2;
  Clk <= '1';
  wait for Clk_period/2;
end process;

-- Stimulus process
stim_proc: process
begin
  wait for 10 ns;
  des_A0 <= '0';
  des_A1 <= '0';
  des_A2 <= '0';
  data <= x"FFFF";

  wait for 10 ns;
  des_A0 <= '0';
  des_A1 <= '0';
  des_A2 <= '1';

```

```

data <= x"EEEE";

wait for 10 ns;
des_A0 <= '0';
des_A1 <= '1';
des_A2 <= '0';
data <= x"DDDD";

wait for 10 ns;
des_A0 <= '0';
des_A1 <= '1';
des_A2 <= '1';
data <= x"CCCC";

wait for 10 ns;
des_A0 <= '1';
des_A1 <= '0';
des_A2 <= '0';
data <= x"BBBB";

wait for 10 ns;
des_A0 <= '1';
des_A1 <= '0';
des_A2 <= '1';
data <= x"AAAA";


wait for 10 ns;
des_A0 <= '1';
des_A1 <= '1';
des_A2 <= '0';
data <= x"9999";

wait for 10 ns;
des_A0 <= '1';
des_A1 <= '1';
des_A2 <= '1';
data <= x"0000";

end process;

END;

```

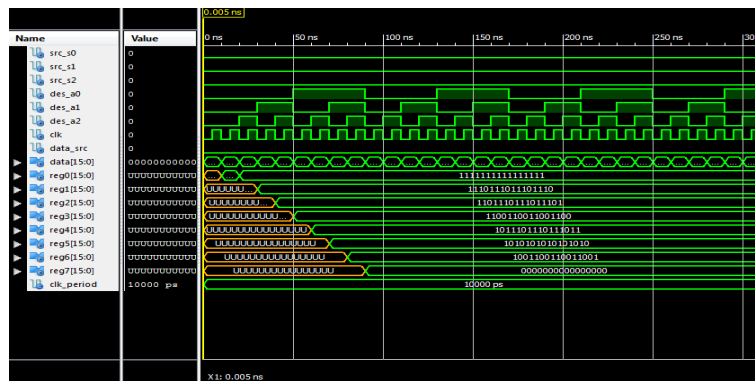

2.2 REGISTER FILE 2

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--USE ieee.numeric_std.ALL;

ENTITY test_register_file_2 IS
END test_register_file_2;

ARCHITECTURE behavior OF test_register_file_2 IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT register_file
    PORT(
        src_S0 : IN std_logic;
        src_S1 : IN std_logic;
        src_S2 : IN std_logic;
        des_A0 : IN std_logic;
        des_A1 : IN std_logic;
        des_A2 : IN std_logic;
        Clk : IN std_logic;
        data_src : IN std_logic;
        data : IN std_logic_vector(15 downto 0);
        reg0 : OUT std_logic_vector(15 downto 0);
        reg1 : OUT std_logic_vector(15 downto 0);
        reg2 : OUT std_logic_vector(15 downto 0);
        reg3 : OUT std_logic_vector(15 downto 0);
        reg4 : OUT std_logic_vector(15 downto 0);
        reg5 : OUT std_logic_vector(15 downto 0);
        reg6 : OUT std_logic_vector(15 downto 0);
        reg7 : OUT std_logic_vector(15 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal src_S0 : std_logic := '0';
    signal src_S1 : std_logic := '0';
    signal src_S2 : std_logic := '0';
    signal des_A0 : std_logic := '0';
    signal des_A1 : std_logic := '0';
    signal des_A2 : std_logic := '0';
    signal Clk : std_logic := '0';
    signal data_src : std_logic := '0';
    signal data : std_logic_vector(15 downto 0) := (others => '0');

    --Outputs
    signal reg0 : std_logic_vector(15 downto 0);
    signal reg1 : std_logic_vector(15 downto 0);
    signal reg2 : std_logic_vector(15 downto 0);
    signal reg3 : std_logic_vector(15 downto 0);
    signal reg4 : std_logic_vector(15 downto 0);
```

```

signal reg5 : std_logic_vector(15 downto 0);
signal reg6 : std_logic_vector(15 downto 0);
signal reg7 : std_logic_vector(15 downto 0);

-- Clock period definitions
constant Clk_period : time := 10 ns;

BEGIN

-- Instantiate the Unit Under Test (UUT)
 uut: register_file PORT MAP (
    src_S0 => src_S0,
    src_S1 => src_S1,
    src_S2 => src_S2,
    des_A0 => des_A0,
    des_A1 => des_A1,
    des_A2 => des_A2,
    Clk => Clk,
    data_src => data_src,
    data => data,
    reg0 => reg0,
    reg1 => reg1,
    reg2 => reg2,
    reg3 => reg3,
    reg4 => reg4,
    reg5 => reg5,
    reg6 => reg6,
    reg7 => reg7
  );

-- Clock process definitions
 Clk_process :process
begin
  Clk <= '0';
  wait for Clk_period/2;
  Clk <= '1';
  wait for Clk_period/2;
end process;

-- Stimulus process
stim_proc: process
begin

  wait for 10ns;
  data <= x"FFFF";
  des_A0 <= '0';
  des_A1 <= '0';
  des_A2 <= '0';

  src_S0 <= '0';
  src_S0 <= '0';
  src_S0 <= '0';

  wait for 20ns;

```

```

    data <= x"EEEE";
    des_A0 <= '0';
    des_A1 <= '0';
    des_A2 <= '1';

    src_S0 <= '0';
    src_S0 <= '0';
    src_S0 <= '1';

wait for 30ns;
    data <= x"DDDD";
    des_A0 <= '0';
    des_A1 <= '1';
    des_A2 <= '0';

    src_S0 <= '0';
    src_S0 <= '1';
    src_S0 <= '0';

wait for 40ns;
    data <= x"CCCC";
    des_A0 <= '0';
    des_A1 <= '1';
    des_A2 <= '1';

    src_S0 <= '0';
    src_S0 <= '1';
    src_S0 <= '1';

wait for 50ns;
    data <= x"BBBB";
    des_A0 <= '1';
    des_A1 <= '0';
    des_A2 <= '0';

    src_S0 <= '1';
    src_S0 <= '0';
    src_S0 <= '0';

wait for 60ns;
    data <= x"AAAA";
    des_A0 <= '1';
    des_A1 <= '0';
    des_A2 <= '1';

    src_S0 <= '1';
    src_S0 <= '0';
    src_S0 <= '1';

wait for 70ns;
    data <= x"9999";
    des_A0 <= '1';
    des_A1 <= '1';
    des_A2 <= '0';

```


END;



2.3 REG8

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY test_reg8 IS
END test_reg8;

ARCHITECTURE behavior OF test_reg8 IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT reg8
    PORT(
        load : IN std_logic;
        Clk : IN std_logic;
        D : IN std_logic_vector(15 downto 0);
        Q : OUT std_logic_vector(15 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal load : std_logic := '0';
    signal Clk : std_logic := '0';
    signal D : std_logic_vector(15 downto 0) := (others => '0');

    --Outputs
    signal Q : std_logic_vector(15 downto 0);

    -- Clock period definitions
    constant Clk_period : time := 10 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: reg8 PORT MAP (
        load => load,
        Clk => Clk,
        D => D,
        Q => Q
    );

    -- Clock process definitions
    Clk_process :process
    begin
        Clk <= '0';
        wait for Clk_period/2;
        Clk <= '1';
        wait for Clk_period/2;
    end process;

    -- Stimulus process
```

```

stim_proc: process
begin
wait for 10ns;
D <= x"FFFF";
load <= '1';


wait for 10ns;
load <= '0';

wait for 10ns;
D<= x"AAAA";
load <= '1';

wait for 10ns;
load <= '0';

end process;
END;

```

 

2.4 DECODER

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--USE ieee.numeric_std.ALL;

ENTITY test_decoder_3to8 IS
END test_decoder_3to8;

ARCHITECTURE behavior OF test_decoder_3to8 IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT decoder_3to8
    PORT(
        A0 : IN std_logic;
        A1 : IN std_logic;
        A2 : IN std_logic;
        Q0 : OUT std_logic;
        Q1 : OUT std_logic;
        Q2 : OUT std_logic;
        Q3 : OUT std_logic;
        Q4 : OUT std_logic;
        Q5 : OUT std_logic;
        Q6 : OUT std_logic;
        Q7 : OUT std_logic
    );
    END COMPONENT;

    --Inputs
    signal A0 : std_logic := '0';
    signal A1 : std_logic := '0';
    signal A2 : std_logic := '0';

    --Outputs
    signal Q0 : std_logic;
    signal Q1 : std_logic;
    signal Q2 : std_logic;
    signal Q3 : std_logic;
    signal Q4 : std_logic;
    signal Q5 : std_logic;
    signal Q6 : std_logic;
    signal Q7 : std_logic;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: decoder_3to8 PORT MAP (
        A0 => A0,
        A1 => A1,
        A2 => A2,
        Q0 => Q0,
```

```

        Q1 => Q1,
        Q2 => Q2,
        Q3 => Q3,
        Q4 => Q4,
        Q5 => Q5,
        Q6 => Q6,
        Q7 => Q7
    );

-- Stimulus process
stim_proc: process
begin
    wait for 10ns;
    A0 <= '0';
    A1 <= '0';
    A2 <= '0';

    wait for 10ns;
    A0 <= '0';
    A1 <= '0';
    A2 <= '1';

    wait for 10ns;
    A0 <= '0';
    A1 <= '1';
    A2 <= '0';

    wait for 10ns;
    A0 <= '0';
    A1 <= '1';
    A2 <= '1';

    wait for 10ns;
    A0 <= '1';
    A1 <= '0';
    A2 <= '0';


    wait for 10ns;
    A0 <= '1';
    A1 <= '1';
    A2 <= '0';

    wait for 10ns;
    A0 <= '1';
    A1 <= '1';
    A2 <= '1';

end process;

END;

```

 

2.5 MUX3

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY test_mux3_16bit IS
END test_mux3_16bit;

ARCHITECTURE behavior OF test_mux3_16bit IS

    COMPONENT mux3_16bit
    PORT(
        s : IN std_logic;
        In0 : IN std_logic_vector(15 downto 0);
        In1 : IN std_logic_vector(15 downto 0);
        Z : OUT std_logic_vector(15 downto 0)
    );
    END COMPONENT;

    --Inputs for the in0 and in1
    signal s : std_logic := '0';
    signal In0 : std_logic_vector(15 downto 0) := (others => '0');
    signal In1 : std_logic_vector(15 downto 0) := (others => '0');

    --Outputs
    signal Z : std_logic_vector(15 downto 0);
    -- No clocks detected in port list. Replace <clock> below with
    -- appropriate port name

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: mux3_16bit PORT MAP (
        s => s,
        In0 => In0,
        In1 => In1,
        Z => Z
    );

    -- Signals tested are here below
    stim_proc: process
    begin
        wait for 10ns;
        In0<= x"FFFF";
        In1<= X"AAAA";

        wait for 10ns;
        s <= '1';

        wait for 10ns;
```

```


s <= '0';

wait for 10ns;
s <= '0';

wait;
end process;

END;

```

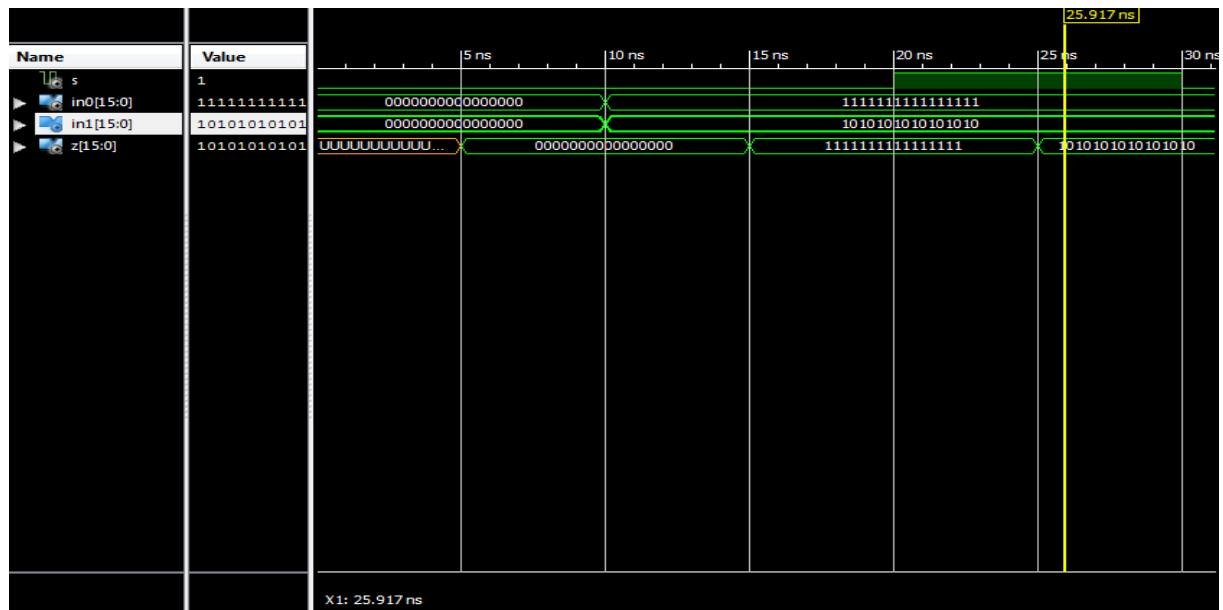

2.6 MUX8

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--USE ieee.numeric_std.ALL;

ENTITY test_mux8_16bit IS
END test_mux8_16bit;

ARCHITECTURE behavior OF test_mux8_16bit IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT mux8_16bit
    PORT(
        S0 : IN std_logic;
        S1 : IN std_logic;
        S2 : IN std_logic;
        In0 : IN std_logic_vector(15 downto 0);
        In1 : IN std_logic_vector(15 downto 0);
        In2 : IN std_logic_vector(15 downto 0);
        In3 : IN std_logic_vector(15 downto 0);
        In4 : IN std_logic_vector(15 downto 0);
        In5 : IN std_logic_vector(15 downto 0);
        In6 : IN std_logic_vector(15 downto 0);
        In7 : IN std_logic_vector(15 downto 0);
        Z : OUT std_logic_vector(15 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal S0 : std_logic := '0';
    signal S1 : std_logic := '0';
    signal S2 : std_logic := '0';
    signal In0 : std_logic_vector(15 downto 0) := (others => '0');
    signal In1 : std_logic_vector(15 downto 0) := (others => '0');
    signal In2 : std_logic_vector(15 downto 0) := (others => '0');
    signal In3 : std_logic_vector(15 downto 0) := (others => '0');
    signal In4 : std_logic_vector(15 downto 0) := (others => '0');
    signal In5 : std_logic_vector(15 downto 0) := (others => '0');
    signal In6 : std_logic_vector(15 downto 0) := (others => '0');
    signal In7 : std_logic_vector(15 downto 0) := (others => '0');

    --Outputs
    signal Z : std_logic_vector(15 downto 0);

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: mux8_16bit PORT MAP (
        S0 => S0,
        S1 => S1,
```

```

        S2 => S2,
        In0 => In0,
        In1 => In1,
        In2 => In2,
        In3 => In3,
        In4 => In4,
        In5 => In5,
        In6 => In6,
        In7 => In7,
        Z => Z
    );

-- Stimulus process
stim_proc: process
begin

    In0 <= x"FFFF";
    In0 <= x"EEEE";
    In0 <= x"DDDD";
    In0 <= x"CCCC";
    In0 <= x"BBBB";
    In0 <= x"AAAA";
    In0 <= x"9999";
    In0 <= x"0000";

    wait for 10ns;
    S0 <= '0';
    S1 <= '0';
    S2 <= '0';

    wait for 10ns;
    S0 <= '0';
    S1 <= '0';
    S2 <= '1';

    wait for 10ns;
    S0 <= '0';
    S1 <= '1';
    S2 <= '0';

    wait for 10ns;
    S0 <= '0';
    S1 <= '1';
    S2 <= '1';

    wait for 10ns;
    S0 <= '1';
    S1 <= '0';
    S2 <= '0';

    wait for 10ns;
    S0 <= '1';
    S1 <= '0';
    S2 <= '1';

```

```

        wait for 10ns;
        S0 <= '1';
        S1 <= '1';
        S2 <= '0';

        wait for 10ns;
        S0 <= '1';
        S1 <= '1';
        S2 <= '1';
    end process;

END;

```

